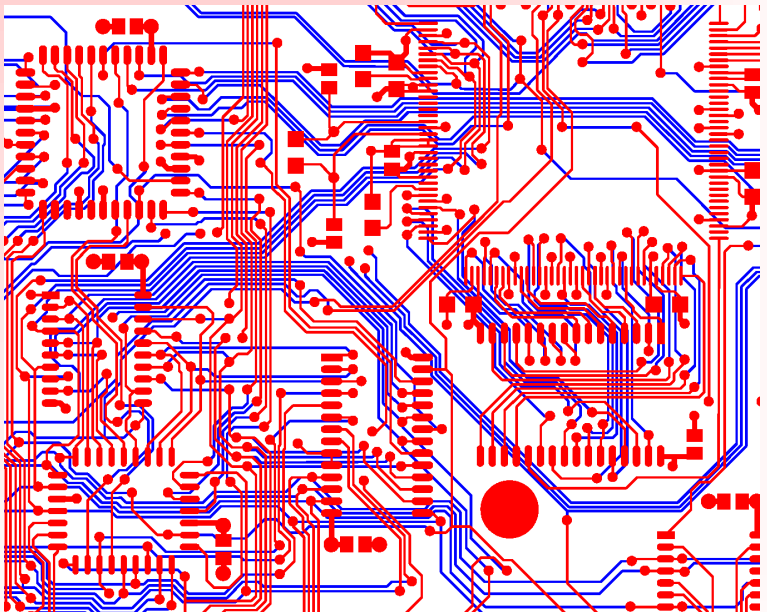


Seminar 32


Tutorial on Echo and Crosstalk in Printed Circuit Boards and Multi-Chip Modules — Lecture Slides

Second Edition

Frédéric Broydé & Evelyne Clavelier



Excem

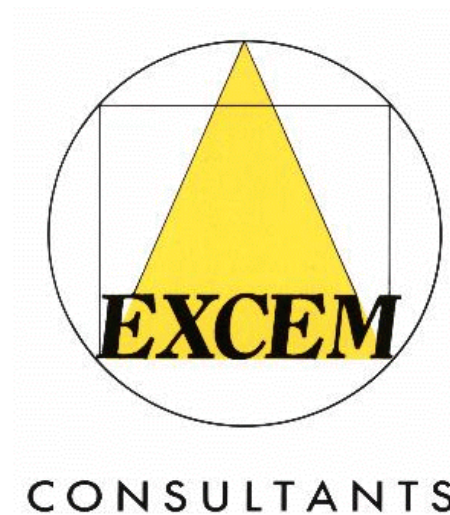

Seminar 32

Tutorial on Echo and Crosstalk in Printed Circuit Boards and Multi-Chip Modules — Lecture Slides

Second Edition

Frédéric Broydé & Evelyne Clavelier

Excem
12, chemin des Hauts de Clairefontaine
78580 Maule, France
<http://www.eurexcem.com>



Copyright © 2012 by Excem

© Excem, 2012

All rights reserved
Published by Excem

Tous droits réservés
Editeur: Excem

ISBN 978-2-909056-06-7

All rights reserved. Except as permitted under articles L.122-5 of the “Code de la propriété intellectuelle” of France, no part of this book may be reproduced in any form or by any means, without the prior written permission of Excem.

Excem grants you a personal non-exclusive free license to access and store an electronic version of this work (referred to as “The E-Book”) according to the following terms. The E-Book is the property of Excem and is protected by the copyright law of France and international copyright treaty provisions. The E-Book is for private use only. Public display and commercial use of The E-book are prohibited. Printing The E-book is prohibited.

Limit of liability and disclaimer of warranty: while Excem and the authors have used their best effort in preparing this book, they make no representation or warranties with respect to the accuracy or completeness of the contents of this book and specifically disclaim any implied warranties of merchantability or fitness for a particular purpose. Neither Excem nor the authors shall be liable for any loss of profits or any other commercial damage.

Registration of copyright: February 2012

Dépôt Légal: février 2012



Foreword

This tutorial explains and compares classical and innovative techniques for controlling crosstalk and echo in printed circuit assemblies and multi-chip modules.

The first part of the tutorial presents propagation models based on the theory of multiconductor transmission lines (MTLs). This theoretical part uses matrix algebra, but is not difficult to follow. It is focused on the following points which are essential for the applications considered in the second part: concisely presenting the MTL model; identifying a few common misconceptions on modal voltages and currents; comparing bi-orthonormal eigenvectors with associated eigenvectors; and explaining the total decoupling of the telegrapher's equations.

In a second part, this theoretical framework is used to describe and analyze most known techniques for reducing crosstalk and echo in a uniform multiconductor interconnection. Here, the purpose is the reduction of the number of transmission conductors and their spacing. The effect of discontinuities such as vias, connectors, etc, is not covered. The following schemes are considered: multiple single-ended links, multiple differential links, links implementing modal transmission schemes and multichannel pseudo-differential links.

*Howard L. Heck
Principal engineer at Intel Corporation
Hillsboro, Oregon
September 2011*



Table of Contents

Part A — Propagation models

1. Introduction and definitions	6
2. The 2-conductor transmission line in the frequency domain	11
3. Problems involving a TL and linear terminations	17
4. Telegrapher's equations of a uniform MTL and modal decomposition	23
5. The characteristic impedance matrix	29
6. Biorthonormal eigenvectors and associated eigenvectors	33
7. The choice of eigenvectors and total decoupling	37
8. Propagation in the frequency domain	43
9. Matched termination circuit and pseudo-matched terminations	47
10. Problems involving an MTL and linear terminations	52



Part B — Techniques for reducing crosstalk and echo

11. The degradation of transmitted signals	59
12. Single-ended parallel links	64
13. Multichannel differential links	77
14. Modal signaling	91
15. Modal signaling in a decoupled interconnection	103
16. Pseudo-differential links	111
Appendix	132
Bibliography	134
Annexes	143



1. Introduction and definitions

- ❑ This tutorial is about a physical device called *interconnection*, which is used as a part of a *link* used for signal transmission. We emphasize the case where the interconnection is built in a PCB or MCM.
- ❑ We shall use multiconductor transmission line (MTL) theory to explain and compare classical and innovative techniques for controlling crosstalk and echo.
- ❑ This tutorial is derived from a much more comprehensive training seminar of Excem, the Seminar 33. Many questions could not be included in the present tutorial.
- ❑ In a first part, we present propagation models based on MTL theory. This allows us to:
 - ◆ define and study modal voltages and currents;
 - ◆ compare bi-orthonormal eigenvectors with associated eigenvectors;
 - ◆ explain the total decoupling of the telegrapher's equations.



- ❑ In a second part, this background is used to describe and analyze most known techniques for reducing crosstalk and echo in a uniform multiconductor interconnection. We will focus on innovative techniques.
- ❑ In circuit theory, interconnections are represented using a 0-D model: the node.
- ❑ The transmission line (TL) model of a two-conductor interconnection may be regarded as:
 - ◆ a simplified 1-D model as regards propagation along the interconnection;
 - ◆ a static 2-D model for the computation of the p.u.l. parameters.
- ❑ The MTL model extends the TL model to problems involving multiple conductors.
- ❑ Why are we devoting time to the MTL model when full-wave 3-D software is available?



- ❑ Rule A: the more comprehensive the model, the smaller the problems it can handle.
- ❑ Rule B: optimization is useful only when a small number of dominant parameters has been identified.
- ❑ Rule C: invention occurs only when the inventor has a simple mental image of the problem and the effect of each main parameter.
- ❑ The best model and problem combination is the one that gives the best result for your objectives, your budget and your deadlines:
 - ◆ for exploring innovative solution, analytical formula provide more insight;
 - ◆ at the initial design stage, no detailed 3-D configuration is specified;
 - ◆ for the analysis of a finalized design, the 3-D data is available (and large).



- ❑ If we use basic circuit theory, where each interconnection is a node, our model ignores the actual behavior of interconnections: it is inaccurate at high frequencies.
- ❑ If we use an enhanced circuit theory where some lumped elements (e.g. a stray capacitance, or a pi network) are used to model the longer interconnections:
 - ◆ our model is more accurate in the lumped-element region [31, ch. 3];
 - ◆ an LC pi network nearing resonance indicates that we have left this region.
- ❑ If we use a TL model for the longer interconnections:
 - ◆ our model describes propagation and reflections;
 - ◆ it allows us to reduce echo and to compensate losses;
 - ◆ it ignores the effect of nearby conductors, which cannot be controlled.
- ❑ If we use a MTL model for the longer interconnections:
 - ◆ our model accurately describes the interactions between conductors;
 - ◆ it allows us to control echo, internal crosstalk and losses.



❑ In this tutorial:

- ◆ interactions between conductors within a multiconductor interconnection are treated using an MTL model;
- ◆ circuit models are used for other parts of the link, with caution;
- ◆ interactions between conductors belonging to different parallel interconnections are treated using a single MTL model;
- ◆ other interactions involving conductors are not considered;
- ◆ emission and immunity, as defined in electromagnetic compatibility (EMC), are not considered.

❑ *Uniform* means invariant along the interconnection or TL or MTL.

❑ *Homogeneous* means invariant in a cross-section of the interconnection or TL or MTL.



2. The 2-conductor transmission line in the frequency domain

- We consider an interconnection with 1 transmission conductor (TC) placed close to a reference conductor (GC) used as a reference for voltage measurements.
- Important: the GC is not necessarily a ground conductor or a combination of ground conductors.
- We define:
 - ◆ the curvilinear abscissa z , the interconnection extending from $z = 0$ to $z = \mathcal{L}$;
 - ◆ the natural current i as the current flowing on the TC, toward $z = \mathcal{L}$;
 - ◆ the natural voltage v as the voltage between the TC and the GC.
- i and v are z -dependent.



- Except when otherwise stated, we shall consider frequency domain quantities and $\sqrt{}$ is always used to denote the principal root.
- We assume that the interconnection can be modeled as a TL. The TL model uses:
 - ◆ a p.u.l. impedance Z' and a p.u.l. admittance Y' ;
 - ◆ the telegrapher's equations

$$\begin{cases} \frac{dv}{dz} = -Z'i \\ \frac{di}{dz} = -Y'v \end{cases} \quad (1)$$

- Z' and Y' are frequency-dependent. Z' and Y' must each represent passive linear systems. Thus, their real part is nonnegative.
- The TL is lossless if and only if $Z' = j\omega L'$ and $Y' = j\omega C'$ where L' and C' are real. In this case, L' and C' must be frequency independent.



□ The TL is said to be uniform if Z' and Y' are independent of z .

□ Assuming a uniform TL, we can derive two second order differential equations

$$\begin{cases} \frac{d^2 v}{dz^2} - Y'Z' v = 0 \\ \frac{d^2 i}{dz^2} - Y'Z' i = 0 \end{cases} \quad (2)$$

□ The general solution of (2) can be written

$$\begin{cases} v = v_{0+} e^{-z\gamma} + v_{0-} e^{z\gamma} \\ i = i_{0+} e^{-z\gamma} + i_{0-} e^{z\gamma} \end{cases} \quad (3)$$

where v_{0+} , v_{0-} , i_{0+} and i_{0-} are z -independent scalars determined by the boundary conditions at $z = 0$ and $z = L$ and where the propagation constant γ is given by:

$$\gamma = \sqrt{Y'Z'} \quad (4)$$

□ $v_{0+} e^{-\gamma z}$ and $i_{0+} e^{-\gamma z}$ propagate with the propagation constant γ toward the far-end;
 $v_{0-} e^{\gamma z}$ and $i_{0-} e^{\gamma z}$ propagate with the propagation constant $-\gamma$ toward the near-end.

□ The characteristic impedance Z_C is defined by

$$Z_C = \sqrt{\frac{Z'}{Y'}} \quad (5)$$

and it is such that

$$\begin{cases} v_{0+} = Z_C i_{0+} \\ v_{0-} = -Z_C i_{0-} \end{cases} \quad (6)$$

□ We define

- ◆ the voltage traveling toward the far-end, given by $v_+ = v_{0+} e^{-\gamma z}$;
- ◆ the voltage traveling toward the near-end, given by $v_- = v_{0-} e^{\gamma z}$;
- ◆ the current traveling toward the far-end, given by $i_+ = i_{0+} e^{-\gamma z}$;
- ◆ the current traveling toward the near-end, given by $i_- = i_{0-} e^{\gamma z}$.



□ We have

$$\begin{cases} v = v_+ + v_- \\ i = i_+ + i_- \end{cases} \quad \begin{cases} v_+ = Z_C i_+ \\ v_- = -Z_C i_- \end{cases} \quad (7)$$

and, consequently

$$v_+ = \frac{v + Z_C i}{2} \quad v_- = \frac{v - Z_C i}{2} \quad (8)$$

□ For a lossless TL, $Z' = j\omega L'$ and $Y' = j\omega C'$ where L' and C' are real. Thus,


$$\gamma = j\omega \sqrt{L'C'} \quad Z_C = \sqrt{\frac{L'}{C'}} \quad (9)$$

so that $c = 1/\sqrt{L'C'}$ is the propagation velocity in the TL. The travel time is $\tau = \frac{L}{c}$.

□ For a lossless TL in an homogeneous dielectric, we also have

$$L'C' = \frac{\epsilon_r}{c_0^2} = \frac{1}{c^2} \quad (10)$$

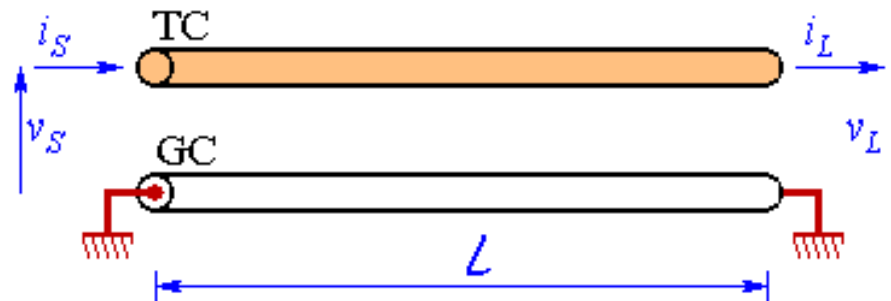where ϵ_r is the relative permittivity of the dielectric.



□ A scattering matrix of the interconnection, denoted by $\mathcal{S}(L)$ and defined by

$$\begin{pmatrix} v_S - Z_C i_S \\ v_L + Z_C i_L \end{pmatrix} = \mathcal{S}(L) \begin{pmatrix} v_S + Z_C i_S \\ v_L - Z_C i_L \end{pmatrix} \quad (11)$$

is given by

$$\mathcal{S}(L) = e^{-\gamma L} \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \quad (12)$$


Proof. This is a direct consequence of (3) and (8). □

□ $\mathcal{S}(L)$ is the usual scattering matrix of a 2-port only when Z_C is real.

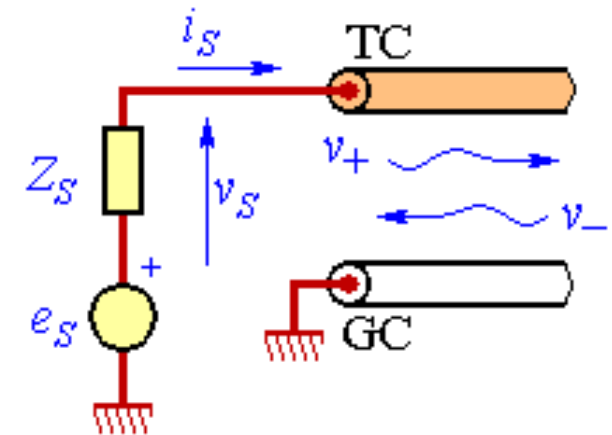3. Problems involving a TL and linear terminations

□ At the near-end, in the configuration shown, we have

$$\begin{cases} v_S = e_S - Z_S i_S \\ v_S = v_+ + v_- \\ i_S = \frac{v_+ - v_-}{Z_C} \end{cases} \quad (13)$$



we obtain


$$v_+ = \frac{Z_C}{Z_S + Z_C} e_S + \rho_S v_- = \frac{1 - \rho_S}{2} e_S + \rho_S v_- \quad (14)$$

where, in this configuration, the voltage reflection coefficient is defined by

$$\rho_S = \frac{Z_S - Z_C}{Z_S + Z_C} \quad (15)$$

□ At the far-end, in the configuration shown, we have
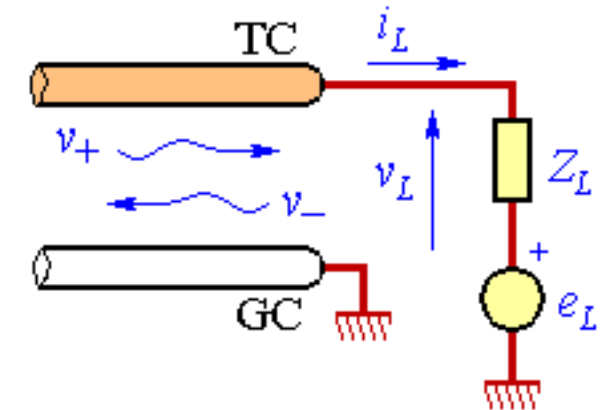
$$\begin{cases} v_L = e_L + Z_L i_L \\ v_L = v_+ + v_- \\ i_L = \frac{v_+ - v_-}{Z_C} \end{cases} \quad (16)$$



we obtain


$$v_- = \frac{Z_C}{Z_L + Z_C} e_L + \rho_L v_+ = \frac{1 - \rho_L}{2} e_L + \rho_L v_+ \quad (17)$$

where, in this configuration, the voltage reflection coefficient is defined by

$$\rho_L = \frac{Z_L - Z_C}{Z_L + Z_C} \quad (18)$$

□ It is also possible to define current reflection coefficients.

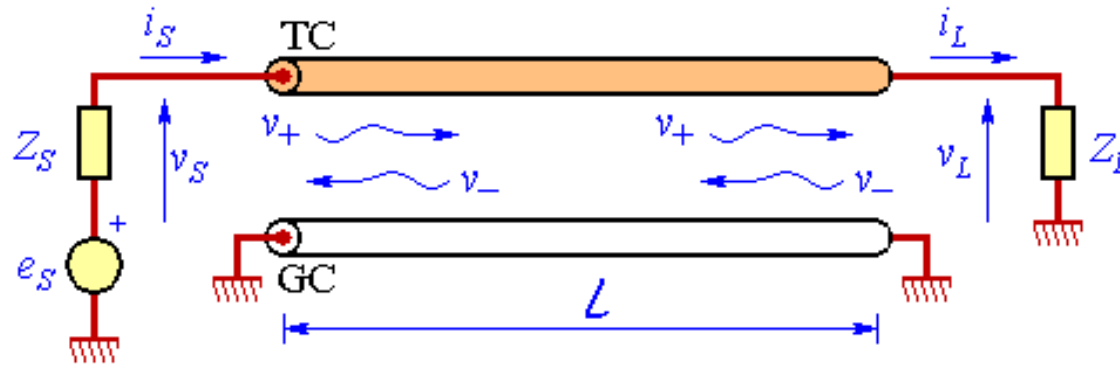□ A termination is matched when it produces no reflection, i.e. for $Z_S = Z_C$ or $Z_L = Z_C$ (we are referring to reflectionless matching, as opposed to conjugate matching).



- Three possible approaches to find v_S and v_L in the configuration shown above:
 - ◆ using the boundary conditions to find v_{0+} , v_{0-} , i_{0+} and i_{0-} in (3);
 - ◆ using the scattering matrix defined by (12) and the reflection coefficients;
 - ◆ using the chain matrix (not studied in this tutorial).


- Following the second approach, we consider multiple reflections occurring at the near-end and at the far-end, and multiple propagation through the TL. We get:

$$\left\{ \begin{array}{l} v_+(0) = e_S \frac{Z_C}{Z_S + Z_C} \sum_{p=0}^{\infty} (\rho_L \rho_S e^{-2\gamma L})^p \\ v_+(L) = e_S \frac{Z_C e^{-\gamma L}}{Z_S + Z_C} \sum_{p=0}^{\infty} (\rho_L \rho_S e^{-2\gamma L})^p \end{array} \right. \quad \text{and} \quad \left\{ \begin{array}{l} v_S = v_+(0) [1 + \rho_L e^{-2\gamma L}] \\ v_L = v_+(L) [1 + \rho_L] \end{array} \right. \quad (19)$$


Thus, we obtain

$$\begin{cases} v_S = \frac{e_S Z_C}{Z_S + Z_C} \frac{1 + \rho_L e^{-2\gamma L}}{1 - \rho_L \rho_S e^{-2\gamma L}} \\ v_L = \frac{e_S Z_C e^{-\gamma L}}{Z_S + Z_C} \frac{1 + \rho_L}{1 - \rho_L \rho_S e^{-2\gamma L}} \end{cases} \quad (20)$$

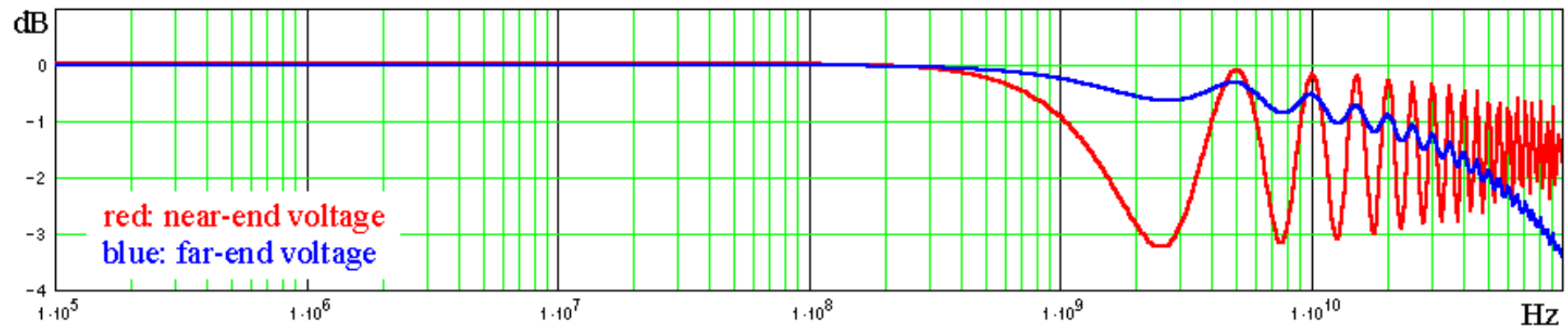
□ An example involving a 20-mm long microstrip built on an enhanced high-speed multifunctional epoxy material. Taking resistive losses and dielectric losses into account in (20) yields:



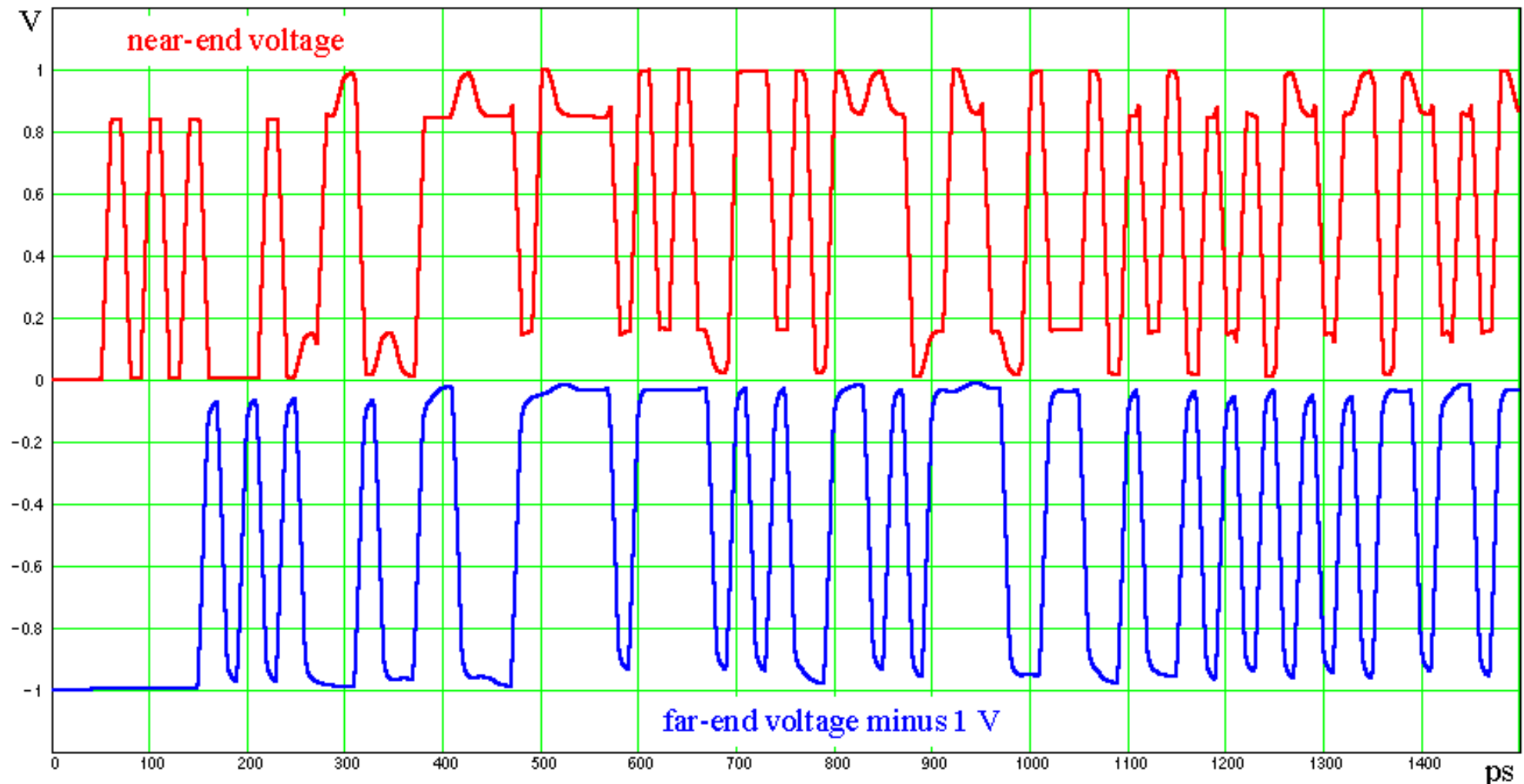□ Time domain results can also be obtained,
here for the unipolar non-return-to-zero level (NRZ-L) sequence
0010101000100110001111101111010100110101111001100100101010101011....:




□ And also eye diagrams

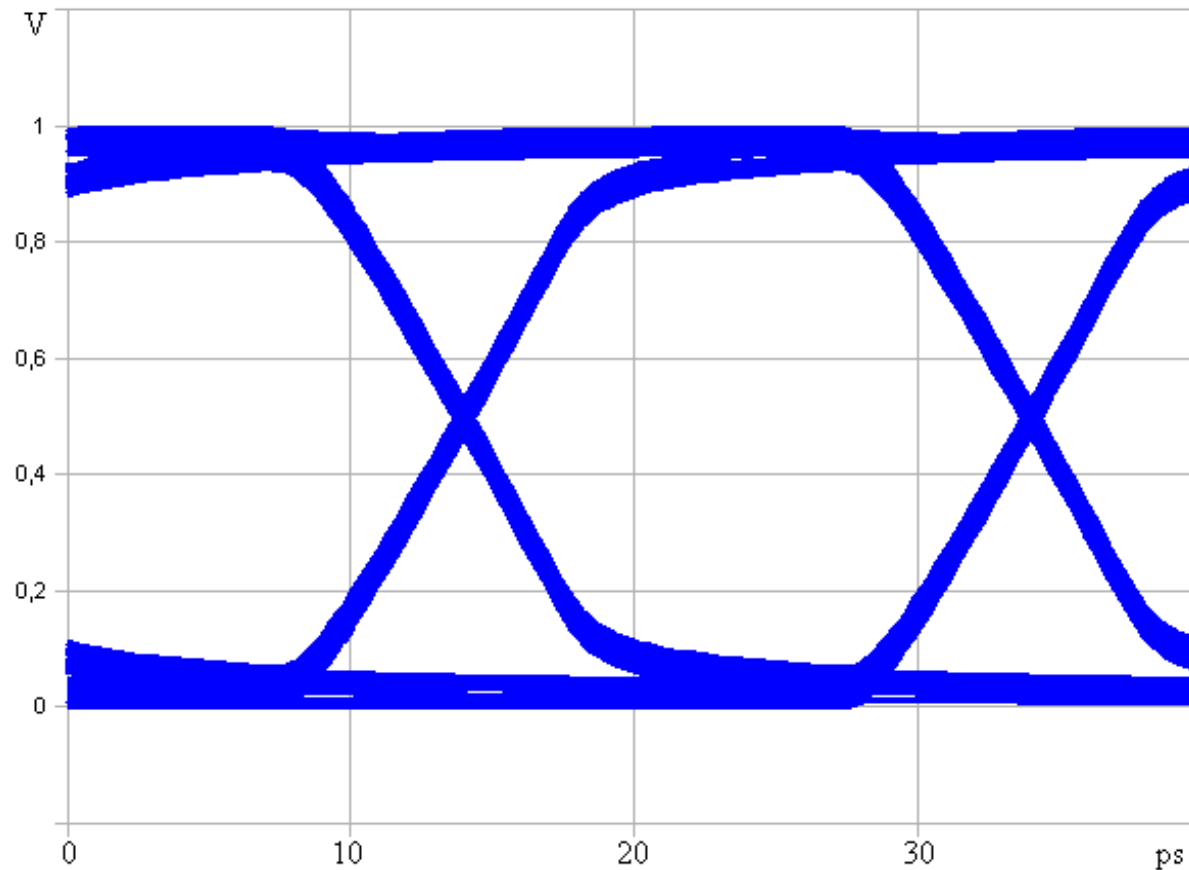

□ All results shown were obtained using a standard numerical computation program.

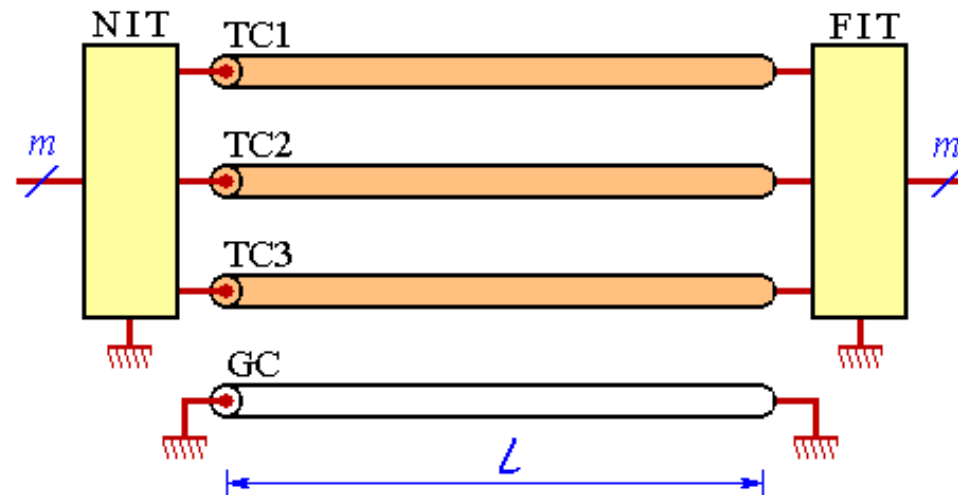4. Telegrapher's equations of a uniform MTL and modal decomposition



- We consider a link providing m channels comprising:
- ◆ an interconnection having n TCs and a GC, where $n \geq m$;
 - ◆ a near-end interface and termination device (NIT);
 - ◆ a far-end interface and termination device (FIT).



- ❑ The GC is used as a reference for voltage measurements.
- ❑ Important: the GC is not necessarily a ground conductor or a combination of ground conductors.
- ❑ We number the TCs from 1 to n , and we define:
 - ◆ the curvilinear abscissa z , the interconnection extending from $z = 0$ to $z = L$;
 - ◆ the natural current i_j as the current flowing on the TC j , toward $z = L$;
 - ◆ the natural voltage v_j as the voltage between the TC j and the GC;
 - ◆ the column vector \mathbf{i} of the natural currents i_1, \dots, i_n , which depends on z ;
 - ◆ the column vector \mathbf{v} of the natural voltages v_1, \dots, v_n , which depends on z .
- ❑ Except when otherwise stated, we shall consider frequency domain quantities.

□ We assume that the interconnection can be modeled as a MTL. The $(n + 1)$ -conductor MTL model uses [1]:

- ◆ a p.u.l. impedance matrix \mathbf{Z}' and a p.u.l. admittance matrix \mathbf{Y}' ;
- ◆ the telegrapher's equations

$$\begin{cases} \frac{d \mathbf{v}}{dz} = -\mathbf{Z}' \mathbf{i} \\ \frac{d \mathbf{i}}{dz} = -\mathbf{Y}' \mathbf{v} \end{cases} \quad (21)$$

□ \mathbf{Z}' and \mathbf{Y}' are frequency-dependent symmetric matrices of size $n \times n$. \mathbf{Z}' and \mathbf{Y}' must each represent a passive linear system. Thus, their real part is positive semidefinite [8, § 7.1]. We shall assume that \mathbf{Z}' and \mathbf{Y}' are invertible.

□ The MTL is lossless if and only if $\mathbf{Z}' = j\omega \mathbf{L}'$ and $\mathbf{Y}' = j\omega \mathbf{C}'$ where \mathbf{L}' and \mathbf{C}' are real matrices of size $n \times n$. In this case, \mathbf{L}' and \mathbf{C}' must be frequency independent.

□ The MTL is said to be uniform if \mathbf{Z}' and \mathbf{Y}' are independent of z .

□ Assuming a uniform MTL, we can derive two second order differential equations

$$\begin{cases} \frac{d^2 \mathbf{v}}{dz^2} - \mathbf{Z}' \mathbf{Y}' \mathbf{v} = \mathbf{0} \\ \frac{d^2 \mathbf{i}}{dz^2} - \mathbf{Y}' \mathbf{Z}' \mathbf{i} = \mathbf{0} \end{cases} \quad (22)$$

□ $\mathbf{Z}' \mathbf{Y}'$ and $\mathbf{Y}' \mathbf{Z}'$ are similar [8, § 1.3.20]. We shall assume that $\mathbf{Z}' \mathbf{Y}'$ is diagonalizable. In this case, there exists two invertible matrices \mathbf{T} and \mathbf{S} such that:

$$\begin{cases} \mathbf{T}^{-1} \mathbf{Y}' \mathbf{Z}' \mathbf{T} = \Gamma^2 \\ \mathbf{S}^{-1} \mathbf{Z}' \mathbf{Y}' \mathbf{S} = \Gamma^2 \end{cases} \quad \text{where} \quad \Gamma = \text{diag}_n(\gamma_1, \dots, \gamma_n) \quad (23)$$

is the diagonal matrix of order n of the propagation constants γ_i , chosen with an argument $\psi \in]-\pi/2, \pi/2]$, so that the γ_i are principal square roots.

□ **T** and **S** define a *modal transform* for the natural currents and the natural voltages. We define \mathbf{v}_M and \mathbf{i}_M by

$$\begin{cases} \mathbf{v} = \mathbf{S} \mathbf{v}_M \\ \mathbf{i} = \mathbf{T} \mathbf{i}_M \end{cases} \quad (24)$$

where

- ◆ we use \mathbf{i}_M to denote the vector of the n modal currents i_{M1}, \dots, i_{Mn} ;
- ◆ we use \mathbf{v}_M to denote the vector of the n modal voltages v_{M1}, \dots, v_{Mn} ;
- ◆ we call **S** the *transition matrix from modal voltages to natural voltages*;
- ◆ we call **T** the *transition matrix from modal currents to natural currents*.

□ Using (23) and (24), (22) takes on a form which contains n times (2):

$$\begin{cases} \frac{d^2 \mathbf{v}_M}{dz^2} - \Gamma^2 \mathbf{v}_M = \mathbf{0} \\ \frac{d^2 \mathbf{i}_M}{dz^2} - \Gamma^2 \mathbf{i}_M = \mathbf{0} \end{cases} \quad (25)$$

□ The general solution of (25) is

$$\begin{cases} \mathbf{v}_M = e^{-z\Gamma} \mathbf{v}_{M0+} + e^{z\Gamma} \mathbf{v}_{M0-} \\ \mathbf{i}_M = e^{-z\Gamma} \mathbf{i}_{M0+} + e^{z\Gamma} \mathbf{i}_{M0-} \end{cases} \quad (26)$$

where \mathbf{v}_{M0+} , \mathbf{v}_{M0-} , \mathbf{i}_{M0+} and \mathbf{i}_{M0-} are z -independent vectors depending on the boundary conditions at $z = 0$ and $z = \mathcal{L}$.

□ For a function $f(u)$ of the variable $u \in \mathbb{C}$ and a diagonal matrix $\text{diag}_n(a_1, \dots, a_n)$, we define $f(\text{diag}_n(a_1, \dots, a_n)) = \text{diag}_n(f(a_1), \dots, f(a_n))$. This was used in (26).

□ For any $\alpha \in \{1, \dots, n\}$, a modal current $i_{M\alpha}$ and a modal voltage $v_{M\alpha}$ may propagate with the propagation constant γ_α toward the far-end, or with the opposite propagation constant $-\gamma_\alpha$ toward the near-end.

□ The column vectors of \mathbf{S} (respectively, of \mathbf{T}) are defined as linearly independent eigenvectors of $\mathbf{Z}'\mathbf{Y}'$ (respectively, of $\mathbf{Y}'\mathbf{Z}'$). **Consequently, \mathbf{S} and \mathbf{T} are not uniquely defined by (23).**



5. The characteristic impedance matrix

□ For a wave traveling toward the far-end, the column vector of the modal voltages is $\mathbf{v}_{M+} = e^{-z\Gamma} \mathbf{v}_{M0+}$ and the column vector of the modal currents is $\mathbf{i}_{M+} = e^{-z\Gamma} \mathbf{i}_{M0+}$.

□ The modal characteristic impedance matrix \mathbf{Z}_{MC} is defined by

$$\mathbf{v}_{M+} = \mathbf{Z}_{MC} \mathbf{i}_{M+} \quad (27)$$

and given by

$$\mathbf{Z}_{MC} = \Gamma^{-1} \mathbf{S}^{-1} \mathbf{Z}' \mathbf{T} = \Gamma \mathbf{S}^{-1} \mathbf{Y}'^{-1} \mathbf{T} = \mathbf{S}^{-1} \mathbf{Y}'^{-1} \mathbf{T} \Gamma = \mathbf{S}^{-1} \mathbf{Z}' \mathbf{T} \Gamma^{-1} \quad (28)$$

□ For a wave traveling toward the near-end, the column vector of the modal voltages is $\mathbf{v}_{M-} = e^{z\Gamma} \mathbf{v}_{M0-}$ and the column vector of the modal currents is $\mathbf{i}_{M-} = e^{z\Gamma} \mathbf{i}_{M0-}$, so that

$$\mathbf{v}_{M-} = -\mathbf{Z}_{MC} \mathbf{i}_{M-} \quad (29)$$



❑ The modal characteristic impedance matrix depends on the choice of **S** and **T**.

❑ We can now define the characteristic impedance matrix \mathbf{Z}_C of the multiconductor transmission line, as:

$$\mathbf{Z}_C = \mathbf{S} \mathbf{Z}_{MC} \mathbf{T}^{-1} \quad (30)$$

❑ Using (28), we get

$$\mathbf{Z}_C = \mathbf{S} \Gamma^{-1} \mathbf{S}^{-1} \mathbf{Z}' = \mathbf{S} \Gamma \mathbf{S}^{-1} \mathbf{Y}'^{-1} = \mathbf{Y}'^{-1} \mathbf{T} \Gamma \mathbf{T}^{-1} = \mathbf{Z}' \mathbf{T} \Gamma^{-1} \mathbf{T}^{-1} \quad (31)$$

❑ For a wave traveling toward the far-end, the column vector of the natural voltages is $\mathbf{v}_+ = \mathbf{S} \mathbf{v}_{M+} = \mathbf{S} e^{-z\Gamma} \mathbf{v}_{M0+}$ and the column vector of the modal currents is $\mathbf{i}_+ = \mathbf{T} \mathbf{i}_{M+} = \mathbf{T} e^{-z\Gamma} \mathbf{i}_{M0+}$. We find:

$$\mathbf{v}_+ = \mathbf{Z}_C \mathbf{i}_+ \quad (32)$$



□ For a wave traveling toward the near-end, the column vector of the natural voltages is $\mathbf{v}_- = \mathbf{S} \mathbf{v}_{M-} = \mathbf{S} e^{z\Gamma} \mathbf{v}_{M0-}$ and the column vector of the modal currents is $\mathbf{i}_- = \mathbf{T} \mathbf{i}_{M-} = \mathbf{T} e^{z\Gamma} \mathbf{i}_{M0-}$. We find:

$$\mathbf{v}_- = -\mathbf{Z}_C \mathbf{i}_- \quad (33)$$

□ Since (32) or (33) hold for any value \mathbf{i}_+ , each can be used as a definition of \mathbf{Z}_C . Thus, **\mathbf{Z}_C is unique and does not depend on the choice of the matrices \mathbf{S} and \mathbf{T} .**

□ For a lossless MTL, real and frequency-independent \mathbf{T} and \mathbf{S} can be computed [4], and we have

$$\gamma_\alpha = \frac{j\omega}{c_\alpha} \quad (34)$$

where the positive real c_α is the propagation velocity of the mode α . Thus, \mathbf{Z}_C is real.

□ The minimum travel time is $\tau_{\min} = \frac{\mathcal{L}}{\max(c_\alpha)}$.

□ Special case of a lossless MTL where the electric field sees an homogeneous dielectric:

◆ we may consider that we have a lossless MTL having an homogeneous dielectric of permittivity ϵ_r , for which it can be shown that [1] [90],

$$\mathbf{C}' = \epsilon_r \epsilon_0 \mu_0 \mathbf{L}'^{-1} \quad (35)$$

so that

$$\mathbf{Z}' \mathbf{Y}' = \mathbf{Y}' \mathbf{Z}' = -\omega^2 \epsilon_r \epsilon_0 \mu_0 \mathbf{1}_n \quad (36)$$

◆ we can use $\mathbf{S} = \mathbf{T} = \mathbf{1}_n$ so that

$$\Gamma = \frac{j\omega}{c_0 / \sqrt{\epsilon_r}} \mathbf{1}_n \quad \mathbf{Z}_C = \frac{\mathbf{C}'^{-1}}{c_0 / \sqrt{\epsilon_r}} = \frac{c_0}{\sqrt{\epsilon_r}} \mathbf{L}' \quad (37)$$

There is only one propagation constant: we have a completely degenerate MTL.



6. Biorthonormal eigenvectors and associated eigenvectors

□ \mathbf{Z}' and \mathbf{Y}' being symmetric, if a diagonalization of the matrix $\mathbf{Y}'\mathbf{Z}'$ produces a matrix \mathbf{T} satisfying the first line of (23), i.e. $\mathbf{T}^{-1}\mathbf{Y}'\mathbf{Z}'\mathbf{T} = \Gamma^2$, we find that a solution of the second line of (23), i.e. $\mathbf{S}^{-1}\mathbf{Z}'\mathbf{Y}'\mathbf{S} = \Gamma^2$ is

$$\mathbf{S} = {}^t\mathbf{T}^{-1} \quad (38)$$

where ${}^t\mathbf{A}$ is used to denote the transpose of a matrix \mathbf{A} .

□ In other words, we can always compute the eigenvectors \mathbf{T}_i of $\mathbf{Y}'\mathbf{Z}'$ and the eigenvectors \mathbf{S}_j of $\mathbf{Z}'\mathbf{Y}'$ in such a way that they satisfy the relation

$${}^t\mathbf{S}_i \mathbf{T}_j = \delta_{ij} \quad (39)$$

where δ_{ij} is Kronecker's symbol. This is called the *biorthonormal property* [15].



□ The possibility of using (38) in (31) shows that \mathbf{Z}_C is symmetric.

□ Note that:

- ◆ biorthonormal eigenvectors can be used with lossy and lossless MTLs;
- ◆ (38) is not a property of (23), it is only a possible choice.

□ If a diagonalization of the matrix $\mathbf{Y}'\mathbf{Z}'$ produces a matrix \mathbf{T} satisfying the first line of (23), i.e. $\mathbf{T}^{-1}\mathbf{Y}'\mathbf{Z}'\mathbf{T} = \Gamma^2$, we find that a solution of the second line of (23), i.e. $\mathbf{S}^{-1}\mathbf{Z}'\mathbf{Y}'\mathbf{S} = \Gamma^2$ is

$$\mathbf{S} = j\omega c_K \mathbf{Y}'^{-1}\mathbf{T} \quad (40)$$

where c_K is an arbitrary scalar different from zero, which may depend on frequency, and which has the dimensions of p.u.l. capacitance.

□ When \mathbf{S} and \mathbf{T} are defined by (23) and (40), we say that they are *associated*, and that the eigenvectors contained in \mathbf{S} and \mathbf{T} (i.e. their column vectors) are associated [10] [12] [16] [22] [27] [38] [39].

□ Using (21) and (24), we can write

$$\left\{ \begin{array}{l} \frac{d \mathbf{v}_M}{dz} = -\mathbf{Z}'_M \mathbf{i}_M \\ \frac{d \mathbf{i}_M}{dz} = -\mathbf{Y}'_M \mathbf{v}_M \end{array} \right. \quad \text{where} \quad \left\{ \begin{array}{l} \mathbf{Z}'_M = \mathbf{S}^{-1} \mathbf{Z}' \mathbf{T} \\ \mathbf{Y}'_M = \mathbf{T}^{-1} \mathbf{Y}' \mathbf{S} \end{array} \right. \quad (41)$$

This defines the modal p.u.l. impedance matrix \mathbf{Z}'_M and the modal p.u.l. admittance matrix \mathbf{Y}'_M . For associated eigenvectors, we find

$$\mathbf{Z}'_M = (j\omega c_K \mathbf{Y}'^{-1} \mathbf{T})^{-1} \mathbf{Z}' \mathbf{T} = \frac{1}{j\omega c_K} \mathbf{T}^{-1} \mathbf{Y}' \mathbf{Z}' \mathbf{T} = \frac{\Gamma^2}{j\omega c_K} \quad (42)$$

and

$$\mathbf{Y}'_M = \mathbf{T}^{-1} \mathbf{Y}' (j\omega c_K \mathbf{Y}'^{-1} \mathbf{T}) = j\omega c_K \mathbf{1}_n \quad (43)$$

Thus, we have shown that, for associated eigenvectors:

- ◆ the modal p.u.l. impedance matrix $\mathbf{Z}'_M = \mathbf{S}^{-1} \mathbf{Z}' \mathbf{T}$ is diagonal; and
- ◆ the modal p.u.l. admittance matrix $\mathbf{Y}'_M = \mathbf{T}^{-1} \mathbf{Y}' \mathbf{S}$ is diagonal.



□ For associated eigenvectors, the modal characteristic impedance matrix is diagonal and given by

$$\mathbf{Z}_{MC} = \frac{1}{j\omega \mathbf{c}_K} \mathbf{\Gamma} \quad (44)$$

□ A more general possible choice (**generalized associated eigenvectors**) is given by

$$\mathbf{S} = j\omega \mathbf{Y}'^{-1} \mathbf{T} \mathbf{c}_K \quad (45)$$

where \mathbf{c}_K is an arbitrary invertible diagonal matrix, possibly frequency-dependent, and having the dimensions of p.u.l. capacitance.

□ We find that, for generalized associated eigenvectors:

- ◆ the modal p.u.l. impedance matrix $\mathbf{Z}'_M = \mathbf{S}^{-1} \mathbf{Z}' \mathbf{T}$ is diagonal;
- ◆ the modal p.u.l. admittance matrix $\mathbf{Y}'_M = \mathbf{T}^{-1} \mathbf{Y}' \mathbf{S}$ is diagonal;
- ◆ the modal characteristic impedance matrix is diagonal and its value is

$$\mathbf{Z}_{MC} = \frac{1}{j\omega} \mathbf{c}_K^{-1} \mathbf{\Gamma} \quad (46)$$

7. The choice of eigenvectors and total decoupling

□ For associated eigenvectors, for a wave propagating in a given direction and for any $\alpha \in \{1, \dots, n\}$, by (27), (29) and (44) we have:

$$v_{M\alpha} = \frac{\varepsilon_D}{j\omega c_K} \gamma_\alpha i_{M\alpha} \quad (47)$$

where ε_D is equal to 1 if the wave propagates toward the far-end, or to -1 if the wave propagates toward the near-end.

□ For generalized associated eigenvectors, using (27), (29) and (46), we find:

$$v_{M\alpha} = \frac{\varepsilon_D}{j\omega c_{K\alpha\alpha}} \gamma_\alpha i_{M\alpha} \quad (48)$$

where $c_{K\alpha\beta}$ denotes an entry of \mathbf{c}_K .



□ According to (26) and to (47) or (48), the propagation of $v_{M\alpha}$ and $i_{M\alpha}$ can be viewed as the propagation on a fictitious 2-conductor transmission line having the propagation constant γ_α and the characteristic impedance $\gamma_\alpha / j\omega c_K$ or $\gamma_\alpha / j\omega c_{K\alpha\alpha}$.

□ We say that a *total decoupling* occurs when a particular choice of \mathbf{T} and \mathbf{S} leads to (47) or (48) so that an equivalent circuit comprising n independent 2-conductor TLs may be defined for the $(n + 1)$ conductor MTL.

□ We see that the diagonalization of $\mathbf{Y}'\mathbf{Z}'$ and $\mathbf{Z}'\mathbf{Y}'$ in (23) provides a decoupling in (26), but it need not provide total decoupling.

□ **Theorem:** Total decoupling means that \mathbf{Z}_{MC} is diagonal. It only occurs for generalized associated eigenvectors, i.e. eigenvectors complying with (45).

Proof. The $c_{K\alpha\alpha}$ being arbitrary scalars, (48) means that \mathbf{Z}_{MC} is diagonal. By (28), we have $\mathbf{S} = \mathbf{Y}'^{-1}\mathbf{T}\Gamma\mathbf{Z}_{MC}^{-1}$ which complies with (45) for $j\omega\mathbf{c}_K = \Gamma\mathbf{Z}_{MC}^{-1}$. □



□ In the literature, we find that:

- ◆ \mathbf{T} and \mathbf{S} satisfy $\mathbf{S} = {}^t\mathbf{T}^{-1}$ [7] [14, § 4.3.2] [17, § 6.2.6] [81, § 4.4.1];
- ◆ the modes are orthogonal, i.e. the eigen-voltages (the columns of \mathbf{S}) or the eigen-currents (the columns of \mathbf{T}) are orthogonal [9] [13, col. 1] [19, col. 4] [33] [34] [81, § 4.4] [86] [88];
- ◆ the modal impedance matrix $\mathbf{Z}'_M = \mathbf{S}^{-1}\mathbf{Z}'\mathbf{T}$ and/or the modal admittance matrix $\mathbf{Y}'_M = \mathbf{T}^{-1}\mathbf{Y}'\mathbf{S}$ are diagonal [6] [7] [81, § 4.4.1];
- ◆ the 3 assertions above **need not be correct** [15] [38, § X] [39, § V and § VI].

□ Bi-orthonormal eigenvectors, defined by the relation $\mathbf{S} = {}^t\mathbf{T}^{-1}$ are such that total decoupling need not be present, so that it need not lead us to an equivalent circuit based on n uncoupled 2-conductor transmission lines.

□ However, when all γ_α are different from one another, i.e. when there is no degenerate propagation constants, any choice of \mathbf{T} and \mathbf{S} complies with (45), so that bi-orthonormal eigenvectors provide a total decoupling in this case.

□ However, in the case of a lossless MTL, it is possible to compute a matrix \mathbf{T} such that [4] [5] [14, § 4.4.3]

$$\mathbf{T}^{-1} = {}^t\mathbf{T} \mathbf{C}'^{-1} \quad (49)$$

for which bi-orthogonal eigenvectors comply with (45), so that they provide a total decoupling (at the cost of a complex algorithm).

□ Using (generalized) associated eigenvectors, because of total decoupling:

- ◆ any $(n + 1)$ -conductor MTL has an equivalent circuit comprising voltage-controlled voltage sources, current-controlled current sources and n uncoupled 2-conductor transmission lines;
- ◆ in general, all electrical parameters of the equivalent circuit are complex and frequency-dependent;
- ◆ if the MTL is lossless, all electrical parameters of the equivalent circuit are real and frequency-independent. It can be used in SPICE [10] [12] [16].



□ Example A: This example relates to a multiconductor microstrip interconnection having 8 TCs, built on a polyimide substrate. We neglect losses.

The worksheet of [Annex A](#) shows that, in this example:

- ◆ there are no degenerate eigenvalues (see § 2);
- ◆ \mathbf{Z}_C is real, not diagonal, and may be realized with a network of $n(n+1)/2$ resistors, some of which being obviously superfluous (see § 3 and § 4);
- ◆ the eigen-voltages and the eigen-currents are not orthogonal (see § 5);
- ◆ for associated eigenvectors, \mathbf{Z}'_M and \mathbf{Y}'_M are diagonal (see § 6);
- ◆ for our choice of bi-orthonormal eigenvectors, \mathbf{Z}_{MC} , \mathbf{Z}'_M and \mathbf{Y}'_M are diagonal (see § 7 and § 8).

✓ Why would the computation of \mathbf{T} in § 2 be inadequate for degenerate eigenvalues?
Answer: the function *eigenvect* cannot return independent eigenvectors for a degenerate eigenvalue.



□ Example B: This example relates to the multiconductor stripline interconnection having 8 TCs, built in a polyimide substrate. We neglect losses.

The worksheet of [Annex B](#) shows that, in this example:

- ◆ we assume an homogeneous dielectric, so that (35) is used to compute \mathbf{C}' and completely degenerate eigenvalues are obtained (see § 1 and § 2);
- ◆ \mathbf{Z}_C is real, not diagonal, and may be realized with a network of $n(n+1)/2$ resistors, many of which being obviously superfluous (see § 3 and § 4);
- ◆ for our choice of associated eigenvectors, the eigen-voltages are not orthogonal while the eigen-currents are orthogonal (see § 5);
- ◆ for associated eigenvectors, \mathbf{Z}'_M and \mathbf{Y}'_M are diagonal (see § 6);
- ◆ for our choice of bi-orthonormal eigenvectors, \mathbf{Z}_{MC} , \mathbf{Z}'_M and \mathbf{Y}'_M are not diagonal (see § 7 and § 8).

8. Propagation in the frequency domain

□ According to (26), \mathbf{v}_M and \mathbf{i}_M are given by

$$\begin{cases} \mathbf{v}_M = \mathbf{v}_{M+} + \mathbf{v}_{M-} \\ \mathbf{i}_M = \mathbf{i}_{M+} + \mathbf{i}_{M-} \end{cases} \quad (50)$$

where

$$\begin{cases} \mathbf{v}_{M+} = e^{-z\Gamma} \mathbf{v}_{M0+} \\ \mathbf{i}_{M+} = e^{-z\Gamma} \mathbf{i}_{M0+} \end{cases} \quad \text{and} \quad \begin{cases} \mathbf{v}_{M-} = e^{z\Gamma} \mathbf{v}_{M0-} \\ \mathbf{i}_{M-} = e^{z\Gamma} \mathbf{i}_{M0-} \end{cases} \quad (51)$$

where

- ◆ \mathbf{v}_{M+} is the column vector of the modal voltages traveling toward the far-end,
- ◆ \mathbf{v}_{M-} is the column vector of the modal voltages traveling toward the near-end,
- ◆ \mathbf{i}_{M+} is the column vector of the modal currents traveling toward the far-end,
- ◆ \mathbf{i}_{M-} is the column vector of the modal currents traveling toward the near-end,
- ◆ \mathbf{v}_{M0+} , \mathbf{v}_{M0-} , \mathbf{i}_{M0+} and \mathbf{i}_{M0-} are z -independent column vectors depending on the boundary conditions at $z = 0$ and $z = \mathcal{L}$.

□ Thus, a *modal scattering matrix*, denoted by $\mathcal{S}_M(z)$ and defined by

$$\begin{pmatrix} \mathbf{v}_{M-}(0) \\ \mathbf{v}_{M+}(z) \end{pmatrix} = \mathcal{S}_M(z) \begin{pmatrix} \mathbf{v}_{M+}(0) \\ \mathbf{v}_{M-}(z) \end{pmatrix} \quad (52)$$

is given by

$$\mathcal{S}_M(z) = \begin{pmatrix} 0 & e^{-z\Gamma} \\ e^{-z\Gamma} & 0 \end{pmatrix} \quad (53)$$

□ This result is similar to (11), which applies to a TL.

□ By (27) and (29), we have

$$\mathbf{v}_{M+} = \frac{\mathbf{v}_M + \mathbf{Z}_{MC} \mathbf{i}_M}{2} \quad \mathbf{v}_{M-} = \frac{\mathbf{v}_M - \mathbf{Z}_{MC} \mathbf{i}_M}{2} \quad (54)$$

□ Using (50), (51), $\mathbf{v} = \mathbf{S} \mathbf{v}_M$ and $\mathbf{i} = \mathbf{T} \mathbf{i}_M$, we find that \mathbf{v} and \mathbf{i} are given by

$$\begin{cases} \mathbf{v} = \mathbf{v}_+ + \mathbf{v}_- \\ \mathbf{i} = \mathbf{i}_+ + \mathbf{i}_- \end{cases} \quad (55)$$

where

$$\begin{cases} \mathbf{v}_+ = \mathbf{S} e^{-z\Gamma} \mathbf{S}^{-1} \mathbf{v}_{0+} \\ \mathbf{i}_+ = \mathbf{T} e^{-z\Gamma} \mathbf{T}^{-1} \mathbf{i}_{0+} \end{cases} \quad \text{and} \quad \begin{cases} \mathbf{v}_- = \mathbf{S} e^{z\Gamma} \mathbf{S}^{-1} \mathbf{v}_{0-} \\ \mathbf{i}_- = \mathbf{T} e^{z\Gamma} \mathbf{T}^{-1} \mathbf{i}_{0-} \end{cases} \quad (56)$$

where

- ◆ \mathbf{v}_+ is the column vector of the natural voltages traveling toward the far-end,
- ◆ \mathbf{v}_- is the column vector of the natural voltages traveling toward the near-end,
- ◆ \mathbf{i}_+ is the column vector of the natural currents traveling toward the far-end,
- ◆ \mathbf{i}_- is the column vector of the natural currents traveling toward the near-end,
- ◆ \mathbf{v}_{0+} , \mathbf{v}_{0-} , \mathbf{i}_{0+} and \mathbf{i}_{0-} are z -independent column vectors depending on the boundary conditions at $z = 0$ and $z = \mathcal{L}$.

□ \mathbf{v}_+ , \mathbf{v}_- , \mathbf{i}_+ and \mathbf{i}_- are independent of the choice of eigenvectors.

□ Thus, a *scattering matrix*, denoted by $\mathcal{S}(z)$ and defined by

$$\begin{pmatrix} \mathbf{v}_-(0) \\ \mathbf{v}_+(z) \end{pmatrix} = \mathcal{S}(z) \begin{pmatrix} \mathbf{v}_+(0) \\ \mathbf{v}_-(z) \end{pmatrix} \quad (57)$$

is given by

$$\mathcal{S}(z) = \begin{pmatrix} 0 & \mathbf{S}e^{-z\Gamma}\mathbf{S}^{-1} \\ \mathbf{S}e^{-z\Gamma}\mathbf{S}^{-1} & 0 \end{pmatrix} = \begin{pmatrix} 0 & e^{-z\sqrt{\mathbf{Z}'\mathbf{Y}'}} \\ e^{-z\sqrt{\mathbf{Z}'\mathbf{Y}'}} & 0 \end{pmatrix} \quad (58)$$

□ By (32) and (33), we have


$$\mathbf{v}_+ = \frac{\mathbf{v} + \mathbf{Z}_C \mathbf{i}}{2} \quad \mathbf{v}_- = \frac{\mathbf{v} - \mathbf{Z}_C \mathbf{i}}{2} \quad (59)$$

□ $\mathcal{S}(\mathcal{L})$ is the usual scattering matrix of a $2n$ -port only when \mathbf{Z}_C is real and diagonal.

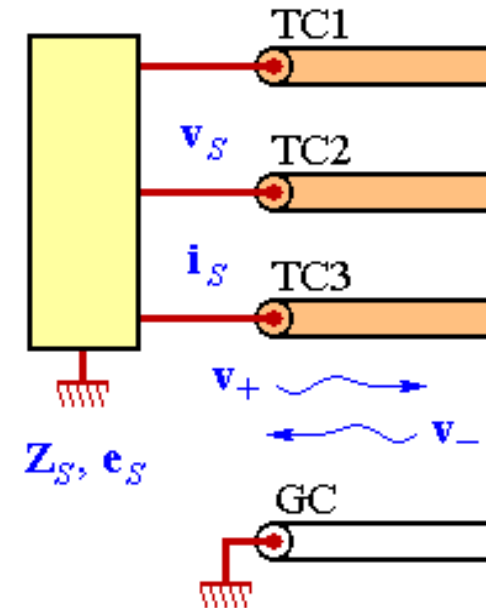9. Matched termination circuit and pseudo-matched terminations


□ We consider, at the near-end, a passive linear $(n + 1)$ -terminal circuit of impedance matrix \mathbf{Z}_S and open-circuit voltage \mathbf{e}_S . We find:

$$\begin{aligned} \mathbf{v}_+ &= \mathbf{Z}_C (\mathbf{Z}_S + \mathbf{Z}_C)^{-1} \mathbf{e}_S + \mathbf{P}_S \mathbf{v}_- \\ &= \frac{\mathbf{1}_n - \mathbf{P}_S}{2} \mathbf{e}_S + \mathbf{P}_S \mathbf{v}_- \end{aligned} \quad (60)$$



where $\mathbf{1}_n$ is the identity matrix of size $n \times n$ and where \mathbf{P}_S is the matrix of the voltage reflection coefficients for this configuration, given by
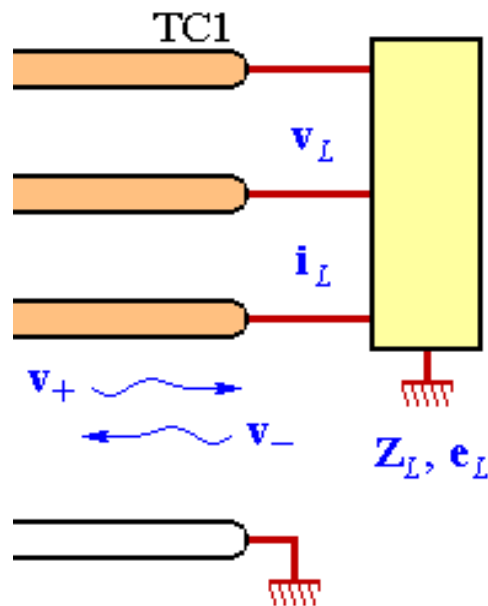
$$\mathbf{P}_S = \mathbf{Z}_C (\mathbf{Z}_S + \mathbf{Z}_C)^{-1} (\mathbf{Z}_S - \mathbf{Z}_C) \mathbf{Z}_C^{-1} = (\mathbf{Z}_S - \mathbf{Z}_C) (\mathbf{Z}_S + \mathbf{Z}_C)^{-1} \quad (61)$$



□ For the corresponding case at the far-end, we find:

$$\begin{aligned} \mathbf{v}_- &= \mathbf{Z}_C (\mathbf{Z}_L + \mathbf{Z}_C)^{-1} \mathbf{e}_L + \mathbf{P}_L \mathbf{v}_+ \\ &= \frac{\mathbf{1}_n - \mathbf{P}_L}{2} \mathbf{e}_L + \mathbf{P}_L \mathbf{v}_+ \end{aligned} \quad (62)$$

where \mathbf{P}_L is the matrix of the voltage reflection coefficients for this configuration, given by

$$\mathbf{P}_L = \mathbf{Z}_C (\mathbf{Z}_L + \mathbf{Z}_C)^{-1} (\mathbf{Z}_L - \mathbf{Z}_C) \mathbf{Z}_C^{-1} = (\mathbf{Z}_L - \mathbf{Z}_C) (\mathbf{Z}_L + \mathbf{Z}_C)^{-1} \quad (63)$$

□ **A matched termination circuit produces no reflection:**

- ◆ at the far-end, if $\mathbf{Z}_L = \mathbf{Z}_C$ or equivalently $\mathbf{P}_L = \mathbf{0}_{nn}$;
- ◆ at the near-end, if $\mathbf{Z}_S = \mathbf{Z}_C$ or equivalently $\mathbf{P}_S = \mathbf{0}_{nn}$.

□ Note that we are again referring to reflectionless matching, as opposed to hermitian matching which provides maximum power transfer [3].



- ❑ For an interconnection in which TC-to-TC coupling is not negligible, a matched termination circuit has a non-diagonal impedance matrix (with respect to the GC).
- ❑ A termination circuit made of n impedors each connected between a TC and the GC has a diagonal impedance matrix (with respect to the GC). **The impedance of an impedor intended to minimize the detrimental effects of reflections is referred to as pseudo-matched-impedance** [36] [38] [39].
- ❑ Pseudo-matched impedances may be chosen as the diagonal elements of \mathbf{Z}_C [10] [12]. This is an arbitrary definition.
- ❑ A second choice of pseudo-matched impedances requires that the diagonal elements of \mathbf{P}_L or \mathbf{P}_S are equal to zero. This is referred to as *diagonal matching* [20].
- ❑ In diagonal matching, if the incident wave exists on a single TC, there is no reflected wave on this TC. Consequently, the termination circuit produces crosstalk, but no echo (however, it may indirectly contribute to echo).

□ A third choice of pseudo-matched impedances requires that the maximum (absolute) column sum norm $|||\mathbf{P}|||_1$ of $\mathbf{P} = \mathbf{P}_S$ or $\mathbf{P} = \mathbf{P}_L$ be minimized. If $\mathbf{P} = [\rho_{\alpha\beta}]$, this matrix norm [8, § 5.6.4] [21, p. 1148] is defined by

$$|||\mathbf{P}|||_1 = \max_j \sum_{i=1}^n |\rho_{ij}| \quad (64)$$

□ $|||\bullet|||_1$ is the matrix norm induced by the L_1 -norm for vectors, defined by

$$\|\mathbf{v}\|_1 = \sum_{i=1}^n |v_i| \quad (65)$$

Thus, for a non-zero incident wave \mathbf{v}

$$\frac{\|\mathbf{P}\mathbf{v}\|_1}{\|\mathbf{v}\|_1} \leq \max_{\mathbf{x} \neq \mathbf{0}} \frac{\|\mathbf{P}\mathbf{x}\|_1}{\|\mathbf{x}\|_1} = |||\mathbf{P}|||_1 \quad (66)$$

□ A fourth choice of pseudo-matched impedances requires that the maximum (absolute) row sum norm $|||\mathbf{P}|||_{\infty}$ of $\mathbf{P} = \mathbf{P}_S$ or $\mathbf{P} = \mathbf{P}_L$ be minimized. If $\mathbf{P} = [\rho_{\alpha\beta}]$, this matrix norm is defined by

$$|||\mathbf{P}|||_{\infty} = \max_i \sum_{j=1}^n |\rho_{ij}| \quad (67)$$

□ $|||\bullet|||_{\infty}$ is the matrix norm induced by the L_{∞} -norm for vectors, defined by

$$\|\mathbf{v}\|_{\infty} = \max_i |v_i| \quad (68)$$


Thus, for a non-zero incident wave \mathbf{v}

$$\frac{\|\mathbf{P}\mathbf{v}\|_{\infty}}{\|\mathbf{v}\|_{\infty}} \leq \max_{\mathbf{x} \neq \mathbf{0}} \frac{\|\mathbf{P}\mathbf{x}\|_{\infty}}{\|\mathbf{x}\|_{\infty}} = |||\mathbf{P}|||_{\infty} \quad (69)$$

□ In the special case where losses are neglected, \mathbf{Z}_C is real and frequency-independent, so that the proposed pseudo-matched impedances are resistances.

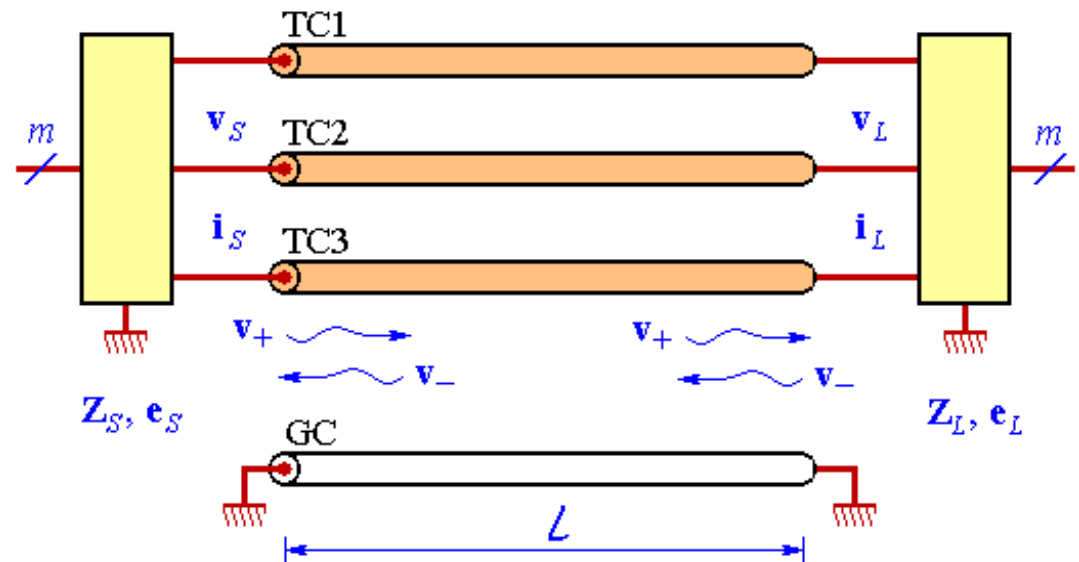10. Problems involving an MTL and linear terminations

In this configuration, \mathbf{e}_S and \mathbf{e}_L are the vectors of the open-circuit voltages at the near-end and at the far-end, respectively.



- Three possible approaches to find \mathbf{v}_S and \mathbf{v}_L in the configuration shown above:
 - ◆ using the boundary conditions to obtain \mathbf{v}_{M0+} , \mathbf{v}_{M0-} , \mathbf{i}_{M0+} and \mathbf{i}_{M0-} in (24) and (26);
 - ◆ using the scattering matrix defined by (58) and the reflection coefficients;
 - ◆ using the chain matrix (not studied in this tutorial).

□ Following the second approach, we consider multiple reflections occurring at the ends and multiple propagation through the MTL. For case $\mathbf{e}_S \neq \mathbf{0}$ and $\mathbf{e}_L = \mathbf{0}$, we get:

$$\begin{cases} \mathbf{v}_+(0) = \left\{ \sum_{p=0}^{\infty} \left(\mathbf{P}_S e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \mathbf{P}_L e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \right)^p \right\} \mathbf{Z}_C (\mathbf{Z}_S + \mathbf{Z}_C)^{-1} \mathbf{e}_S \\ \mathbf{v}_+(L) = e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \left\{ \sum_{p=0}^{\infty} \left(\mathbf{P}_S e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \mathbf{P}_L e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \right)^p \right\} \mathbf{Z}_C (\mathbf{Z}_S + \mathbf{Z}_C)^{-1} \mathbf{e}_S \end{cases} \quad (70)$$


and

$$\begin{cases} \mathbf{v}_S = \left[\mathbf{1}_n + e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \mathbf{P}_L e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \right] \mathbf{v}_+(0) \\ \mathbf{v}_L = [\mathbf{1}_n + \mathbf{P}_L] \mathbf{v}_+(L) \end{cases} \quad (71)$$


Using [8, § 5.6.16], we obtain

$$\begin{cases} \mathbf{v}_S = \left(\mathbf{1}_n + e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \mathbf{P}_L e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \right) \left(\mathbf{1}_n - \mathbf{P}_S e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \mathbf{P}_L e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \right)^{-1} \mathbf{Z}_C (\mathbf{Z}_S + \mathbf{Z}_C)^{-1} \mathbf{e}_S \\ \mathbf{v}_L = (\mathbf{1}_n + \mathbf{P}_L) e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \left(\mathbf{1}_n - \mathbf{P}_S e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \mathbf{P}_L e^{-L\sqrt{\mathbf{Z}'\mathbf{Y}'}} \right)^{-1} \mathbf{Z}_C (\mathbf{Z}_S + \mathbf{Z}_C)^{-1} \mathbf{e}_S \end{cases} \quad (72)$$

□ Example: a 300-mm long multiconductor microstrip built on a general-purpose FR-4 material, having 4 TCs, used for single-ended transmission with pseudo-matched terminations such that $||\mathbf{P}_S|||_\infty = ||\mathbf{P}_L|||_\infty \approx 0.130$ and $||\mathbf{P}_S|||_1 = ||\mathbf{P}_L|||_1 \approx 0.138$.

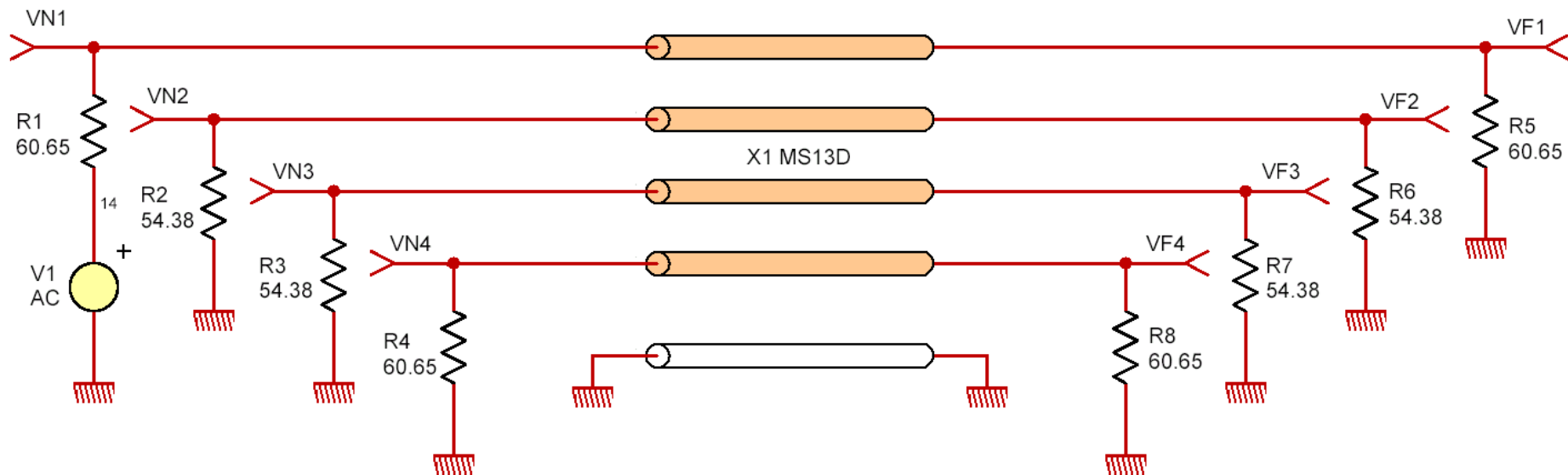


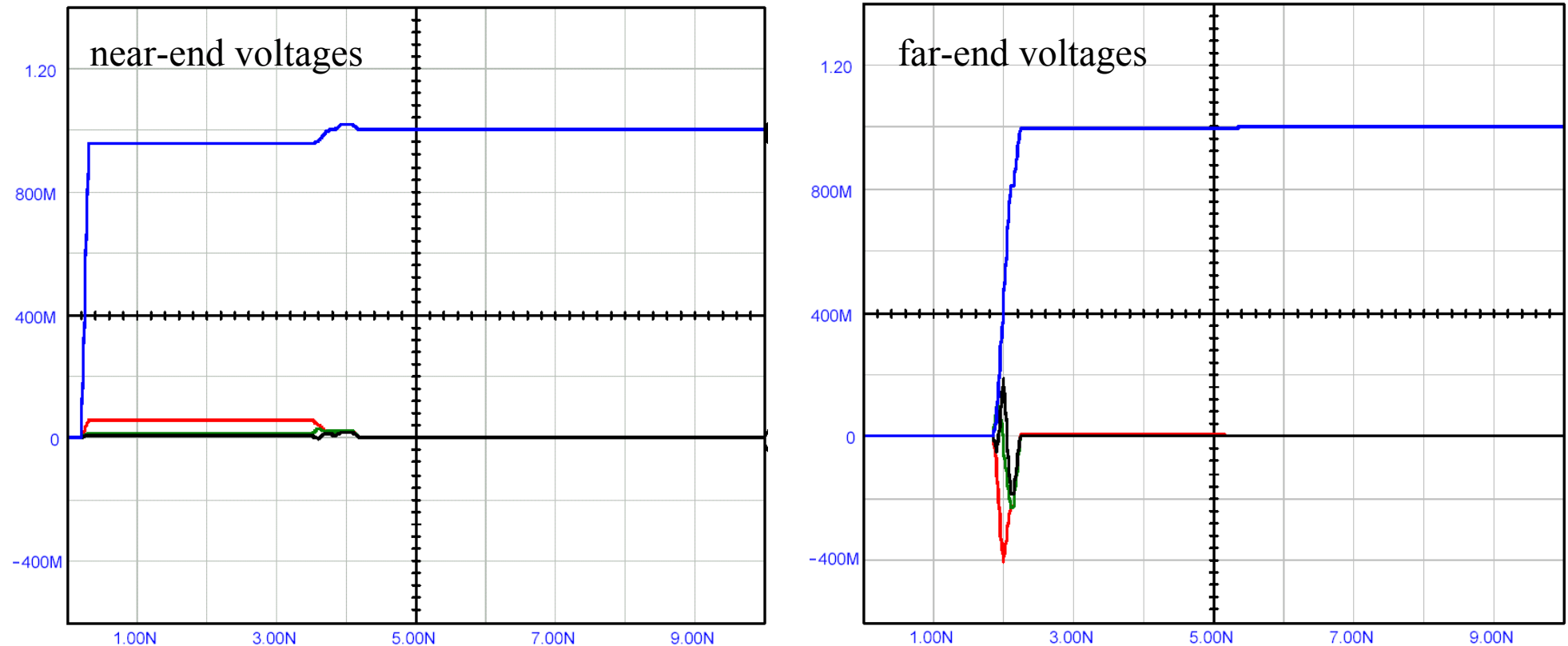Simulation using a circuit simulation program (based on Berkeley SPICE 3F.2) and a lossless MTL model generated by SpiceLine [10] [12] [16] [22].




Voltages in mV versus time in ns. TC1: blue curves. TC2: red curves. TC3: green curves. TC4: black curves.

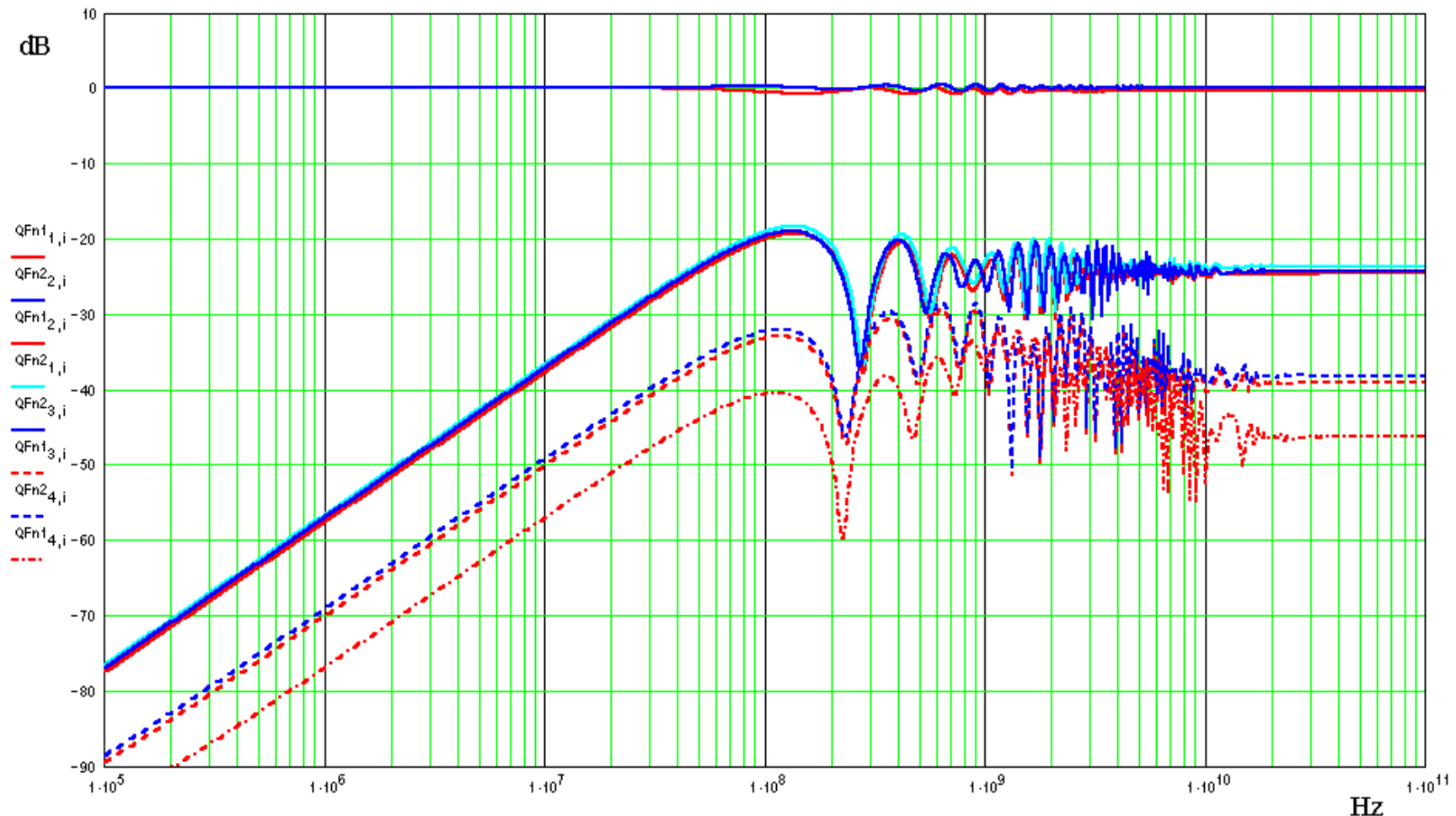
In the frequency domain, some near-end voltages obtained with a standard numerical computation program, resistive and dielectric losses being taken into account



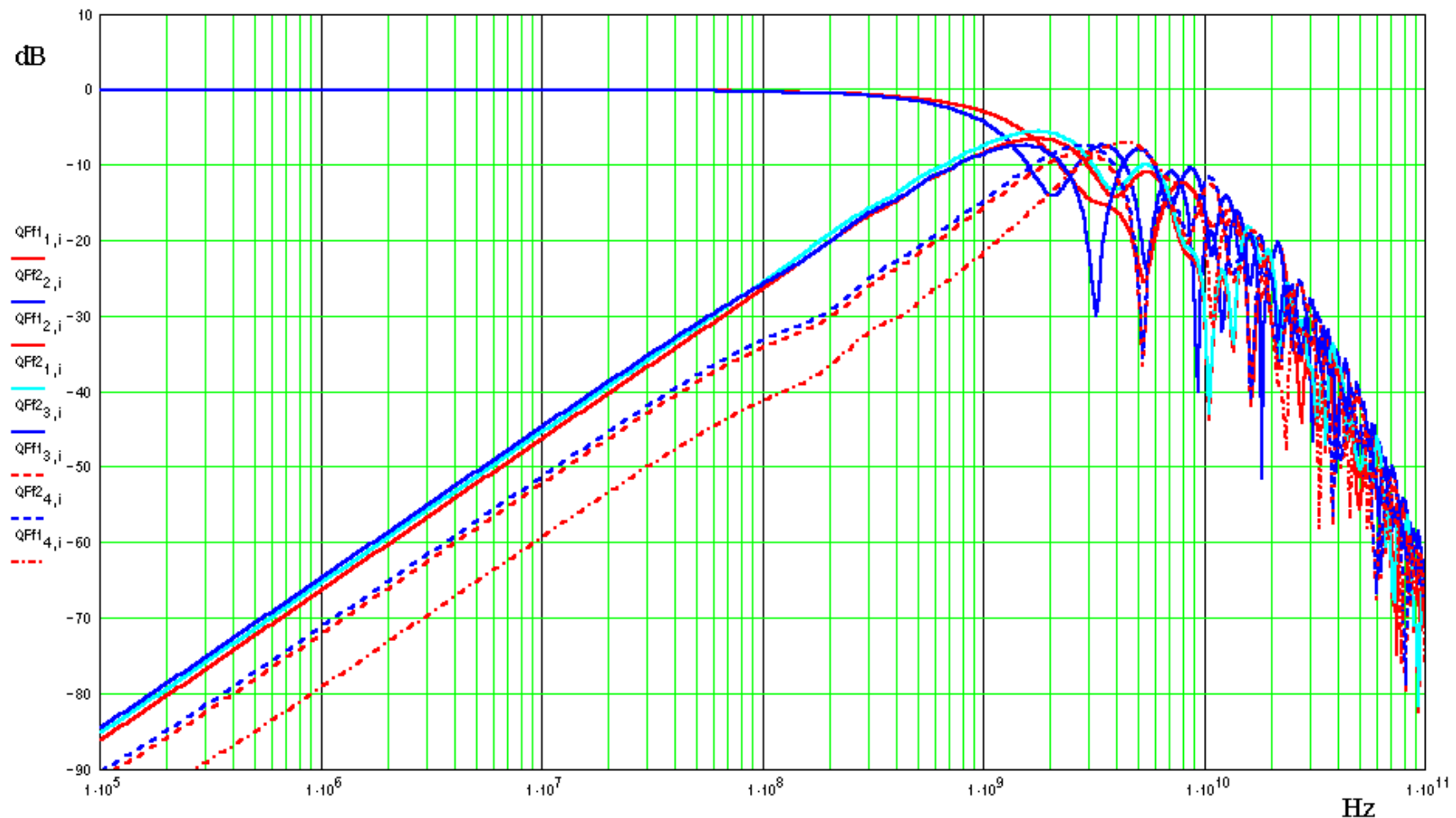
Some voltages at the far-end, computed with the same tool, resistive and dielectric losses being taken into account.



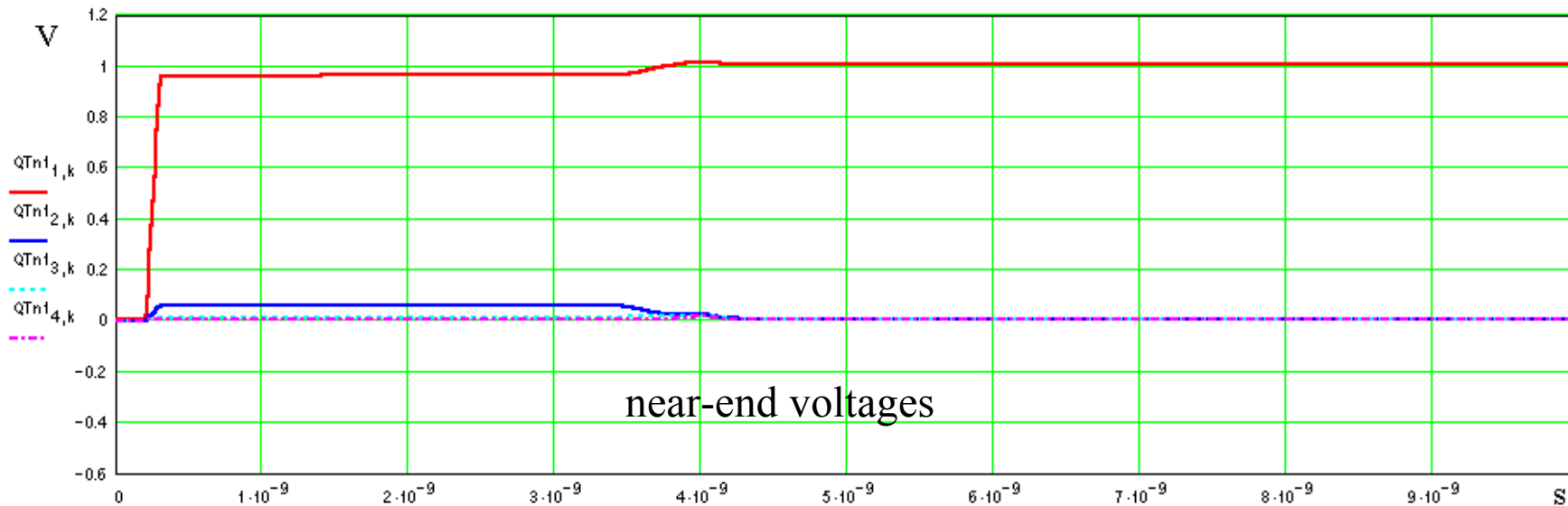Time domain results using the same tool,
resistive and dielectric losses being taken into account.



near-end voltages

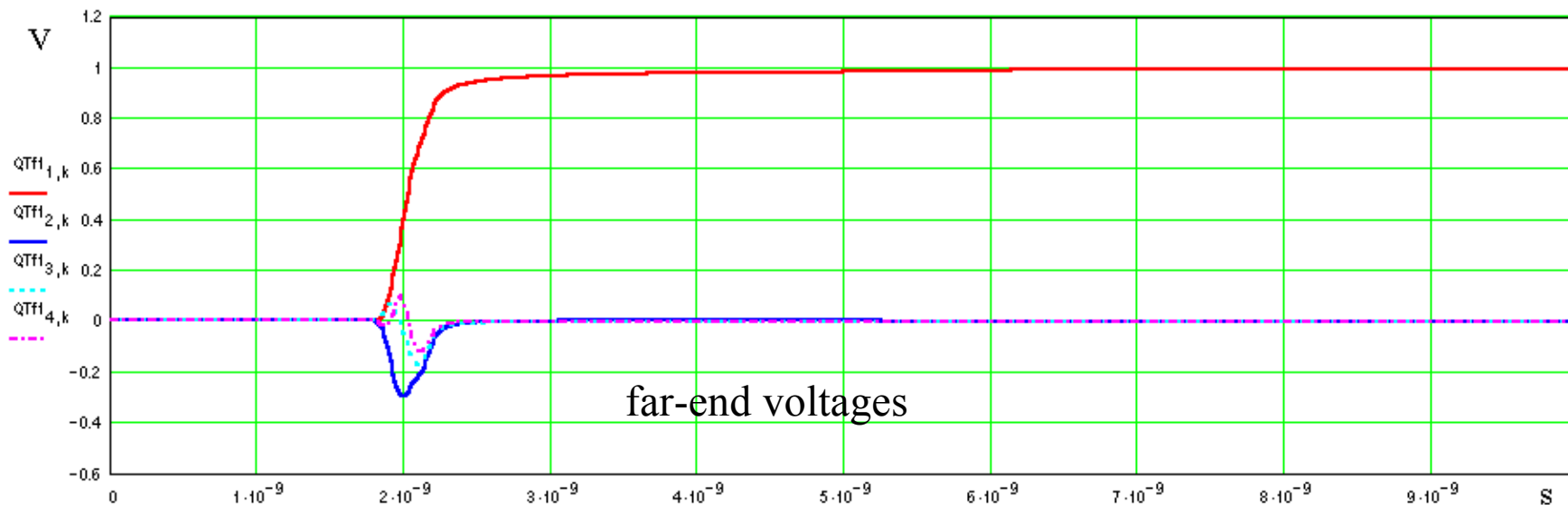

far-end voltages



11. The degradation of transmitted signals

□ The degradation of signals transmitted through a linear multichannel link is the result of five phenomena related to the properties of the interconnection:


- ◆ *attenuation* of the wanted signal;
- ◆ *echo*, the detrimental phenomenon by which a signal sent or received at an end of the link, in one of the channels, is followed by the reception of a delayed noise on the same channel, at the same end of the link;
- ◆ *internal crosstalk*, the detrimental phenomenon by which a signal sent in one of the channels produces noise in another channel;
- ◆ *other linear distortions*, of the wanted signal, which may be due to the variation of the propagation velocity with frequency (dispersion) or other causes;
- ◆ *thermal noise*.

□ We have not included the *propagation delay* in this list, but this phenomenon might also be a problem.



- ❑ In the case of a signal applied at the near-end,
 - ◆ *near-end crosstalk* (NEXT) is the internal crosstalk occurring at the near-end;
 - ◆ *far-end crosstalk* (FEXT) is the internal crosstalk occurring at the far-end.
- ❑ *Reflection* is the phenomenon by which a wave propagating in a given direction, involving one or more TCs, produces a wave propagating in the opposite direction.
- ❑ Reflections may be responsible for echo and/or internal crosstalk.
- ❑ If the interconnection is uniform, reflection can only be caused by the items connected at its ends.
- ❑ *TC-to-TC coupling* collectively designates p.u.l. mutual capacitance between the TCs and p.u.l. mutual impedance between loops comprising the TCs and the GC.
- ❑ TC-to-TC coupling may be responsible for internal crosstalk.

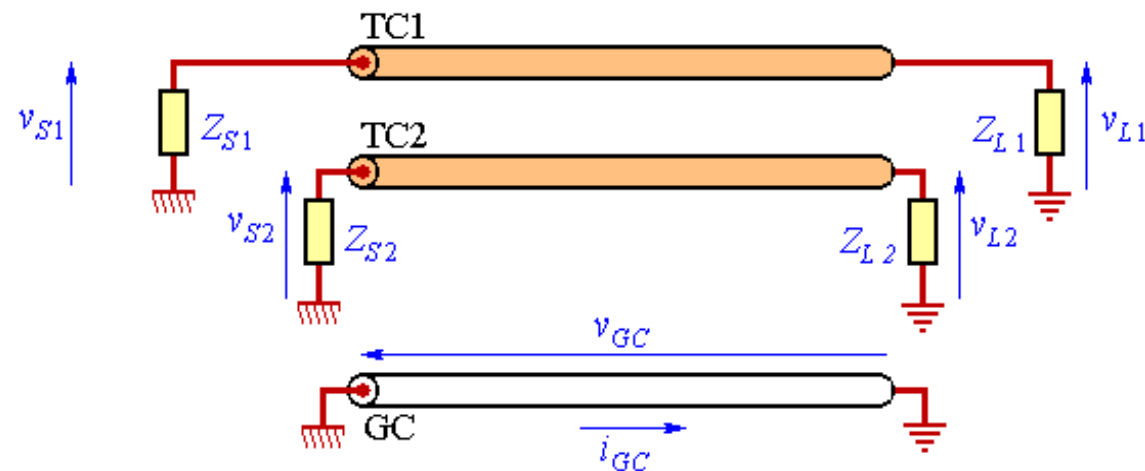- ❑ Detrimental interactions between the link and other circuits of the chip, MCM, SiP or PCB in which the link is built are referred to as *external crosstalk*.
- ❑ External crosstalk is often associated with a current i_{GC} flowing in the GC because of such other circuit, causing a voltage drop v_{GC} along the GC, often referred to as *ground shift* or *noisy ground*.



- ❑ This concept is valid at dc and very low frequencies, but **it is not compatible with the MTL model**.

- This is not a deficiency of the MTL model:
 - ◆ at high frequencies, the voltages between the conductors are defined unambiguously only in a cross-section of the interconnection;
 - ◆ a TC must be added to allow i_{GC} to flow, and included in the MTL model.

- Possible causes of external crosstalk degrading transmission in a given link:
 - ◆ a conductor parallel to the interconnection, excited at the near-end;
 - ◆ a conductor parallel to the interconnection, excited at the far-end;
 - ◆ a conductor crossing the interconnection (below or above the TCs);
 - ◆ common-mode coupling at the near-end (sending end);
 - ◆ common-mode coupling at the far-end (receiving end).

- The mitigation techniques for internal crosstalk apply to the first two cases.



- ❑ Crossing at a right angle produces a local coupling, which can often be modeled with a circuit model only comprising stray capacitances.
- ❑ Common-mode coupling at the near-end or at the far-end typically happens in the line drivers or line receivers of an IC, because of currents produced by other circuits of the IC, flowing in a common impedance across which unwanted voltages referred to as *bounces* appear (e.g. the so-called *ground bounce* and *power bounce*).
- ❑ The common impedance is often caused by mutual inductance in the reference or power supply conductors within the IC package, or the corresponding leads.
- ❑ The currents having the worst effects are often caused by multiple switching in the IC, producing the so-called *simultaneous switching output* (SSO) noise.
- ❑ Once the common impedance has been reduced to the smaller practical value, a crosstalk cancellation scheme must be used to reduce external noise in the channel.

12. Single-ended parallel links

- ❑ *Single-ended transmission*: any transmission scheme in which a single TC is allocated to each channel, and in which a global net such as GND or VCC, referred to as the GC, is used as a voltage reference for receiving signals.
- ❑ A *single-ended link* uses single-ended transmission. It must be such that
 - ◆ TC-to-TC coupling is small;
 - ◆ the near-end interface and termination device (NIT) and the far-end interface and termination device (FIT) do not introduce any significant couplings between the voltages and currents in the TCs.
- ❑ Thus, for small signals, in any state, the impedance matrices of the NIT and FIT with respect to ground may be regarded as diagonal (or almost diagonal) matrices.



- ❑ A single-ended link may use:
 - ◆ voltage-mode signaling (low impedance NIT, high impedance FIT);
 - ◆ current-mode signaling (high impedance NIT, low impedance FIT);
 - ◆ pseudo-matched impedances at the NIT and/or at the FIT.

- ❑ Voltage-mode and current mode circuits can be used in the line drivers and line receivers of different types of single-ended links. For instance:
 - ◆ a voltage-mode line driver fitted with a series resistor (series termination) can provide a suitable pseudo-matched impedance;
 - ◆ a current-mode line driver or a voltage-mode line receiver fitted with a parallel termination can provide a suitable pseudo-matched impedance.


- ❑ A single-ended link can be point-to-point or multidrop.



- ❑ Each TC of a single-ended point-to-point link can be used for unidirectional (simplex) transmission, alternate bidirectional (half duplex) transmission or simultaneous bidirectional (full duplex) transmission.
- ❑ Each TC of a single-ended multidrop link can be used for unidirectional transmission or as a bus.
- ❑ The interconnection model underlying the concept of single-ended links excludes TC-to-TC coupling. Thus, possible models for preliminary link design are:
 - ◆ one ideal node for each TC, in the case of a short interconnection;
 - ◆ a lumped elements model for each TC, for longer but electrically short interconnections;
 - ◆ a TL model for each TC;
 - ◆ a uniform TL model for each TC if the interconnection is uniform.



- ❑ Since the underlying interconnection model does not include TC-to-TC coupling, actual non-zero TC-to-TC coupling is likely to produce crosstalk.
- ❑ In the case $n \geq 2$, it is advisable to take TC-to-TC coupling into account at the analysis stage. It is possible to use:
 - ◆ a lumped element model for an electrically short interconnection;
 - ◆ the weak coupling approximation applied to a lossless MTL model;
 - ◆ an exact solution of a lossless MTL model;
 - ◆ an exact solution of a MTL model taking losses into account.
- ❑ The weak coupling approximation provides closed-form solutions which reveal the underlying physics and can be used for comparing design options.
- ❑ We can use a first order perturbation theory where the undisturbed solution corresponds to uncoupled TLs.

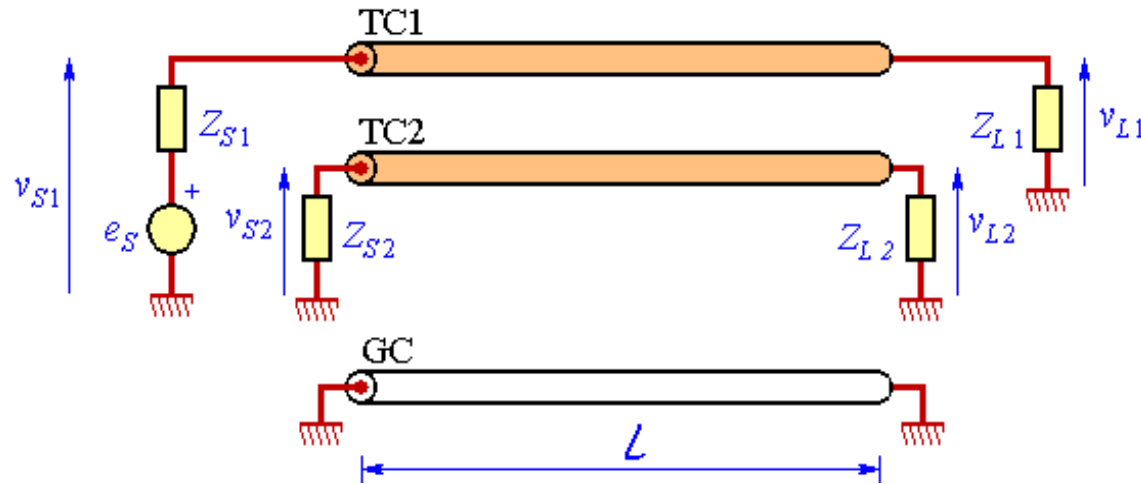

□ For the single-ended link shown, let us assume a uniform and lossless interconnection such that

$$\mathbf{Z}' = j\omega \begin{pmatrix} L'_{11} & L'_{12} \\ L'_{12} & L'_{22} \end{pmatrix} \quad \text{and} \quad \mathbf{Y}' = j\omega \begin{pmatrix} C'_{11} & C'_{12} \\ C'_{12} & C'_{22} \end{pmatrix} \quad (73)$$

□ Let us define

$$Z_{01} = \sqrt{\frac{L'_{11}}{C'_{11}}} \quad , \quad Z_{02} = \sqrt{\frac{L'_{22}}{C'_{22}}} \quad , \quad c_1 = \frac{1}{\sqrt{L'_{11}C'_{11}}} \quad \text{and} \quad c_2 = \frac{1}{\sqrt{L'_{22}C'_{22}}} \quad (74)$$

which would be characteristic impedances and propagation velocities if coupling was not present.

□ Let us define the capacitive coupling coefficient ξ_2 and the relative magnetic coupling coefficient Ξ_2 as:

$$\xi_2 = -\frac{C'_{12}}{C'_{22}} \quad \text{and} \quad \Xi_2 = -\frac{L'_{12}C'_{11}}{L'_{22}C'_{12}} \quad (75)$$

□ For $Z_{S1} = Z_{L1} = Z_{01}$, $Z_{S2} = Z_{L2} = Z_{02}$ and $c_1 = c_2 = c$, we get the result of Jarvis [2]:

$$v_{S2} = \frac{e_s \xi_2}{8} (\Xi_2 + 1) \left(1 - e^{-2j\frac{\omega}{c}L} \right) \quad (76)$$

$$v_{L2} = -j\frac{\omega}{c} \frac{e_s \xi_2}{4} (\Xi_2 - 1) L e^{-j\frac{\omega}{c}L} \quad (77)$$

□ We can check that the maximum value of $|v_{S2}/v_{L1}|$ is $\frac{\xi_2}{2} (\Xi_2 + 1)$, first achieved at $\omega = \frac{\pi c}{2L}$. This maximum is independent of L .



□ In the time domain, in the same case, the Jarvis formulas are:

$$v_{S2}(t) = \frac{\xi_2}{8} (\Xi_2 + 1) \left(e_S(t) - e_S\left(t - \frac{2\mathcal{L}}{c}\right) \right) \quad (78)$$

and


$$v_{L2}(t) = -\frac{\xi_2}{4c} (\Xi_2 - 1) \mathcal{L} \frac{de_S}{dt} \left(t - \frac{\mathcal{L}}{c} \right) \quad (79)$$

□ This approximation predicts that:


- ◆ $v_{S2}(t)$ is proportional to $e_S(t) - e_S(t - 2\mathcal{L}/c)$ and otherwise independent of \mathcal{L} ;
- ◆ the form of (76) or (78) shows that a reflection takes place at the far end;
- ◆ $v_{L2}(t)$ is proportional to \mathcal{L} and to the time derivative of $e_S(t - \mathcal{L}/c)$;
- ◆ $v_{L2}(t)$ vanishes for $\Xi_2 = 1$;
- ◆ thus, for $\Xi_2 = 1$, we have a *directional coupling*.

□ In a multiconductor stripline structure, we have $\Xi_2 = 1$. In a multiconductor microstrip structure, we have $\Xi_2 > 1$.

- ❑ Z_{01} and Z_{02} are not characteristic impedances but pseudo-matched impedances.
- ❑ An example of NEXT loss $|v_{L1}/v_{S2}|$ and FEXT loss $|v_{L1}/v_{L2}|$ in a 300-mm long multiconductor microstrip built on FR-4, having 2 TCs, according to the weak coupling approximation.

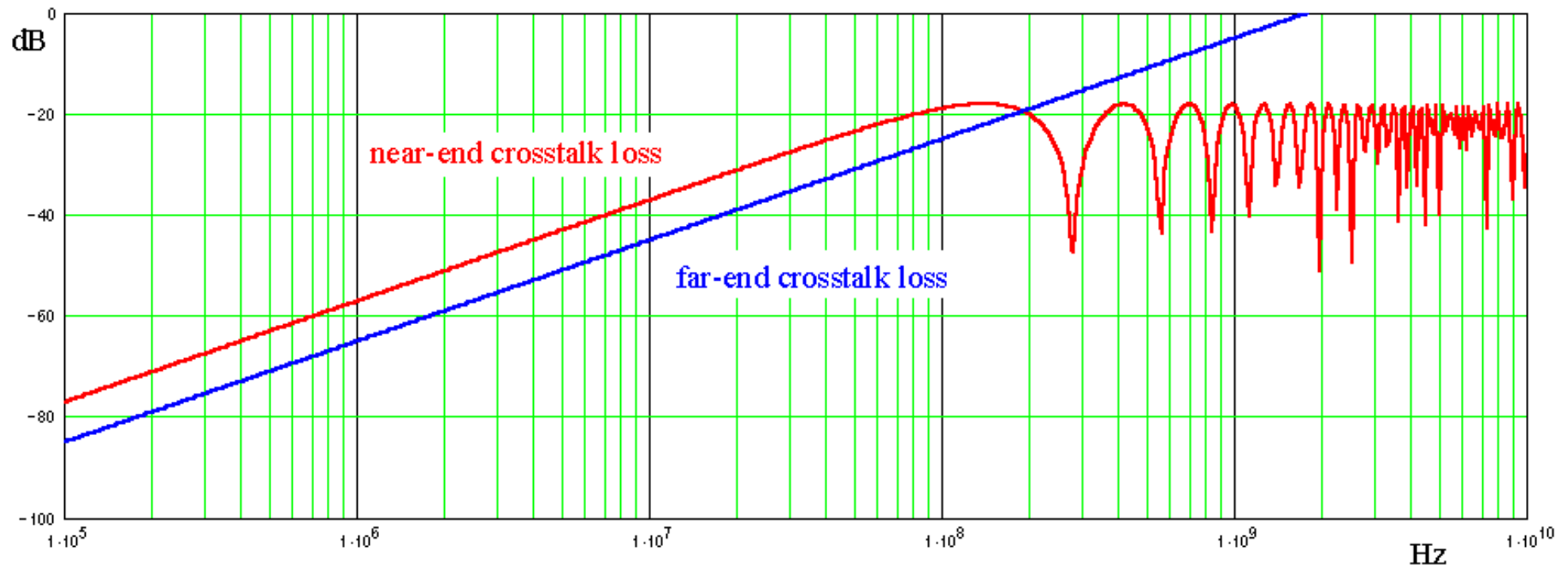

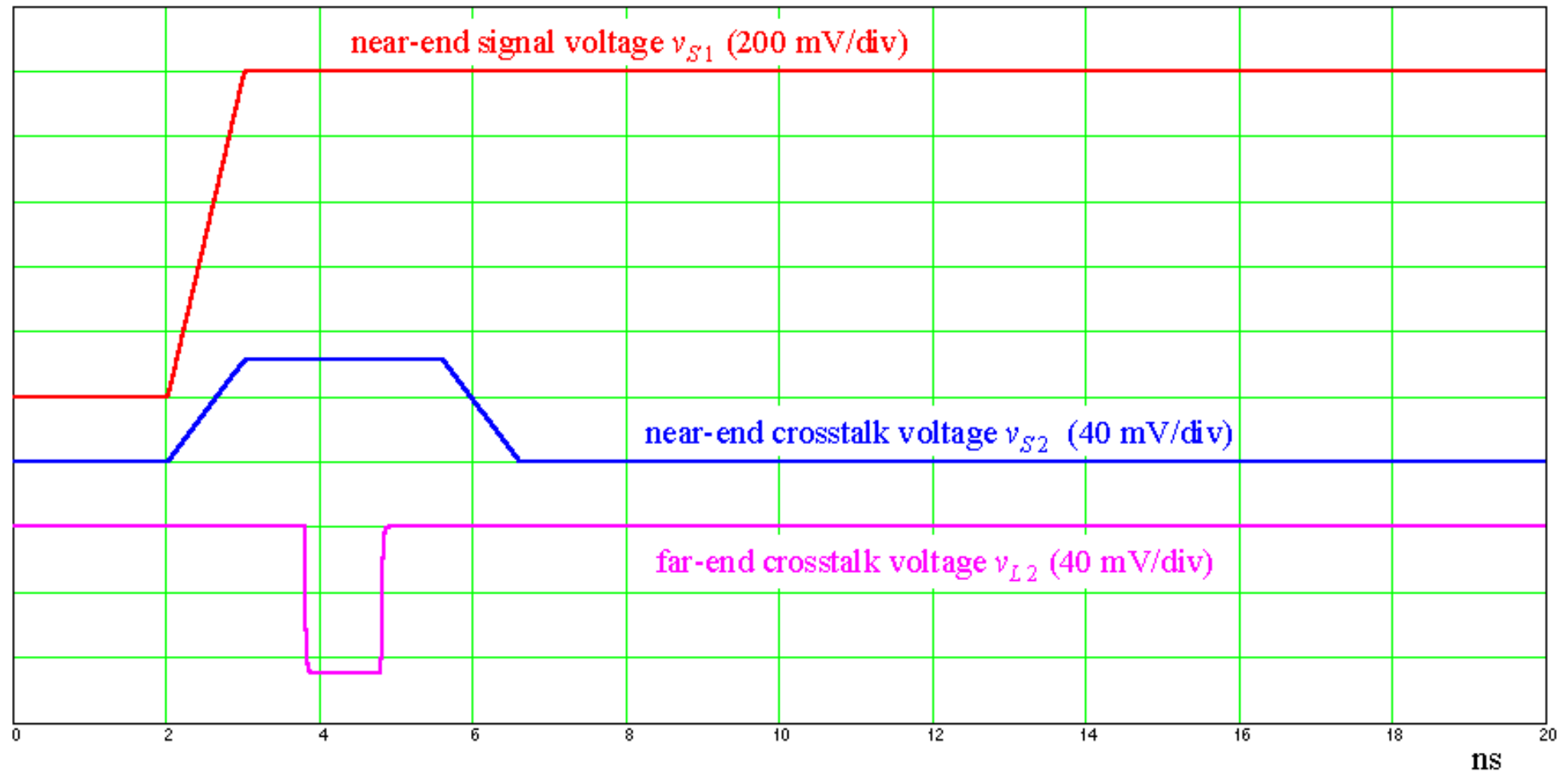In the time domain, for the step having 0%-100% rise time of 1 ns, we obtain the classical waveforms of this approximation:



□ If we do not assume $Z_{S1} = Z_{L1} = Z_{01}$, it is useful to define the parameters

$$\rho_{S1} = \frac{Z_{S1} - Z_{01}}{Z_{S1} + Z_{01}} \quad \text{and} \quad \rho_{L1} = \frac{Z_{L1} - Z_{01}}{Z_{L1} + Z_{01}} \quad (80)$$

and

$$K_{MR1} = \sum_{p=0}^{\infty} \left(\rho_{S1} \rho_{L1} e^{-2j\frac{\omega}{c_1}L} \right)^p = \frac{1}{1 - \rho_{S1} \rho_{L1} e^{-2j\frac{\omega}{c_1}L}} \quad (81)$$

□ If we do not assume $Z_{S2} = Z_{L2} = Z_{02}$, it is useful to define the parameters

$$\rho_{S2} = \frac{Z_{S2} - Z_{02}}{Z_{S2} + Z_{02}} \quad \text{and} \quad \rho_{L2} = \frac{Z_{L2} - Z_{02}}{Z_{L2} + Z_{02}} \quad (82)$$

and

$$K_{MR2} = \sum_{p=0}^{\infty} \left(\rho_{S2} \rho_{L2} e^{-2j\frac{\omega}{c_2}L} \right)^p = \frac{1}{1 - \rho_{S2} \rho_{L2} e^{-2j\frac{\omega}{c_2}L}} \quad (83)$$

□ If we only assume negligible losses, weak coupling and $c_1 = c_2 = c$, we get:

$$v_{S2} = \frac{e_S(1 - \rho_{S1})(1 + \rho_{S2})K_{MR1}K_{MR2}\xi_2}{4} \left\{ \begin{aligned} &\left(1 + \rho_{L1}\rho_{L2}e^{-2j\frac{\omega}{c}L}\right) \frac{\Xi_2 + 1}{2} \left(1 - e^{-2j\frac{\omega}{c}L}\right) \\ &-(\rho_{L1} + \rho_{L2}) \frac{j\omega}{c} (\Xi_2 - 1) \mathcal{L} e^{-2j\frac{\omega}{c}L} \end{aligned} \right\} \quad (84)$$

and

$$v_{L2} = \frac{e_S(1 - \rho_{S1})(1 + \rho_{L2})K_{MR1}K_{MR2}\xi_2}{4} \left\{ \begin{aligned} &(\rho_{L1} + \rho_{S2}) \frac{\Xi_2 + 1}{2} \left(1 - e^{-2j\frac{\omega}{c}L}\right) \\ &-\left(1 + \rho_{L1}\rho_{S2}e^{-2j\frac{\omega}{c}L}\right) \frac{j\omega}{c} (\Xi_2 - 1) \mathcal{L} \end{aligned} \right\} e^{-j\frac{\omega}{c}L} \quad (85)$$

- In the case where \mathcal{L} is not electrically short, a practical link is such that, for reducing echo, the NIT and/or the FIT must provide a low reflection coefficient at at least one end of each TC. Thus, we can assume that $K_{MR1} \approx 1$ and $K_{MR2} \approx 1$.
- The internal crosstalk mitigation approaches taught by (84) and (85) are:
 - ◆ increasing the distance between the TCs relative to the distance between a TC and the GC, to obtain a decrease of ξ_{12} ;
 - ◆ making Ξ_2 close to 1;
 - ◆ making Z_{L1} close to Z_{01} reduces the absolute value of 2 terms in (84) and 2 terms in (85);
 - ◆ making Z_{L2} close to Z_{02} reduces the absolute value of 2 terms in (84);
 - ◆ making Z_{S2} close to Z_{02} reduces the absolute value of 2 terms in (85);
 - ◆ decreasing as much as possible the bandwidth of the line receivers;
 - ◆ decreasing as much as possible the bandwidth of the line drivers.




- Eq. (72) shows that, for a lossless MTL, at a time $t < 2 \tau_{\min}$ from an excitation, \mathbf{v}_S is only determined by $\mathbf{Z}_C (\mathbf{Z}_S + \mathbf{Z}_C)^{-1} \mathbf{e}_S$. This exact result is compatible with (78) and (84): \mathcal{L} plays no role and ω plays no role except, possibly, in \mathbf{Z}_S .
- Using (72), it can be shown that, for a completely degenerate MTL seeing pseudo-matched impedances at the ends of each TC, there is no FEXT to the first order in the weak coupling approximation. This result is compatible with (79).
- Thus, in a long single-ended link terminated with pseudo-matched impedances,
 - ◆ the cause of NEXT is the lack of matching at the near-end; and
 - ◆ the cause of FEXT is the propagation of modes at unequal velocities.
- It is often difficult to use low-swing transmission in the single-ended links of a digital IC due to common-mode coupling at the near-end or at the far-end.
- A compensation or equalization scheme used to flatten the channel gain in the bandwidth used for transmission unfortunately increases the FEXT.

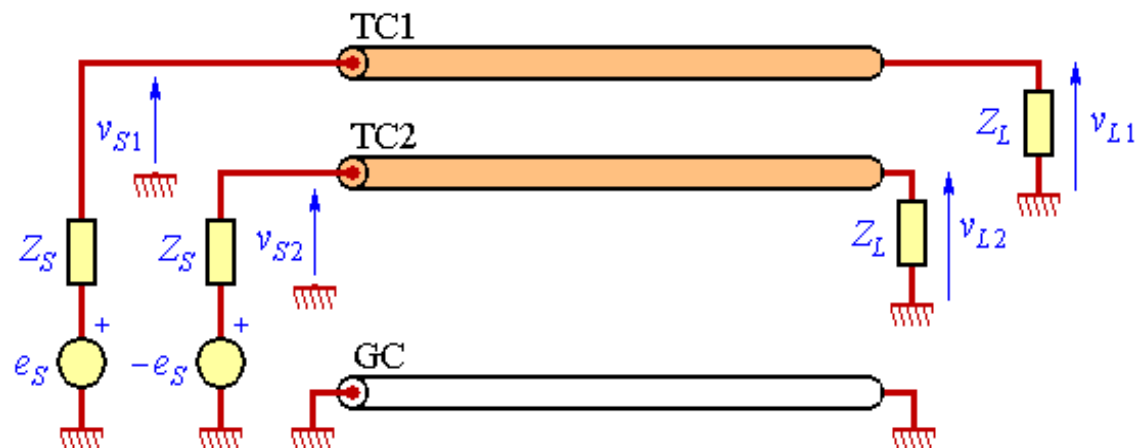13. Multichannel differential links

- ❑ A **balanced pair** comprises 2 TCs having the same *averaged* p.u.l. impedance and p.u.l. admittance with respect to the GC.
- ❑ In a link using a 2-TC interconnection, a NIT or FIT is balanced if the signal terminals present the same admittance with respect to the GC.
- ❑ Using a balanced pair and balanced NIT and FIT, *it seems that* a differential-mode source and a common-mode source produce opposite and equal voltages with respect to the GC, respectively, at each z .

For instance, for $L'_{11} = L'_{22}$ and $C'_{11} = C'_{22}$, in the link shown, by symmetry we have
 $-v_{S2} = v_{S1}$ and $-v_{L2} = v_{L1}$.



- ❑ A single-channel differential link uses this configuration with:
 - ◆ a transmitting circuit using a differential-mode source for signaling (differential line driver); and
 - ◆ a receiving circuit sensitive to differential mode signals and insensitive to the common-mode voltages (differential line receiver).

- ❑ This crosstalk cancellation scheme may effectively reduce the effect of 3 causes of external crosstalk:
 - ◆ a conductor crossing the interconnection;
 - ◆ common-mode coupling at the near-end;
 - ◆ common-mode coupling at the far-end.

- ❑ However, this is only true if other parallel conductors do not disturb the symmetry of the TCs. For instance, the following geometry may cause problems:



- ❑ A **perfectly balanced pair** comprises 2 TCs such that [50]:
 - ◆ the TCs have the same *averaged* p.u.l. impedance and p.u.l. admittance with respect to the GC;
 - ◆ the excitation of the pair in differential mode induces no voltage and injects no current in any other conductor.
- ❑ Reciprocity entails that a voltage appearing on or a current flowing in such other conductor produces no differential mode excitation in the perfectly balanced pair.
- ❑ A single-channel differential link using a perfectly balanced pair implements a crosstalk cancellation scheme which reduces all causes of external crosstalk.
- ❑ The second condition for a perfectly balanced pair may be satisfied using a sufficient distance from other parallel conductors, or using a frequent twisting [30]:



□ The twisted pair behaves as a uniform interconnection only if the length of a twist is much smaller than the wavelength, hence the use of *averaged* in the definitions.

□ Let us study the propagation in an isolated pair which need not be balanced.

◆ We write:

$$\mathbf{Z}' = \begin{pmatrix} Z'_{11} & Z'_{12} \\ Z'_{12} & Z'_{22} \end{pmatrix} \quad \text{and} \quad \mathbf{Y}' = \begin{pmatrix} Y'_{11} & Y'_{12} \\ Y'_{12} & Y'_{22} \end{pmatrix} \quad (86)$$

so that

$$\mathbf{Z}' \mathbf{Y}' = \begin{pmatrix} Z'_{11}Y'_{11} + Z'_{12}Y'_{12} & Z'_{11}Y'_{12} + Z'_{12}Y'_{22} \\ Z'_{12}Y'_{11} + Z'_{22}Y'_{12} & Z'_{12}Y'_{12} + Z'_{22}Y'_{22} \end{pmatrix} \quad (87)$$

◆ We find that the propagation constants are the solutions of the equation

$$\gamma^2 = \frac{1}{2} \left(\begin{array}{c} Z'_{11}Y'_{11} + 2Z'_{12}Y'_{12} + Z'_{22}Y'_{22} \\ \pm \sqrt{(Z'_{11}Y'_{11} - Z'_{22}Y'_{22})^2 + 4(Z'_{11}Y'_{12} + Z'_{12}Y'_{22})(Z'_{22}Y'_{12} + Z'_{12}Y'_{11})} \end{array} \right) \quad (88)$$

◆ For $(Z'_{11}Y'_{11} - Z'_{22}Y'_{22})^2 + 4(Z'_{11}Y'_{12} + Z'_{12}Y'_{22})(Z'_{22}Y'_{12} + Z'_{12}Y'_{11}) = 0$, we have degenerate eigenvalues. Assuming that $\mathbf{Z}' \mathbf{Y}'$ is diagonalizable, we reach the conclusion that $\mathbf{Z}' \mathbf{Y}'$ is diagonal.

Thus, \mathbf{S} can be any invertible matrix. Any non-trivial linear combination of natural voltages is a modal voltage. Same thing for the currents. We find:

$$\mathbf{Z}_C = \Gamma^{-1} \mathbf{Z}' = \frac{2}{Z'_{11}Y'_{11} + 2Z'_{12}Y'_{12} + Z'_{22}Y'_{22}} \begin{pmatrix} Z'_{11} & Z'_{12} \\ Z'_{12} & Z'_{22} \end{pmatrix} \quad (89)$$

◆ For $(Z'_{11}Y'_{11} - Z'_{22}Y'_{22})^2 + 4(Z'_{11}Y'_{12} + Z'_{12}Y'_{22})(Z'_{22}Y'_{12} + Z'_{12}Y'_{11}) \neq 0$, we have two distinct eigenvalues, denoted by γ_1 and γ_2 . We find that we can use

$$\mathbf{S} = \begin{pmatrix} -Z'_{11}Y'_{12} - Z'_{12}Y'_{22} & -Z'_{11}Y'_{12} - Z'_{12}Y'_{22} \\ Z'_{11}Y'_{11} + Z'_{12}Y'_{12} - \gamma_1^2 & Z'_{11}Y'_{11} + Z'_{12}Y'_{12} - \gamma_2^2 \end{pmatrix} \quad (90)$$

There is no simple result for $\mathbf{Z}_C = \mathbf{S} \Gamma^{-1} \mathbf{S}^{-1} \mathbf{Z}'$.

□ For a perfectly balanced pair, we have $Z'_{11} = Z'_{22}$ and $Z'_{12} = Z'_{21}$ so that (88) and (90) lead us to:

$$\begin{cases} \gamma_1 = \sqrt{Z'_{11}Y'_{11} + Z'_{12}Y'_{12} - Z'_{11}Y'_{12} - Z'_{12}Y'_{11}} = \sqrt{(Z'_{11} - Z'_{12})(Y'_{11} - Y'_{12})} \\ \gamma_2 = \sqrt{Z'_{11}Y'_{11} + Z'_{12}Y'_{12} + Z'_{11}Y'_{12} + Z'_{12}Y'_{11}} = \sqrt{(Z'_{11} + Z'_{12})(Y'_{11} + Y'_{12})} \end{cases} \quad (91)$$

□ Here, we can use the traditional biorthonormal eigenvectors defined by

$$\mathbf{S} = \begin{pmatrix} 1/2 & 1 \\ -1/2 & 1 \end{pmatrix} \quad \text{and} \quad \mathbf{T} = {}^t\mathbf{S}^{-1} = \begin{pmatrix} 1 & 1/2 \\ -1 & 1/2 \end{pmatrix} \quad (92)$$

for which

- ◆ v_{M1} is the differential-mode voltage $v_{DM} = v_1 - v_2$;
- ◆ i_{M1} is the differential-mode current $i_{DM} = (i_1 - i_2)/2$;
- ◆ v_{M2} is the common-mode voltage $v_{CM} = (v_1 + v_2)/2$;
- ◆ i_{M2} is the common-mode current $i_{CM} = i_1 + i_2$.

□ For the isolated balanced pair, we obtain

$$\mathbf{Z}_{MC} = \text{diag}_2(Z_{DM}, Z_{CM}) \quad (93)$$

where

$$Z_{DM} = 2 \sqrt{\frac{Z'_{11} - Z'_{12}}{Y'_{11} - Y'_{12}}} \quad \text{and} \quad Z_{CM} = \frac{1}{2} \sqrt{\frac{Z'_{11} + Z'_{12}}{Y'_{11} + Y'_{12}}} \quad (94)$$


Z_{DM} and Z_{CM} are traditionally referred to as the *differential-mode characteristic impedance* and the *common-mode characteristic impedance*, respectively.

□ For an isolated balanced pair, the characteristic impedance matrix is given by:

$$\mathbf{Z}_C = \begin{pmatrix} Z_{CM} + \frac{1}{4} Z_{DM} & Z_{CM} - \frac{1}{4} Z_{DM} \\ Z_{CM} - \frac{1}{4} Z_{DM} & Z_{CM} + \frac{1}{4} Z_{DM} \end{pmatrix} \quad (95)$$



- ❑ Many link designs use terminations only intended to provide a suitable Z_{DM} .
- ❑ A **perfectly balanced interconnection** comprises p pairs such that [50]:
 - ◆ the TCs of the same pair have the same *averaged* p.u.l. impedance and p.u.l. admittance with respect to the GC;
 - ◆ the excitation of any pair in differential mode induces no voltage and injects no current in any other conductor.
- ❑ The second condition for a perfectly balanced pair may be satisfied using a sufficient distance from other parallel conductors and/or using a frequent transposition of the TCs of each pair.
- ❑ In transposition, the TCs of each pair exchange position at intervals along the line so as to balance out, as exactly as possible, unwanted voltages and currents induced by adjacent circuits, while complying with the first condition.

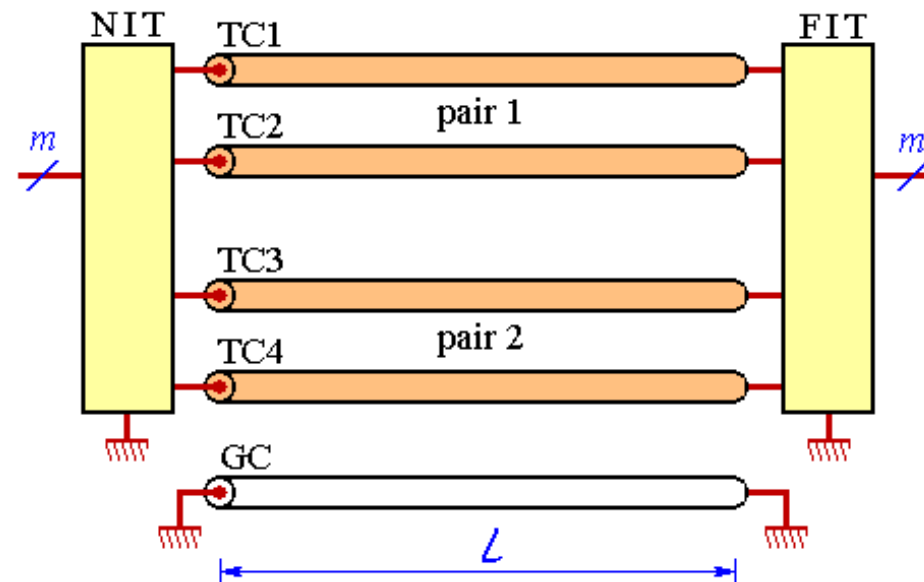

- ❑ *Differential transmission*: any transmission scheme in which two TCs (*a pair*), a differential line driver and a differential line receiver are allocated to each channel.
- ❑ A *multichannel differential link* uses differential transmission. It must be such that:
 - ◆ the interconnection nearly behaves as a perfectly balanced interconnection;
 - ◆ each pair of signal terminals of the NIT or of the FIT, intended to be connected to an end of a single pair, is nearly balanced.



- ❑ Note that TC-to-TC coupling is not a problem:
 - ◆ between the TCs of the same pair;
 - ◆ if it occurs between the TCs of different pairs, if it is balanced out.
- ❑ A multichannel differential link using a perfectly balanced interconnection implements a crosstalk cancellation scheme which:
 - ◆ reduces internal crosstalk;
 - ◆ reduces the effect of all causes of external crosstalk.
- ❑ A differential link can be point-to-point or multidrop.
- ❑ Each pair of a differential point-to-point link can be used for unidirectional (simplex) transmission, alternate bidirectional (half duplex) transmission or simultaneous bidirectional (full duplex) transmission.
- ❑ Each pair of a differential multidrop link can be used for unidirectional transmission or as a bus.

□ For p pairs, for $\alpha \in \{1, \dots, p\}$, we can define

- ◆ p differential-mode voltages $v_{DM\alpha} = v_{2\alpha-1} - v_{2\alpha}$;
- ◆ p differential-mode currents $i_{DM\alpha} = (i_{2\alpha-1} - i_{2\alpha})/2$;
- ◆ p pair common-mode voltages $v_{CM\alpha} = (v_{2\alpha-1} + v_{2\alpha})/2$;
- ◆ p pair common-mode currents $i_{CM\alpha} = i_{2\alpha-1} + i_{2\alpha}$.

□ We do not imply that these variables are propagation modes of the interconnection.

□ It can be shown that, **for a perfectly balanced interconnection** [50]:

- ◆ the differential-mode voltages and the differential-mode currents are propagation modes of the interconnection;
- ◆ thus, there is no coupling between the differential-mode variables of a pair and the differential-mode or pair common-mode variables of another pair;
- ◆ thus, **in the case of an ideal NIT and of an ideal FIT**, there is no internal crosstalk.



- ❑ In a densely wired PCB or MCM, the interconnection is often far from being perfectly balanced.
- ❑ The interconnection model underlying the concept of differential links excludes any coupling between the differential-mode variables of a pair and currents or voltages on other conductors. Thus, possible models are:
 - ◆ one ideal node for each TC, in the case of a short interconnection;
 - ◆ a lumped elements model for each pair, in the case of a longer but electrically short interconnections;
 - ◆ a 3-conductor MTL model for each pair;
 - ◆ a uniform 3-conductor MTL model for each pair, if the interconnection is uniform;
 - ◆ a TL model for the differential-mode variable of each pair;
 - ◆ a uniform TL model for the differential-mode variable of each pair, if the interconnection is uniform.

- ❑ Since the underlying interconnection model excludes the couplings between the differential-mode variables on a pair and the differential-mode or pair common-mode variables relating to another pair, actual non-zero values of these couplings are likely to produce internal crosstalk.
- ❑ In the case $n \geq 2$, it is advisable to take TC-to-TC coupling into account at the analysis stage. It is possible to use:
 - ◆ a lumped element model for an electrically short interconnection;
 - ◆ an exact solution of a lossless MTL model using natural variables;
 - ◆ an exact solution of a lossless MTL model using the differential-mode and common-mode variables;
 - ◆ an exact solution of a MTL model taking losses into account;
 - ◆ an exact solution of a MTL model using the differential-mode and common-mode variables and taking losses into account.

- ❑ In the usual case where transposition is not used, a discussion of the design options for a multichannel differential link must take into account the length L and :
 - ◆ the types of pairs (microstrip, edge-coupled stripline, broadside-coupled stripline, ...) and the tightness of the coupling between the TCs of each pair;
 - ◆ the relative position of the pairs;
 - ◆ the type of termination for each pair (unterminated, terminated at one or both ends, using pseudo-matched or floating impedors, or π or Y terminations);
 - ◆ the type of differential line driver and differential line receivers (voltage-mode, current mode [52] [82] [89]).

- ❑ A differential link of a digital IC can use low-swing transmission if it is sufficiently immune to common-mode coupling at the near-end and at the far-end.

- ❑ A wide-band differential link can use a compensation or equalization schemes to flatten the channel gain, if the high-frequency crosstalk is sufficiently low [81].

14. Modal signaling


□ Up to now, we have considered the modal decomposition as a step in the MTL theory used for computing voltages and currents in a uniform multiconductor interconnection having n TCs.

□ In § 4, we used

$$\begin{cases} \mathbf{v}_M = e^{-z\Gamma} \mathbf{v}_{M0+} + e^{z\Gamma} \mathbf{v}_{M0-} \\ \mathbf{i}_M = e^{-z\Gamma} \mathbf{i}_{M0+} + e^{z\Gamma} \mathbf{i}_{M0-} \end{cases} \quad (26)$$

where \mathbf{v}_{M0+} , \mathbf{v}_{M0-} , \mathbf{i}_{M0+} and \mathbf{i}_{M0-} are z -independent vectors. We see that propagation entails an alteration of $\mathbf{v}_{M+} = e^{-z\Gamma} \mathbf{v}_{M0+}$, $\mathbf{v}_{M-} = e^{z\Gamma} \mathbf{v}_{M0-}$, $\mathbf{i}_{M+} = e^{-z\Gamma} \mathbf{i}_{M0+}$ and $\mathbf{i}_{M-} = e^{z\Gamma} \mathbf{i}_{M0-}$, but no interference between the entries of each of these vectors.

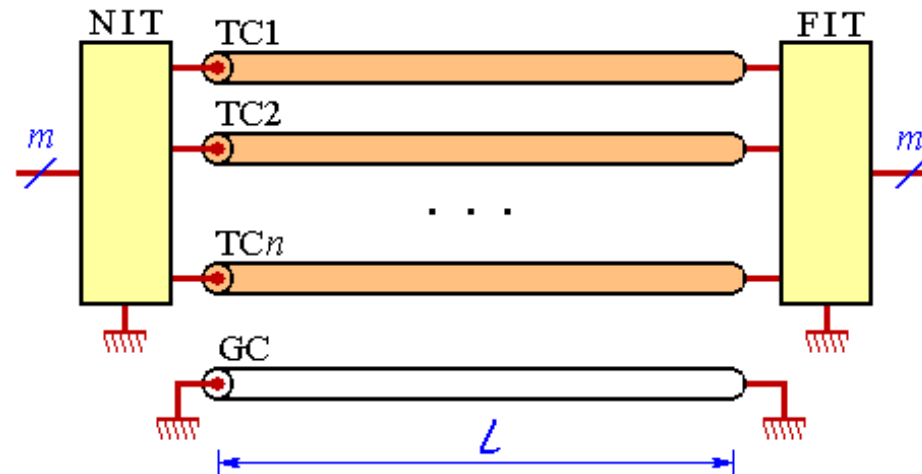□ This suggests a modal signaling method for removing crosstalk in a m -channel link using a uniform multiconductor interconnection having $n \geq m$ TCs.



□ In modal signaling:

- ◆ for each of the m transmission channels, we use a modal electrical variable (modal voltage or modal current), instead of a natural electrical variable (natural voltage or natural current) in single-ended signaling;
- ◆ the modal electrical variables used for transmission are all modal voltages or all modal currents;
- ◆ the NIT and the FIT must perform the necessary conversions, which are defined by a transition matrix from modal electrical variables to natural electrical variables, i.e., **S** or **T**.



- A differential link implements modal signaling, for $m = 1$ and $n = 2$. In this case, \mathbf{S} and \mathbf{T} are determined by the symmetry of the interconnection so that:
 - ◆ they are frequency-independent, according to (92);
 - ◆ \mathbf{v}_M and \mathbf{i}_M are easily defined in the time and frequency domains.
- In most multiconductor interconnections such that $n \geq 3$, \mathbf{S} and \mathbf{T} are not fully determined by the symmetries and are frequency dependent complex matrices.
- A simplified definition of the general ZXtalk method reads as follows:
 - ◆ for each of the m transmission channels, we use a modal voltage or a modal current (modal signaling);
 - ◆ the interconnection has n TCs, with $n \geq m$, and it is terminated with at least one matched or almost matched termination, i.e. a $(n + 1)$ -terminal linear termination circuit having an impedance matrix approximating \mathbf{Z}_C .



- ❑ According to this simplified definition of the general ZXtalk method, no internal crosstalk and no echo occurs in the transmission channels since:
 - ◆ the total decoupling provides an independent propagation of each eigen-voltage with the associated eigen-current;
 - ◆ the termination circuits absorb incident waves so that they do not create couplings between the modes.

- ❑ According to this simplified definition, at each frequency used for transmission,
 - ◆ a transmitting circuit (TX circuit) must combine the input signals according to linear combinations defined by \mathbf{S} or \mathbf{T} ;
 - ◆ a receiving circuit (RX circuit) must combine the signals present on the TCs according to linear combinations defined by \mathbf{S}^{-1} or \mathbf{T}^{-1} .

- ❑ Unfortunately, it is difficult to perform the modal variable to natural variable conversion when \mathbf{S} and \mathbf{T} are frequency dependent complex matrices.



□ In the RC region [31, ch. 3], we may consider that $\mathbf{Z}' \approx \mathbf{R}'$ and $\mathbf{Y}' \approx j\omega \mathbf{C}'$ where \mathbf{R}' and \mathbf{C}' are frequency-independent matrices. Thus,

◆ \mathbf{Z}_C is in the form
$$\mathbf{Z}_C \approx \frac{1-j}{\sqrt{2}\omega} \mathbf{A}_C \quad (96)$$

where \mathbf{A}_C is a real and frequency-independent matrix;

◆ this \mathbf{Z}_C cannot be realized accurately over a wide relative bandwidth, using a lumped termination circuit;

◆ thus, we are in trouble to implement the simplified definition of the general ZXtalk method at low frequencies.


□ However,

◆ a reduction of crosstalk or echo is not needed at low frequencies;

◆ the simplified definition of the general ZXtalk method is easy to implement at high frequencies such that $\mathbf{Z}' \approx j\omega \mathbf{L}'$, where \mathbf{Z}_C is real and frequency-independent, and where \mathbf{S} and \mathbf{T} may be chosen real and frequency-independent.

□ According to a more general definition [27] [28], the general ZXtalk method relates to an m -channel link such that:


- ◆ the interconnection has n TCs, with $n \geq m$, and may be modeled as a uniform $(n + 1)$ -conductor MTL, with a sufficient accuracy, in a known frequency band;
- ◆ the interconnection is connected at at least one end to a termination circuit having, in the known frequency band, an impedance matrix near \mathbf{Z}_C ;
- ◆ a TX circuit delivers modal electrical variables defined by \mathbf{S} or \mathbf{T} , each modal electrical variable being mainly determined by one and only one input signal;
- ◆ a RX circuit delivers output signals, each of the output signals being mainly determined by one and only one of said modal electrical variables.

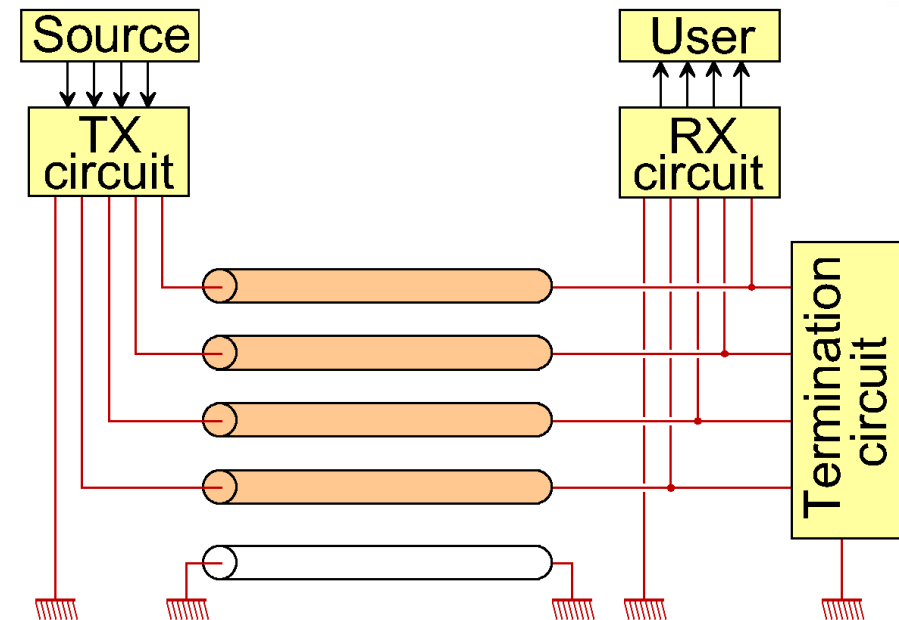

□ The “known frequency band” may correspond to high frequencies such that $\mathbf{Z}' \approx j\omega\mathbf{L}'$. Thus, for the synthesis of the link, we can use a lossless MTL model.


□ Consequently, we can use:

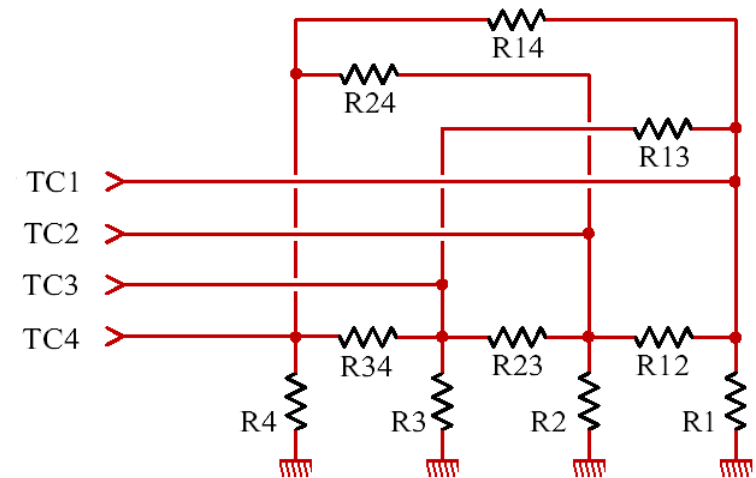- ◆ a termination circuit made of $n(n+1)/2$ resistors, as shown here for $n = 4$;
- ◆ TX circuits and RX circuits performing real and frequency-independent linear combinations.



□ Outside the known frequency band, the MTL model used for the synthesis of the link is not required to be an accurate model of the actual interconnection.

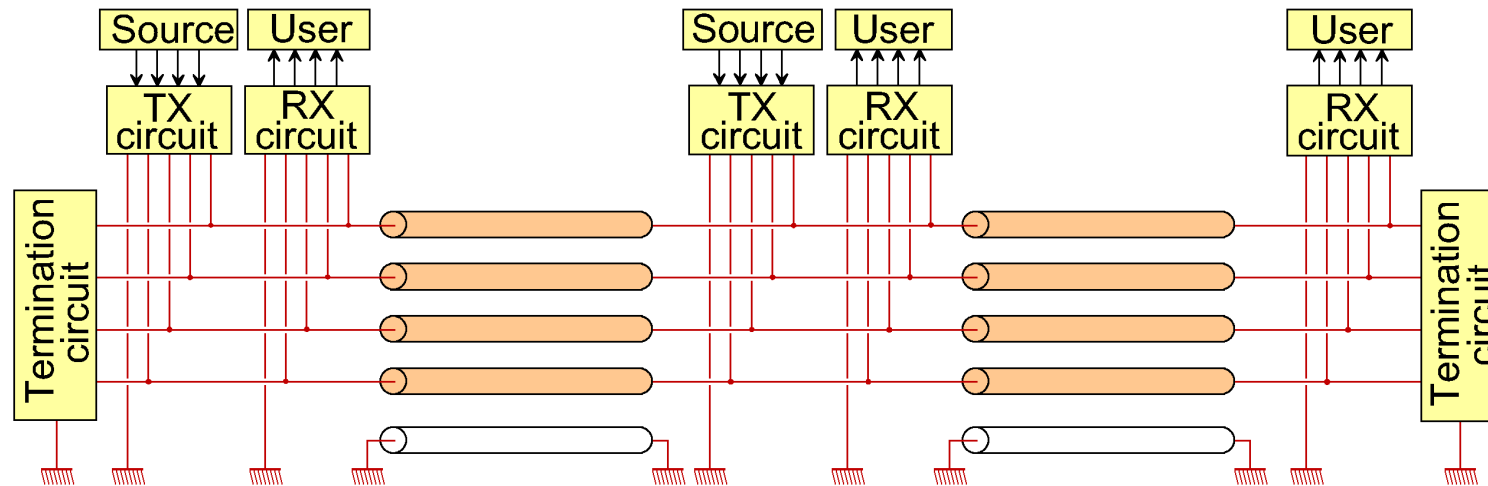□ Of course, for the analysis of the link, we should use an MTL model providing accurate predictions in the whole frequency band used for transmission. This accurate model could include losses and departures from the assumption of uniformity.



- ❑ A link implementing the ZXtalk method can be point-to-point or multidrop. Above: a bus using parallel connection for the TX circuits and RX circuits.
- ❑ Each mode of a point-to-point link implementing the ZXtalk method can be used for simplex, half duplex or full duplex transmission.
- ❑ Each mode of a multidrop link implementing the ZXtalk method can be used for simplex transmission or as a bus.

□ There are 8 possible designs, corresponding to the following equations:

Interface	Connection	Design using modal voltages (voltage-mode signaling)	Design using modal currents (current-mode signaling)
TX circuit	series (low impedance)	$\mathbf{v}_T = \pm a \mathbf{S} \text{diag}_n(\alpha_1, \dots, \alpha_n) \mathbf{x}_I$	$\mathbf{v}_T = a \mathbf{Z}_C \mathbf{T} \text{diag}_n(\lambda_1, \dots, \lambda_n) \mathbf{x}_I$
	parallel (high impedance)	$\mathbf{i}_T = a \mathbf{Z}_C^{-1} \mathbf{S} \text{diag}_n(\alpha_1, \dots, \alpha_n) \mathbf{x}_I$	$\mathbf{i}_T = \pm a \mathbf{T} \text{diag}_n(\lambda_1, \dots, \lambda_n) \mathbf{x}_I$
RX circuit	series (low impedance)	$\mathbf{x}_O = \pm \text{diag}_n(\beta_1, \dots, \beta_n) \mathbf{S}^{-1} \mathbf{Z}_C \mathbf{i}_R$	$\mathbf{x}_O = \text{diag}_n(\mu_1, \dots, \mu_n) \mathbf{T}^{-1} \mathbf{i}_R$
	parallel (high impedance)	$\mathbf{x}_O = \text{diag}_n(\beta_1, \dots, \beta_n) \mathbf{S}^{-1} \mathbf{v}_R$	$\mathbf{x}_O = \pm \text{diag}_n(\mu_1, \dots, \mu_n) \mathbf{T}^{-1} \mathbf{Z}_C^{-1} \mathbf{v}_R$

(97)

where \mathbf{x}_I , \mathbf{v}_T and \mathbf{i}_T are the column vectors of the input signals, output voltages and output currents of the TX circuit, respectively, a is the number of termination circuits; \mathbf{v}_R , \mathbf{i}_R and \mathbf{x}_O are the column vectors of the input voltages, input currents and output signals of the RX circuit, respectively; the α_i , λ_i , β_i , and the μ_i are arbitrary nonzero constants.



□ Between a TX circuit and a RX circuit connected to the interconnection at $z = z_{TX}$ and $z = z_{RX}$, respectively, we have, in the known frequency band:

$$x_{Oi} = \alpha_i \beta_i e^{-\gamma_i |z_{RX} - z_{TX}|} x_{Ii} \quad \text{or} \quad x_{Oi} = \lambda_i \mu_i e^{-\gamma_i |z_{RX} - z_{TX}|} x_{Ii} \quad (98)$$


according to the case.

□ It can be shown that voltage-mode signaling and current mode signaling are equivalent when generalized associated eigenvectors are used.

□ The general ZXtalk method reduces echo and internal crosstalk, but it does not reduce external crosstalk


□ For $n \geq 3$, a termination circuit can often use less than $n(n+1)/2$ resistors, for instance only $2n-1$ resistors.

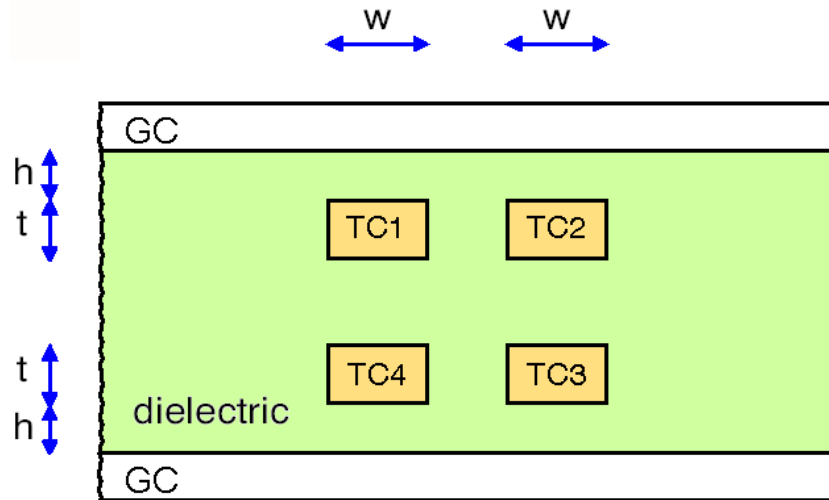□ However, the general ZXtalk method is mostly appropriate for small values of n , because the complexity of the TX and RX circuits increases as n^2 .



□ The ZXtalk method can easily be applied to a differential pair [38], to the 4-TC configuration shown [83] and to two differential pairs [87] [91].

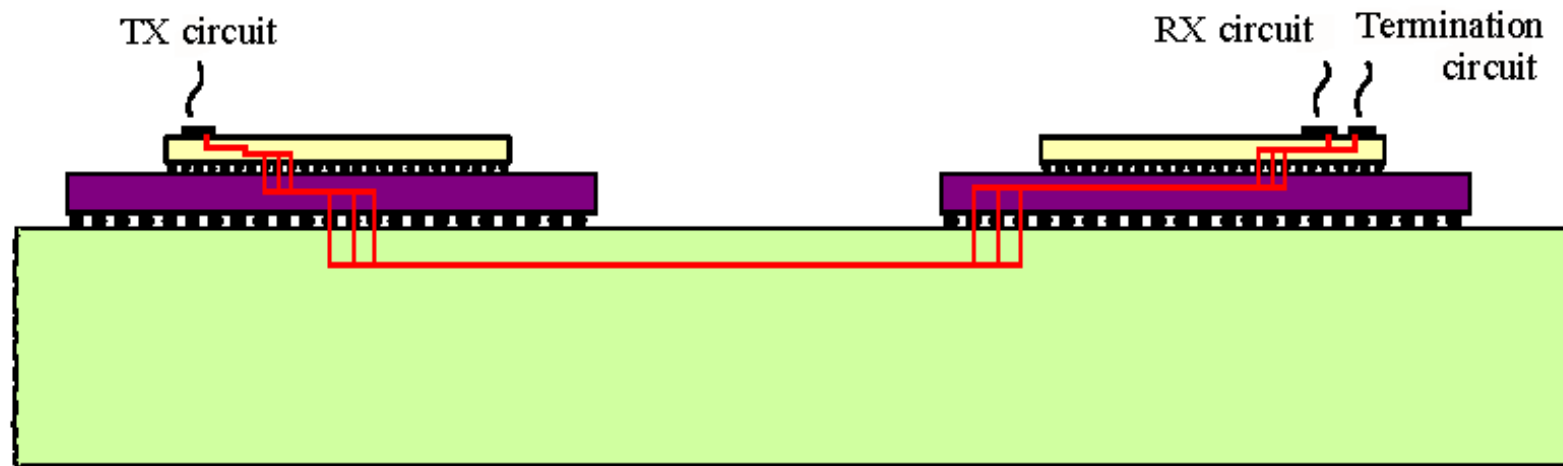□ It is possible to extend the general ZXtalk method to some interconnections which cannot be modeled with a uniform MTL. This extension is useful when one wishes to consider an interconnection spanning several substrates, such as shown below.



□ The basic ideas of this extension are the following [77]:

- ◆ we assume that the interconnection can be modeled as a non-uniform MTL, so that, at each point z we can formally define \mathbf{S} , \mathbf{T} and \mathbf{Z}_C using (23) and (31);
- ◆ we can require that \mathbf{S} and \mathbf{Z}_C are independent of z , a result which can easily be obtained in several important types of interconnections;
- ◆ we can then define \mathbf{v}_M and \mathbf{i}_M with (24), and show that they satisfy

$$\begin{cases} \frac{d^2 \mathbf{v}_M}{dz^2} - \Gamma^2 \mathbf{v}_M = \frac{d \Gamma}{dz} \Gamma^{-1} \frac{d \mathbf{v}_M}{dz} \\ \frac{d^2 \mathbf{i}_M}{dz^2} - \Gamma^2 \mathbf{i}_M = \frac{d \Gamma}{dz} \Gamma^{-1} \frac{d \mathbf{i}_M}{dz} \end{cases} \quad (99)$$

- ◆ Γ and $d \Gamma/dz$ being diagonal matrices, these equations are decoupled, so that we have achieved a modal decomposition applicable to the non-uniform MTL.

□ Suggested reading relating or relevant to modal signaling [9] [13] [19] [27] [28] [36] [37] [38] [39] [43] [55] [56] [67] [77] [80] [83] [85] [87] [91] [92].

15. Modal signaling in a decoupled interconnection

□ By definition, a completely degenerate interconnection (CDI) is such that $\gamma_1, \dots, \gamma_n$ may be regarded as equal, in a given frequency band. This for instance occurs when losses are negligible and the propagation medium is homogeneous, but we won't need these assumptions [11].

□ In the given frequency band, (23) defining \mathbf{T} and \mathbf{S} becomes

$$\begin{cases} \mathbf{T}^{-1} \mathbf{Y}' \mathbf{Z}' \mathbf{T} = \gamma^2 \mathbf{1}_n \\ \mathbf{S}^{-1} \mathbf{Z}' \mathbf{Y}' \mathbf{S} = \gamma^2 \mathbf{1}_n \end{cases} \quad (100)$$

where γ is the common value of the propagation constants. In (100) the eigenvalues are completely degenerate. We have :

$$\mathbf{Y}' \mathbf{Z}' = \mathbf{Z}' \mathbf{Y}' = \gamma^2 \mathbf{1}_n \quad (101)$$

Thus, \mathbf{S} and/or \mathbf{T} may be chosen equal to $\mathbf{1}_n$, so that

$$\mathbf{Z}_C = \frac{1}{\gamma} \mathbf{Z}' = \gamma \mathbf{Y}'^{-1} \quad (102)$$



- ❑ This choice clearly simplifies the ZXtalk method, since linear combinations are no longer needed in the TX circuits and RX circuits.
- ❑ A special ZXtalk method for CDI was defined, in which it was required that, in the known frequency band, the propagation constants of the different propagation modes may be considered as substantially equal [44] [73] [29].
- ❑ However, this definition is too restrictive since the desired effect of being able to choose \mathbf{S} and/or \mathbf{T} equal to $\mathbf{1}_n$ is obtained if and only if $\mathbf{Z}'\mathbf{Y}'$ is diagonal (or, equivalently $\mathbf{Y}'\mathbf{Z}'$ is diagonal).
- ❑ This circumstance can be referred to as a decoupled interconnection.
- ❑ We therefore propose the following definition of a *special ZXtalk method* in which it is required that, in the known frequency band, the interconnection may be considered as decoupled.

- According to a general definition, the special ZXtalk method relates to an m -channel link such that:
 - ◆ the interconnection has n TCs, with $n \geq m$, and may be modeled, with a sufficient accuracy, in a known frequency band, as a uniform $(n + 1)$ -conductor MTL such that the transition matrix from modal electrical variables to natural electrical variables may be considered as substantially equal to $\mathbf{1}_n$;
 - ◆ the interconnection is connected at at least one end to a termination circuit having, in the known frequency band, an impedance matrix near \mathbf{Z}_C ;
 - ◆ a TX circuit delivers natural electrical variables, each natural electrical variable being mainly determined by one and only one input signal;
 - ◆ a RX circuit delivers output signals, each of the output signals being mainly determined by one and only one of said natural electrical variables.

- The special ZXtalk method corresponds to a particular implementation of the general ZXtalk method, in which \mathbf{S} or \mathbf{T} are chosen equal to $\mathbf{1}_n$.

□ There are 8 possible designs, corresponding to the following equations:

Interface	Connection	Design using modal voltages (voltage-mode signaling)	Design using modal currents (current-mode signaling)
TX circuit	series (low impedance)	$\mathbf{v}_T = \pm a \text{diag}_n(\alpha_1, \dots, \alpha_n) \mathbf{x}_I$	$\mathbf{v}_T = a \mathbf{Z}_C \text{diag}_n(\lambda_1, \dots, \lambda_n) \mathbf{x}_I$
	parallel (high impedance)	$\mathbf{i}_T = a \mathbf{Z}_C^{-1} \text{diag}_n(\alpha_1, \dots, \alpha_n) \mathbf{x}_I$	$\mathbf{i}_T = \pm a \text{diag}_n(\lambda_1, \dots, \lambda_n) \mathbf{x}_I$
RX circuit	series (low impedance)	$\mathbf{x}_O = \pm \text{diag}_n(\beta_1, \dots, \beta_n) \mathbf{Z}_C \mathbf{i}_R$	$\mathbf{x}_O = \text{diag}_n(\mu_1, \dots, \mu_n) \mathbf{i}_R$
	parallel (high impedance)	$\mathbf{x}_O = \text{diag}_n(\beta_1, \dots, \beta_n) \mathbf{v}_R$	$\mathbf{x}_O = \pm \text{diag}_n(\mu_1, \dots, \mu_n) \mathbf{Z}_C^{-1} \mathbf{v}_R$


(103)


where \mathbf{x}_I , \mathbf{v}_T and \mathbf{i}_T are the column vectors of the input signals, output voltages and output currents of the TX circuit, respectively, a is the number of termination circuits; \mathbf{v}_R , \mathbf{i}_R and \mathbf{x}_O are the column vectors of the input voltages, input currents and output signals of the RX circuit, respectively; the α_i , λ_i , β_i , and the μ_i are arbitrary nonzero constants.

❑ In the designs shown above, the remaining difficulty is the floating TX circuits or RX circuits, connected in series with the interconnection.

❑ This difficulty is circumvented using a MIMO series-series feedback amplifier (MIMO-SSFA) that can be used to perform all linear combinations containing \mathbf{Z}_C^{-1} in the previous table, in a wide bandwidth.

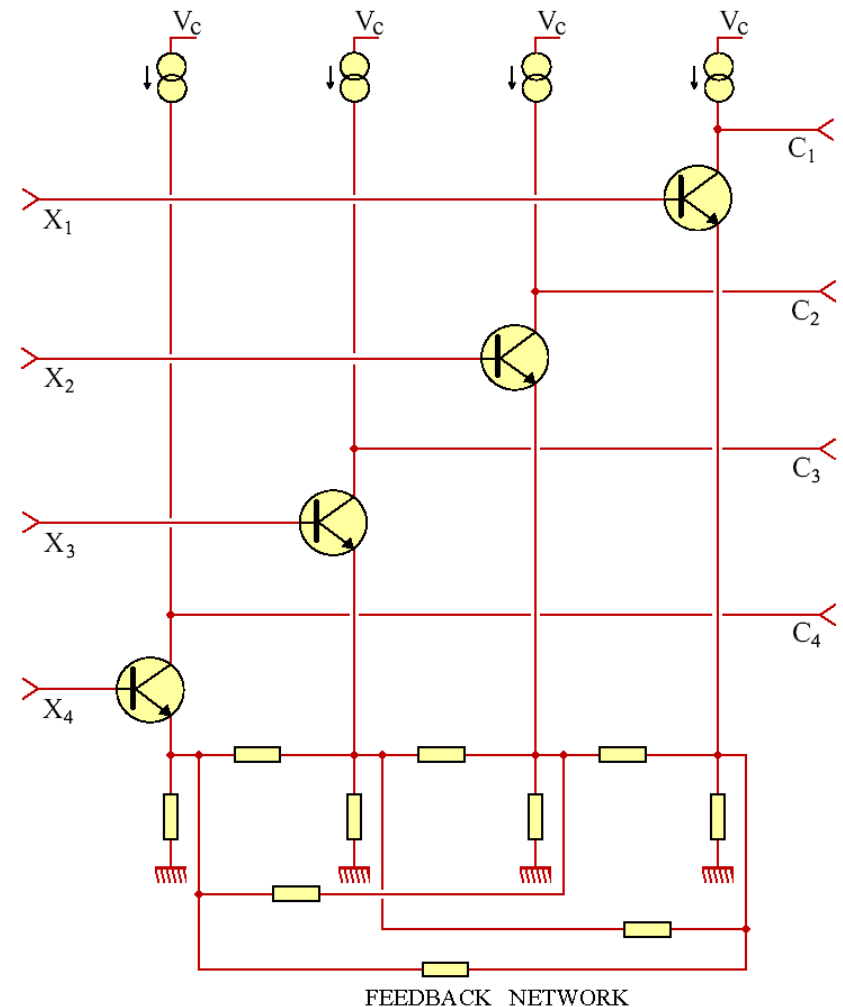Structure of a simple 4-channel MIMO-SSFA using bipolar transistors →



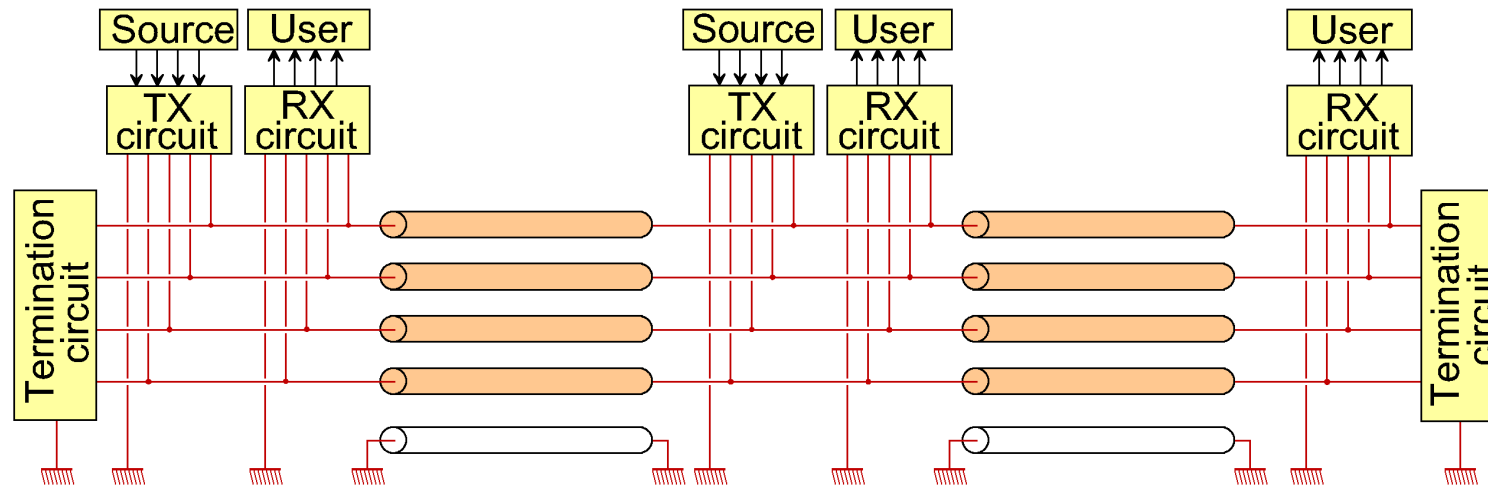

- ❑ A design using a MIMO-SSFA in each TX circuit may have the TX circuits and RX circuits connected in parallel with the interconnection.
- ❑ It is often possible to design such a link so that the number of circuit elements in the termination circuits and TX circuits is proportional to n when n is large [44].
- ❑ Thus, this method is appropriate for reducing echo and internal crosstalk in the widest bandwidth, and it is applicable to massively parallel interconnections.



□ We have seen that the FEXT is small, to the first order in the weak coupling approximation, in a single-ended link using a CDI and pseudo-matched impedances at the ends of each TC. Thus, the special ZXtalk method is mostly of interest in cases where:


- ◆ there is a strong coupling between the TCs; and/or
- ◆ the interconnection is used for bidirectional transmission.

□ Like the general ZXtalk method, the special ZXtalk method can be extended to some interconnections which cannot be modeled with a uniform MTL.


□ Suggested reading relating or relevant to the special ZXtalk method [29] [33] [34] [35] [38] [39] [41] [43] [44] [51] [53] [73] [76] [77] [83] [86] [88].

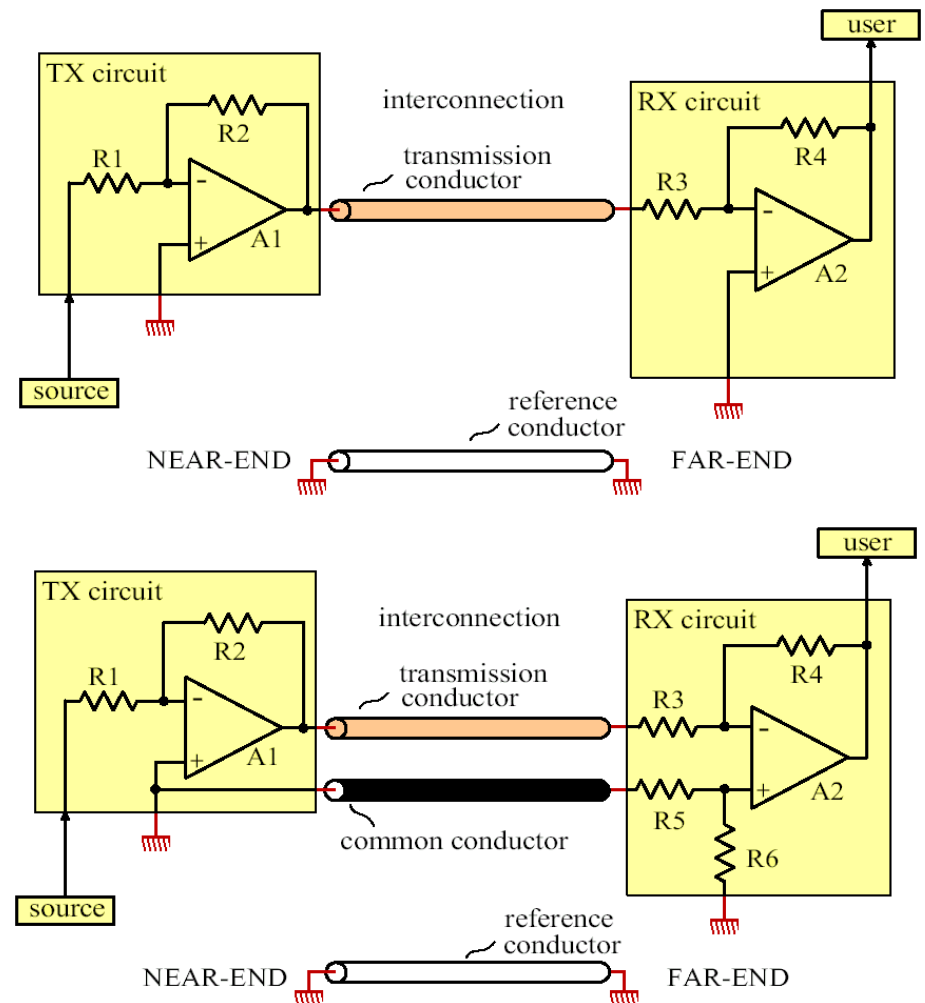16. Pseudo-differential links

- ❑ A single-ended link is subject to external crosstalk with other circuits on the same chip, MCM or PCB.
- ❑ A simple pseudo-differential link (PDL) is protected against crosstalk using little additional hardware.
- ❑ A PDL providing m channels uses only $m + 1$ conductors to reduce external crosstalk in m channels.
- ❑ There are four possible PDL architectures.




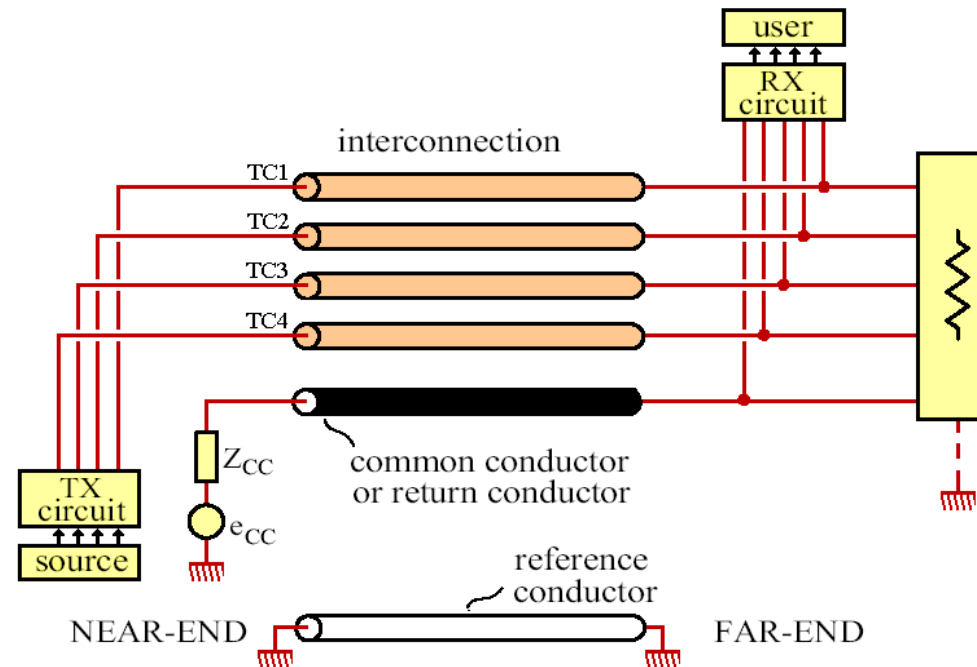❑ First architecture: a unidirectional PDL with voltage-driven common conductor (VDCC). The common conductor (CC) may be used as a return conductor (RC).




- ◆ The termination circuit may or may not be present.
- ◆ The TX circuit may be a conventional line driver (but this is not necessary).
- ◆ This VDCC architecture cannot be used in a bidirectional PDL.

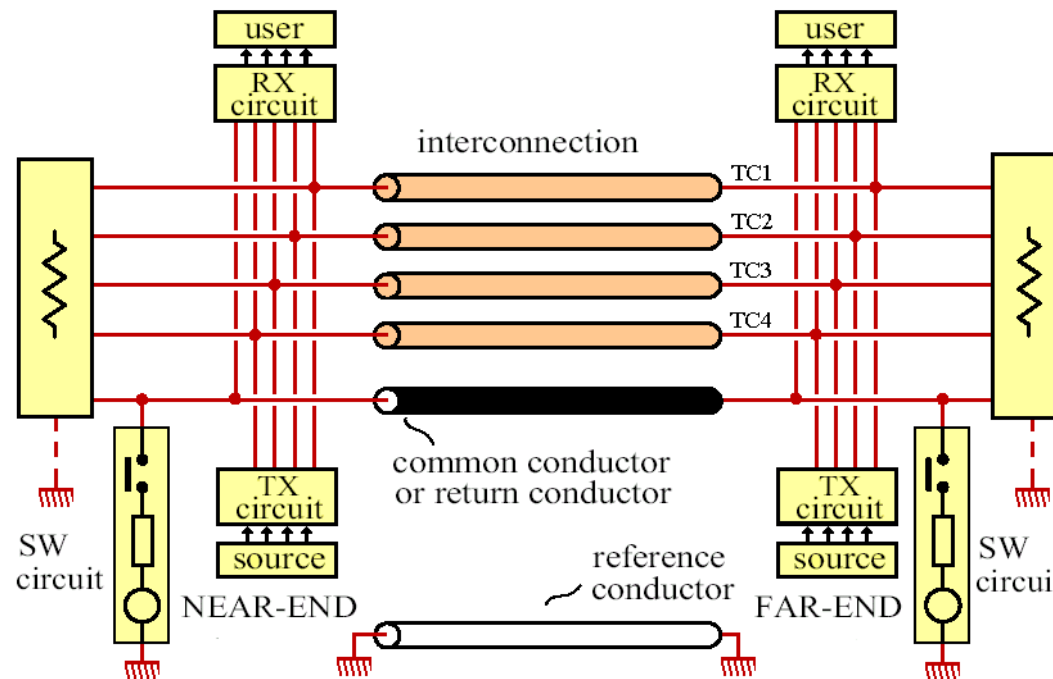
❑ Second architecture: a bidirectional PDL may be built using common terminal switching circuits (SW circuits).



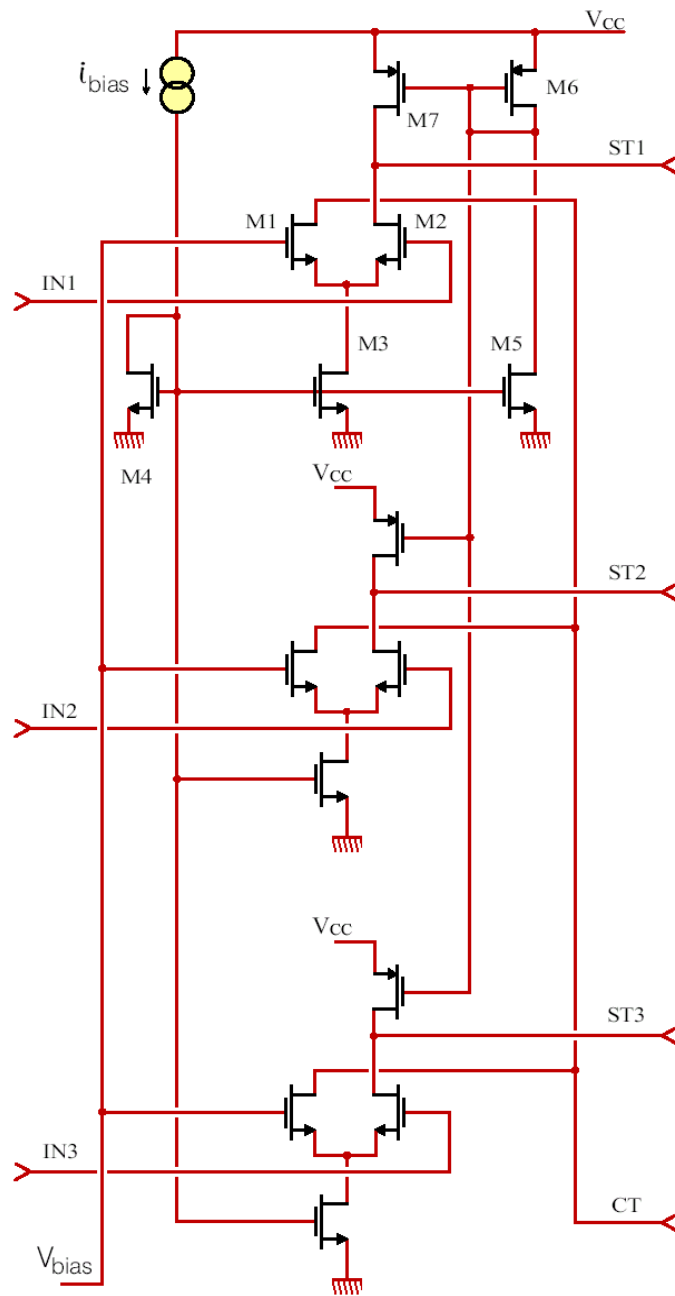
- ◆ One or more of the termination circuits may or may not be present.
- ◆ The TX circuits may be conventional 3-state line drivers.
- ◆ This SW circuit architecture cannot be used for full duplex operation.




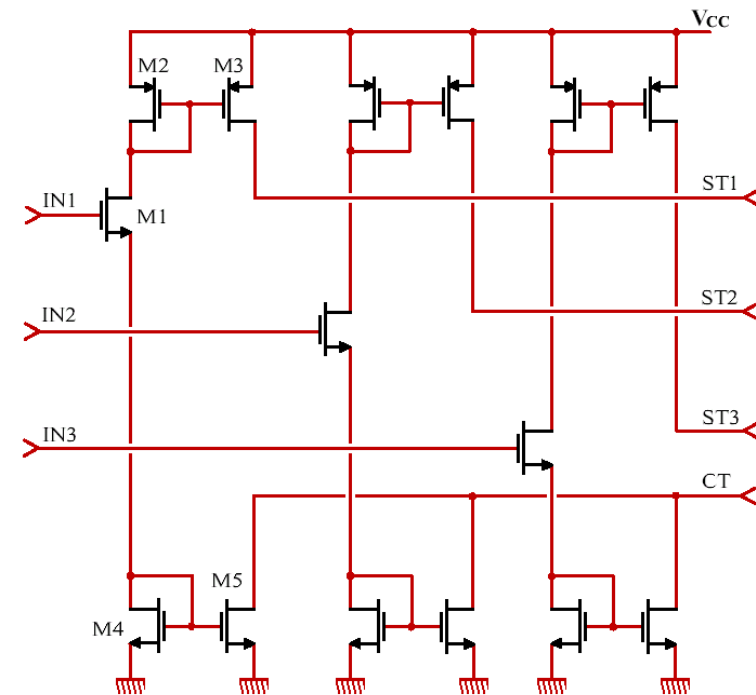□ PDLs may also use TX circuits producing a constant (or zero) common-mode current, such as the two 3-channels TX circuits shown here. The STn output terminal is coupled to the TCn . The CT output terminal is coupled to the RC.



- Let us use i_j to denote the current flowing from ST j to the TC j , and i_C to denote the current flowing from CT to the RC. In the TX-circuits shown above, a balancing circuit controls i_C in such a way that the TX circuit does not cause any significant variation of the common-mode current $i_1 + \dots + i_n + i_C$.
- Using such TX circuits, we can introduce constant common-mode current (CCMC) architectures

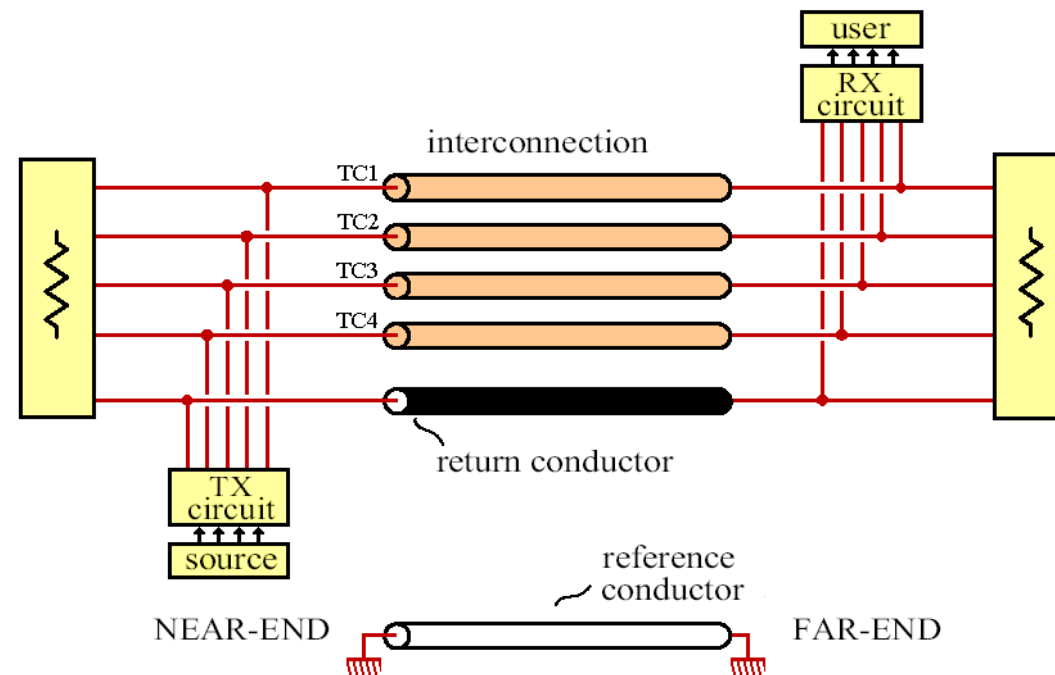

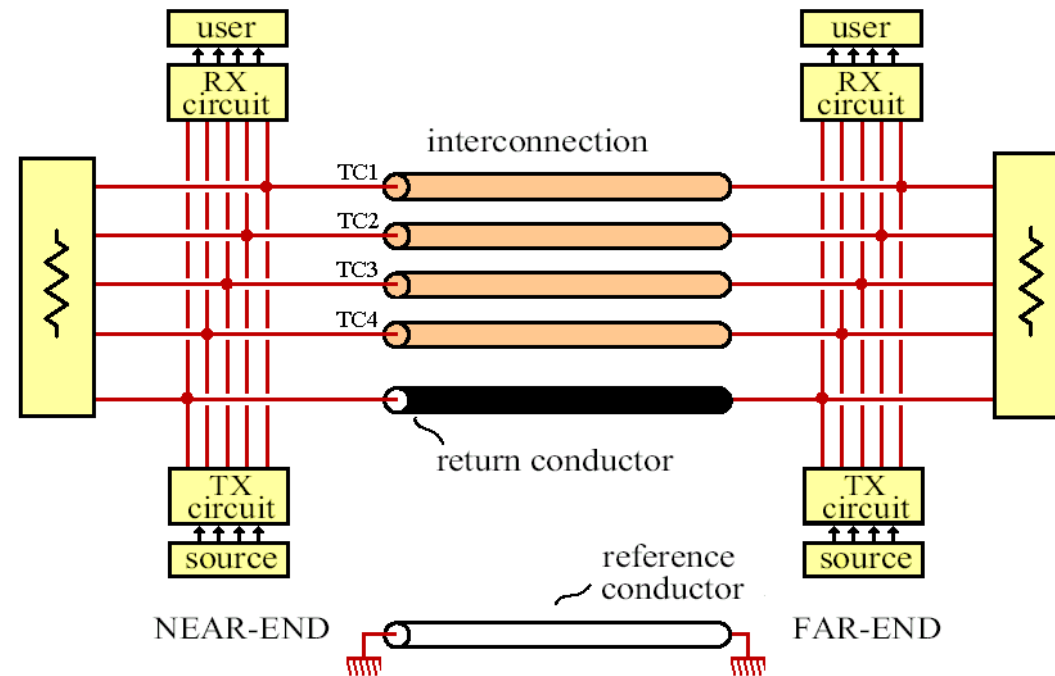


- ◆ A least one floating termination circuit is needed.
- ◆ The bidirectional CCMC architecture is compatible with full duplex signaling.

□ At this stage, we have identified four PDL architectures: PDL with VDCC, PDL using SW circuits, unidirectional PDL operating at CCMC and bidirectional PDL operating at CCMC.

❑ We can define four types of termination circuit.


❑ Type 0: no termination.

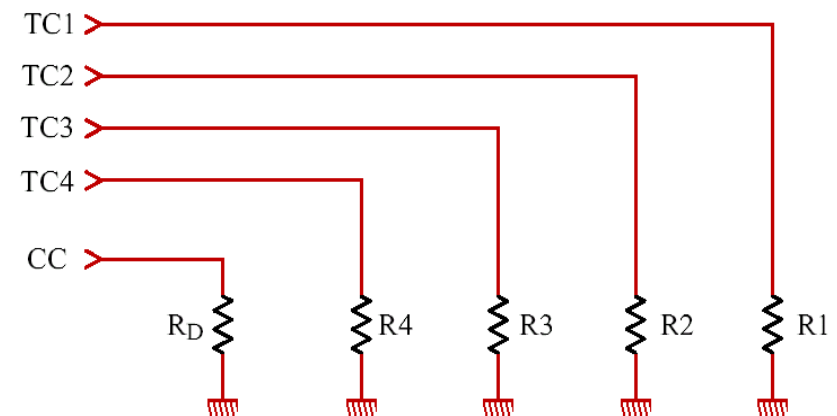❑ Type 1: termination circuit typically made of impedors connected to the GC or to a power supply node.




- ◆ Operates as intended only if the electric and magnetic fields of the signals are mainly located between the TCs and the GC.
- ◆ The GC belongs to the signal path: **this is a problem.**
- ◆ Not compatible with the CCMC architecture.

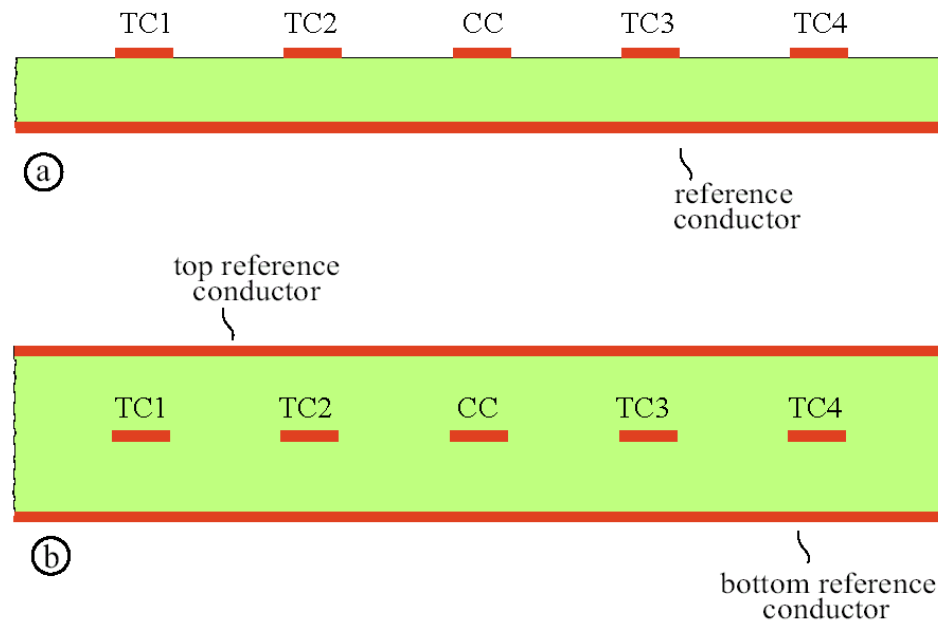□ Example of 2 interconnection-ground structures compatible with type 1 termination circuits:




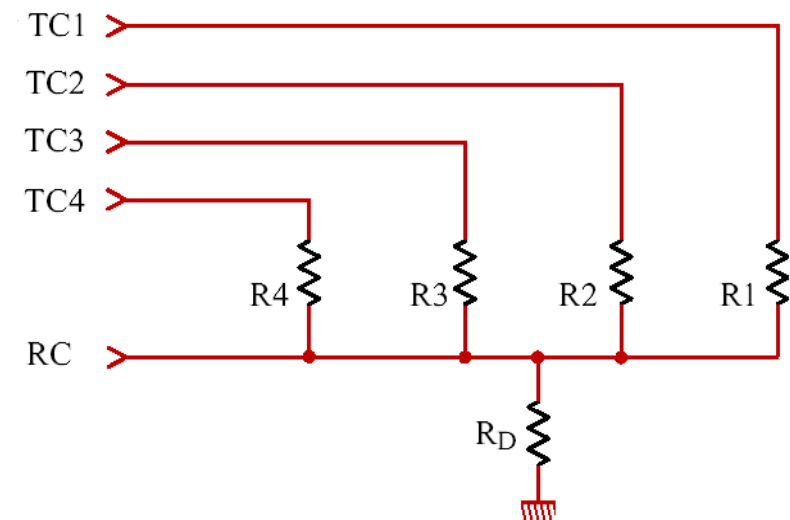□ Type 2: floating termination circuit made of impedors connected between a TC and the RC.







- ◆ Operates as intended only if the electric and magnetic fields of the signals are mainly located between the TCs and the RC.
- ◆ Does not degrade the reduction of external crosstalk.
- ◆ Compatible with the CCMC architecture.

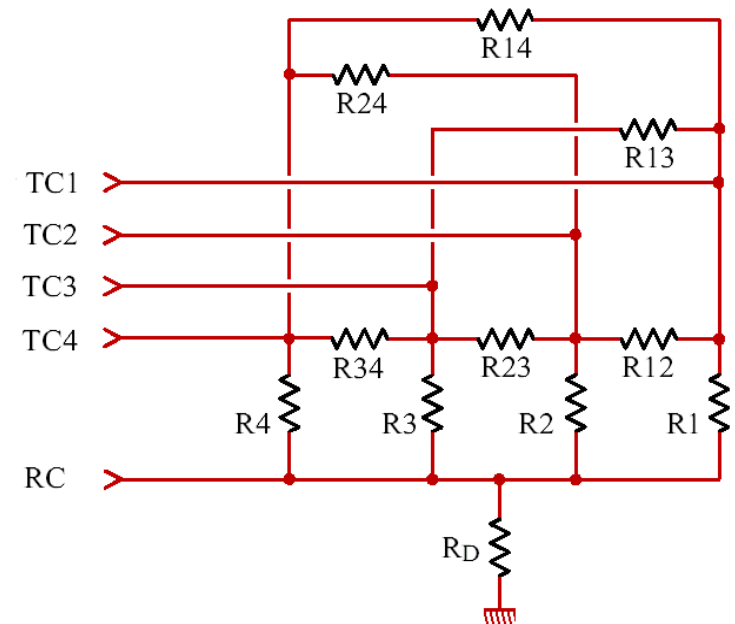□ Type 3: floating termination circuit comprising impedors connected between a TC and the RC and impedors connected between two TCs.



- ◆ Operates as intended only if the requirement for the second type is met and a variation of the ZXtalk method is used to reduce internal crosstalk.
- ◆ External crosstalk and internal crosstalk can be effectively reduced.
- ◆ Compatible with the CCMC architecture.

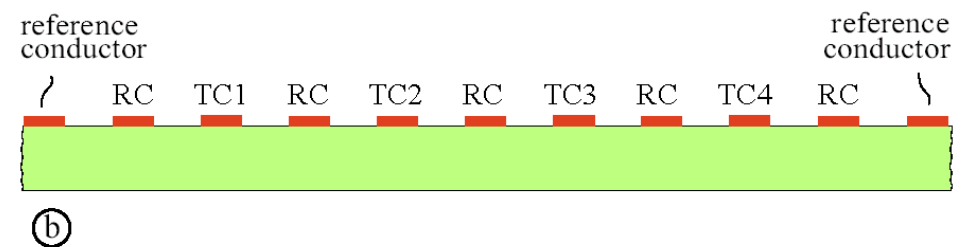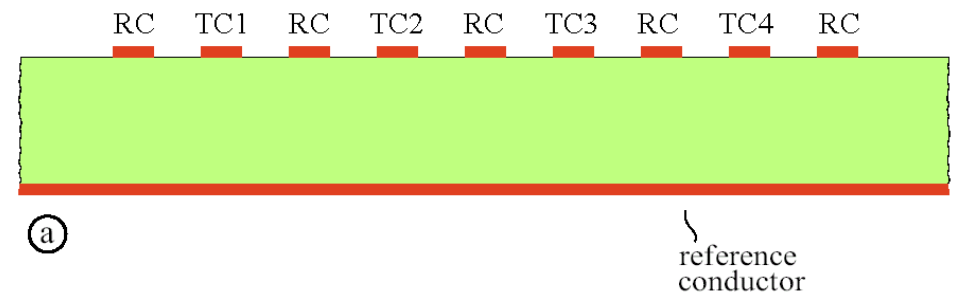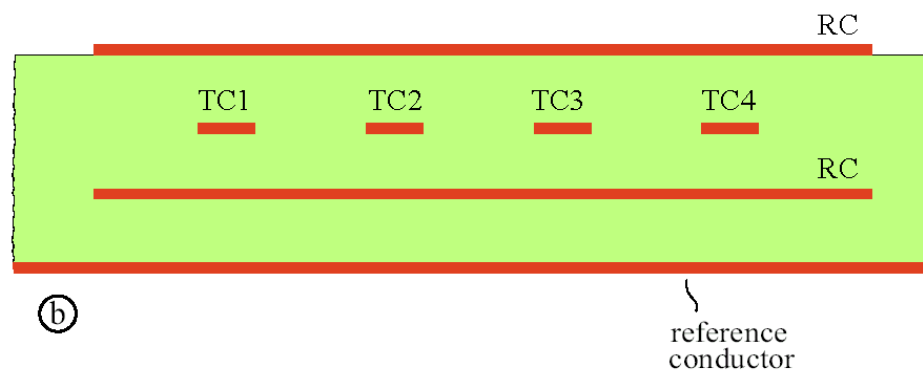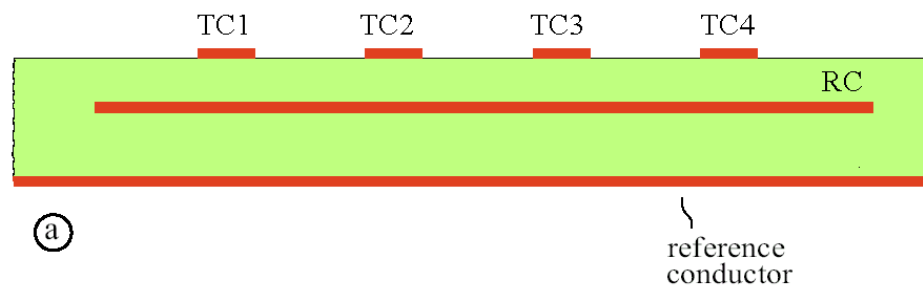□ Example of 4 interconnection-ground structures compatible with floating (i.e. type 2 or type 3) termination circuits:



□ An interconnection comprising n TCs and a CC or RC may be modeled as a $(n + 2)$ -conductor MTL, this MTL using natural voltages referenced to ground and natural currents as variables.

□ For such a model, we use, at a given abscissa z along the interconnection:

- ◆ for any integer α such that $1 \leq \alpha \leq n$, the natural current i_α ;
- ◆ the current flowing in the RC, denoted by i_{n+1} ;
- ◆ for any integer α such that $1 \leq \alpha \leq n$, the voltage between the TC number α and the GC, denoted by $v_{G\alpha}$;
- ◆ the voltage between the RC and the GC, denoted by v_{Gn+1} .

□ Later, we will also need:

- ◆ the common-mode current $i_{CM} = i_1 + \dots + i_{n+1}$;
- ◆ for any integer α such that $1 \leq \alpha \leq n$, the voltage between the TC number α and the RC, denoted by $v_{R\alpha}$ and given by $v_{R\alpha} = v_{G\alpha} - v_{Gn+1}$.

□ For the $(n + 2)$ -conductor MTL model, the telegrapher's equations are:

$$\begin{cases} \frac{d \mathbf{v}_G}{dz} = -\mathbf{Z}'_G \mathbf{i}_G \\ \frac{d \mathbf{i}_G}{dz} = -\mathbf{Y}'_G \mathbf{v}_G \end{cases} \quad (104)$$

where

\mathbf{v}_G is the column vector of the natural voltages referenced to ground, the entries of which are v_{G1}, \dots, v_{Gn+1} ;

\mathbf{i}_G is the column vector of the natural currents, the entries of which are i_{G1}, \dots, i_{Gn+1} ;

\mathbf{Z}'_G is the p.u.l. impedance matrix with respect to ground;

\mathbf{Y}'_G is the p.u.l. admittance matrix with respect to ground.

□ \mathbf{Z}'_G and \mathbf{Y}'_G are symmetric matrices of size $(n + 1) \times (n + 1)$.

□ The interconnection can also be described by an equivalent set of equations [79]:

$$\left\{ \begin{array}{l} \frac{d \mathbf{v}_R}{dz} = -\mathbf{Z}'_R \mathbf{i}_R + i_{MC} \mathbf{Z}'_E \\ \frac{d \mathbf{i}_R}{dz} = -\mathbf{Y}'_R \mathbf{v}_R - v_{Gn+1} \mathbf{Y}'_E \end{array} \right. \quad \text{and} \quad \left\{ \begin{array}{l} \frac{d v_{Gn+1}}{dz} = {}^t \mathbf{Z}'_E \mathbf{i}_R - i_{MC} Z'_{EE} \\ \frac{d i_{MC}}{dz} = -{}^t \mathbf{Y}'_E \mathbf{v}_R - v_{Gn+1} Y'_{EE} \end{array} \right. \quad (105)$$

where

\mathbf{v}_R is the column vector of the natural voltages referenced to the RC, the entries of which are v_{R1}, \dots, v_{Rn} ;

\mathbf{i}_R is the column vector of the natural currents i_1, \dots, i_n ;

\mathbf{Z}'_R is the p.u.l. impedance matrix with respect to the RC, of size $n \times n$;

\mathbf{Y}'_R is the p.u.l. admittance matrix with respect to the RC, of size $n \times n$;

\mathbf{Z}'_E is the p.u.l. transfer impedance vector, of size $n \times 1$;

\mathbf{Y}'_E is the p.u.l. transfer admittance vector, of size $n \times 1$;

Z'_{EE} is the p.u.l. external circuit impedance; and

Y'_{EE} is the p.u.l. external circuit admittance.

□ If the RC behaves as a good electromagnetic screen, norms of \mathbf{Z}'_E and \mathbf{Y}'_E are small, so that we may use the following approximation

$$\begin{cases} \frac{d \mathbf{v}_R}{dz} \approx -\mathbf{Z}'_R \mathbf{i}_R \\ \frac{d \mathbf{i}_R}{dz} \approx -\mathbf{Y}'_R \mathbf{v}_R \end{cases} \quad (106)$$

and

$$\begin{cases} \frac{d v_{Gn+1}}{dz} \approx -i_{MC} Z'_{EE} \\ \frac{d i_{MC}}{dz} \approx -v_{Gn+1} Y'_{EE} \end{cases} \quad (107)$$

□ By (106), the propagation of signals in the interconnection may be modeled as a propagation in a $(n + 1)$ -conductor MTL.




- ❑ The *ZXnoise method* is the combination of a floating termination circuit (type 2 or type 3 termination circuit) and an appropriate interconnection-ground structure [49] [62] [63] [78].
- ❑ The interconnection is proportioned such that all conductors other than the n TCs and the RC may be neglected when one models propagation in the interconnection, at the design stage.
- ❑ More precisely, the **design stage involves the assumption that the interconnection may be modeled with a sufficient accuracy as a $(n + 1)$ -conductor MTL.**
- ❑ This assumption leads to a floating termination circuit.
- ❑ A more accurate analysis of course requires a $(n + 2)$ -conductor MTL model.
- ❑ If a type 3 termination circuit is used, the designer combines the ZXnoise and ZXtalk methods.



□ Example 1: a compact 4-channel 0.03-m long PDL using single-ended line drivers, a RC grounded at the near-end (VDCC) and type 2 termination circuits.

The TCs are very close to each other, so that internal crosstalk is relatively high. However, echo is low and a good rejection of external crosstalk is obtained.

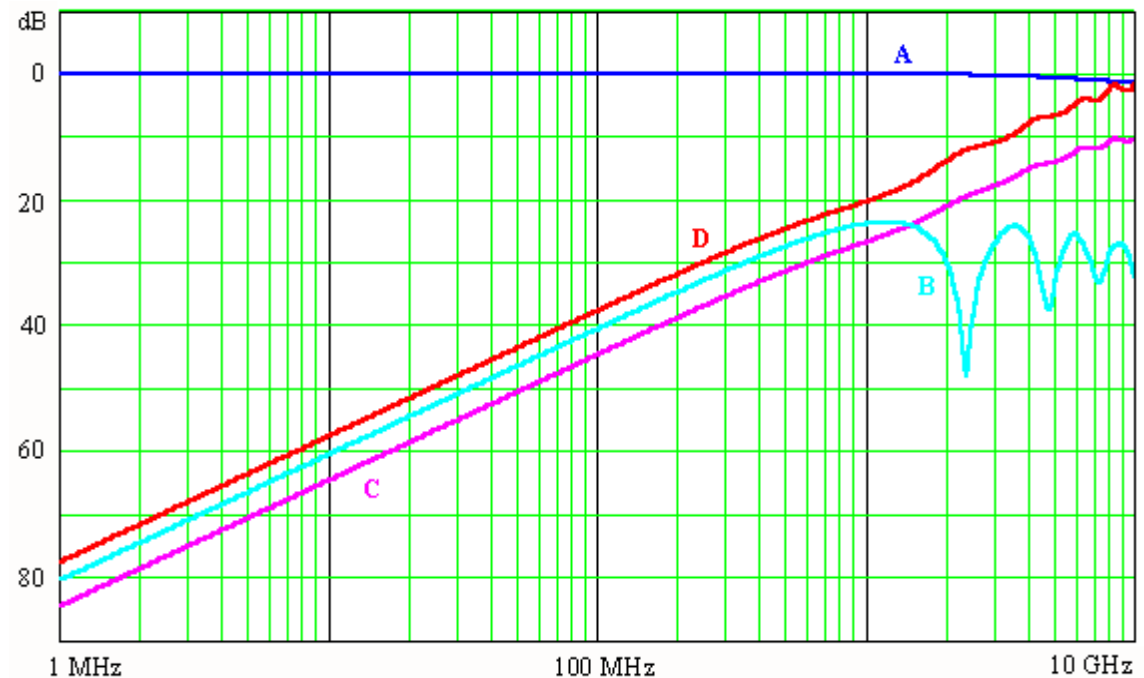
Attenuation of transmitted signal when TC1 is excited: curve A. NEXT loss on TC2 when TC1 is excited: curve B. FEXT loss on TC2 when TC1 is excited: curve C. Far-end external crosstalk loss on TC1 for ground bounce in the TX circuit: curve D. **Note that the far-end external crosstalk loss would be 0 dB for a single-ended link !**




❑ Example 2: Two compact 4-channel 0.3-m long PDLs using the same interconnection-ground structure, single-ended line drivers and VDCC.

The First PDL uses a type 2 termination circuit (ZXnoise method). The Second PDL is a ZXnoise + ZXtalk design (using a type 3 termination circuit).

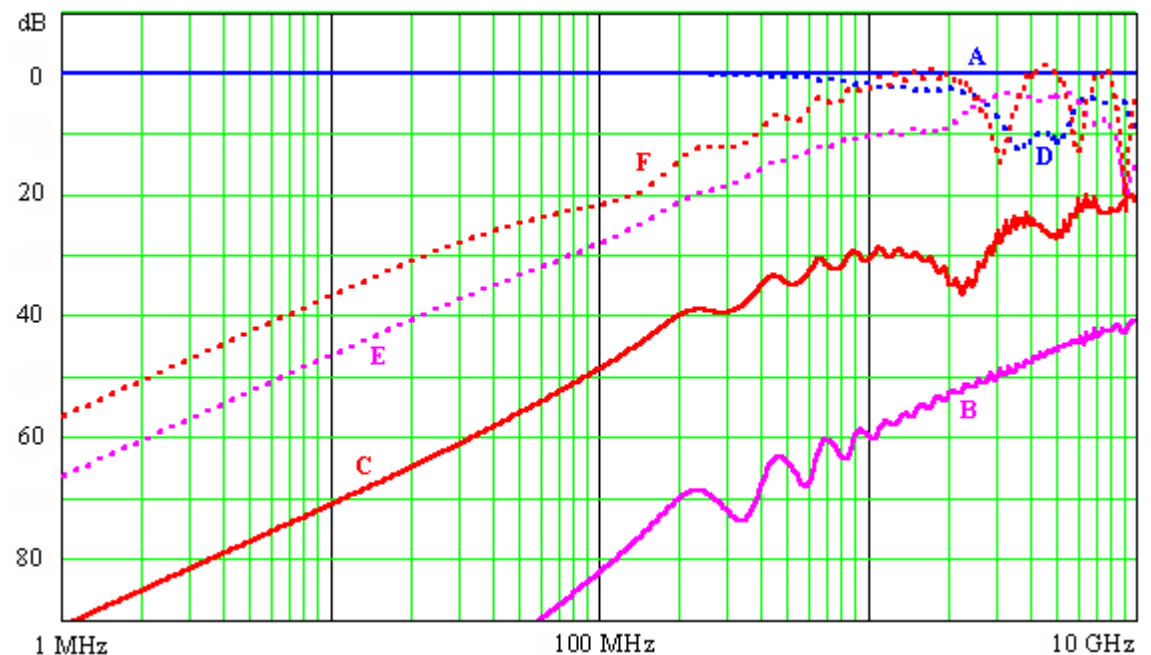When a type 3 termination circuit is used, in channel 2: attenuation of transmitted signal (curve A), lowest FEXT loss when channel 3 or 4 are excited (curve B), attenuation of ground bounce (curve C). When a type 2 termination circuit is used, in TC2: attenuation of transmitted signal (curve D), lowest FEXT loss (curve E), attenuation of ground bounce (curve F).



Time domain voltages in the PDL, measured on conductor 2 in the case of a type 2 termination circuit (First PDL) or on channel 2 in the case of a type 3 termination circuit (Second PDL), the stimulus being a 1V step having a 100 ps rise time. In the first PDL, conductor 1 is the one that produces the highest peak crosstalk voltage on conductor 2. In the second PDL, channel 4 is the one that produces the highest peak crosstalk voltage on channel 2.

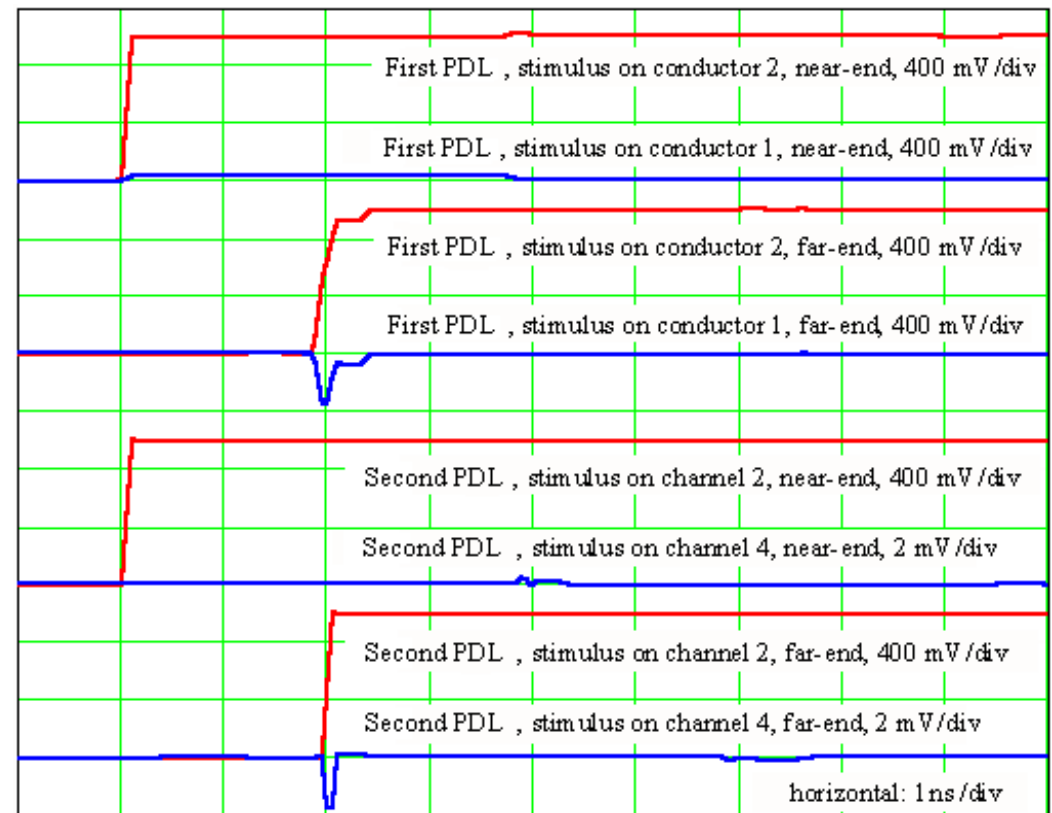

- From the presentation of pseudo-differential signaling, we see that:
 - ◆ pseudo-differential signaling effectively reduces external crosstalk using $m + 1$ conductors instead of $2m$ conductors for m differential links;
 - ◆ the ZXnoise method effectively reduces external crosstalk and echo;
 - ◆ the ZXnoise + ZXtalk combination also effectively reduces internal crosstalk.
- There are 12 pseudo-differential transmission schemes corresponding to the compatible combinations of an architecture and a type of termination circuit.

Termination circuit	Architecture of the PDL			
	VDCC (unidirectional)	SW circuit (bidirectional)	Unidirectional CCMC	Bidirectional CCMC
Type 0	Prior Art	New		
Type 1	Prior Art	New		
Type 2 (ZXnoise)	New	New	New	New
Type 3 (ZXnoise)	New	New	New	New



- ❑ Several authors have introduced other multichannel transmission schemes, in which one or more of the output signals of the RX circuit are mainly determined by the voltages between two TCs, sometimes with the addition of a code maintaining a constant current [25] [45] [68] [69] [72] [74].
- ❑ Even though some such transmission schemes are sometimes referred to as pseudo-differential, they have not been considered in this presentation.
- ❑ Suggested reading on pseudo-differential signaling [18] [23] [24] [26] [32] [40] [42] [46] [47] [48] [49] [54] [57] [58] [59] [60] [61] [62] [63] [64] [65] [66] [70] [71] [73] [75] [78] [79] [84].



Appendix: Inventions of Excem quoted in this tutorial

❑ Cross-reference:

Internal No.	Reference	Internal No.	Reference	Internal No.	Reference	Internal No.	Reference
P26	[27]	P36	[47]	P41	[59]	P46	[71]
P27	[28]	P37	[48]	P42	[60]	P47	[77]
P28	[29]	P38	[49]	P43	[62]	P48	[78]
P30	[41]	P39	[57]	P44	[63]	P49	[82]
P35	[46]	P40	[58]	P45	[70]		

❑ Inventions on the ZXtalk method (essential inventions in red):

ZXtalk method	Link	
	Not pseudo-differential	Pseudo-differential (ZXnoise + ZXtalk)
General	P26, P27, P47 , P39, P40, P42	P39, P40, P43, P48 , P42, P45, P46
Special	P28, P47 P30, P33, P36, P39, P40, P41, P42	P39, P40, P44, P48 P30, P33, P36, P41, P42, P45, P46

❑ Inventions on pseudo-differential signaling (essential inventions in red):

Termination circuit	Architecture of the PDL			
	VDCC (unidirectional)	SW circuit (bidirectional)	Unidirectional CCMC	Bidirectional CCMC
Type 0	Prior Art P39, P46	P37 P39, P46		
Type 1	Prior Art P39, P46	P37 P39, P46		
Type 2 (ZXnoise)	P35, P38, P48 P39, P41, P46	P35, P37, P38, P48 P39, P41, P46	P35, P36, P38, P48 P39, P41, P42, P46	
Type 3 (ZXnoise+ZXtalk)	P39, P40, P43, P44, P48 P30, P33, P41, P46	P39, P40, P43, P44, P45 P48 , P30, P33, P41, P46	P36, P39, P40, P42, P43, P44, P48 P30, P33, P41, P46	




Bibliography


- [1] L.A. Pipes, “Steady-State Analysis of Multiconductor Transmission Lines”, *Journal of Applied Physics*, vol. 12, pp. 782-799, Nov. 1941.
- [2] D.B. Jarvis, “The Effect of Interconnections on High-Speed Logic Circuits”, *IEEE Transactions on Electronic Computers*, pp. 476-487, Oct. 1963.
- [3] C.A. Desoer, “The Maximum Power Transfer Theorem for n -Ports”, *IEEE Trans. Circuit Theory*, vol. 20, No. 3, pp. 328-330, May 1973.
- [4] K.D. Marx, “Propagation Modes, Equivalent Circuits, and Characteristic Terminations for Multiconductor Transmission Lines with Inhomogeneous Dielectrics”, *IEEE Trans. on Microwave Theory Tech.*, vol. MTT-21, No. 7, pp. 450-457, July 1973.
- [5] C. R. Paul, “Efficient Numerical Computation of the Frequency Response of Cables Illuminated by an Electromagnetic Field”, *IEEE Trans. on Microwave Theory Tech*, vol.. MTT-22, No. 4, pp. 454-457, April 1974.
- [6] J. Chilo, T. Arnaud, “Coupling Effects in the Time Domain for an Interconnecting Bus in High-Speed GaAs Logic Circuits”, *IEEE Trans. Electron Devices*, vol. ED-31, No. 3, pp. 347-352, March 1984.
- [7] V. K. Tripathi, J.B. Rettig, “A SPICE Model for Multiple Coupled Microstrips and Other Transmission Lines”, *IEEE Trans. on Microwave Theory Tech.*, vol. MTT-33, No. 12, pp. 1513-1518, Dec. 1985.
- [8] R.A. Horn, C.R. Johnson, *Matrix analysis*, Cambridge: Cambridge University Press, 1985.
- [9] T.H. Nguyen, T.R. Scott, “Propagation over Multiple Parallel Transmission Lines Via Modes”, *IBM Technical Disclosure Bulletin*, vol. 32, No. 11, pp. 1-6, April 1990.
- [10] F. Broydé, E. Clavelier, F. Vaillant, S. Bigot, “Crosstalk and Field to Wire Coupling Problems: the SPICE Simulator Approach”, *Proc. 9th Int. Zurich Symposium and Technical Exhibition on Electromagnetic Compatibility*, pp. 23-28, 12-14 March, 1991.
- [11] J.P.K. Gilb, C.A. Balanis “Asymmetric, multi-conductor low-coupling structures for high-speed, high-density digital interconnects”, *IEEE Trans. on Microwave Theory Tech.*, vol. 39, No. 12, pp. 2100-2106, Dec. 1991.




- [12] F. Broydé, E. Clavelier, C. Hymowitz, “Simulating Crosstalk and Field to Wire coupling with a Spice Simulator”, *IEEE Circuits & Devices*, Vol. 8, No. 5, pp. 8-16, Sept. 1992.
- [13] B.K. Chan, T.R. Scott, *Modal propagation of information through a defined transmission medium*, United States patent No. 5,412,689 . Filed: 23 Dec. 1992.
- [14] C.R. Paul *Analysis of Multiconductor Transmission Lines*, New York, N.Y.: John Wiley & Sons, 1994.
- [15] G.-T. Lei, G.-W. Pan, B.K. Gilbert “Examination, Clarification and Simplification of Modal Decoupling Method for Multiconductor Transmission Lines”, *IEEE Trans. on Microwave Theory Tech.*, vol. 43, No. 9, pp. 2090-2100, Sept. 1995.
- [16] F. Broydé, E. Clavelier, L. Hoeft, “Comments on «A SPICE Model for Multiconductor Transmission Lines Excited by an Incident Electromagnetic Field»”, *IEEE Trans. Electromagn. Compat.*, Vol. 38, No. 1, pp. 104-108, Feb. 1996.
- [17] F.M. Tesche, M.V. Ianoz, T. Karlsson, *EMC Analysis Methods and Computational Models*, New York, N.Y.: John Wiley & Sons, 1997.
- [18] T. Frodsham, *Multi-agent pseudo-differential signaling scheme*, United States patent No. 6,195,395. Filed: March 18, 1998.
- [19] D.C. Mansur, *Eigen-mode encoding of signals in a data group*, United States patent No. 6,226,330. Filed: July 16, 1998.
- [20] Y. You, O.A. Palusinski, F. Szidarovszky, “New Matrix Algorithm for Calculating Diagonally Matched Impedance of Packaging Interconnecting Lines”, *IEEE Trans. on Microwave Theory Tech.*, vol. 47, No. 6, pp. 798-801, June 1999.
- [21] E.W. Weisstein, *CRC Concise Encyclopedia of Mathematics*, CRC Press, 1999.
- [22] *SPICELINE 2.23 with Telecom Line Predictor — User’s Guide*, document Excem 00012107B, March 2000.
- [23] S. Sidiropoulos, Y. Li, M.A. Horowitz, *Reducing coupled noise in pseudo-differential signaling systems*, United States patent No. 7,099,395. Filed 7 Nov. 2000.
- [24] S.Y. Borkar, M.B. Haycock, S.R. Mooney, A.K. Martin, J.T. Kennedy, *System for interchip communication*, United States patent No. 6,847,617. Filed: March 26, 2001.
- [25] A. Carusone, K. Farzan, D.A. Johns, “Differential signaling with a reduced number of signal paths”, *IEEE Trans. Circuits Syst. II: Express Briefs*, vol. 48, No. 3, pp. 294-300, March 2001.
- [26] S. Dabral, S.R. Mooney, T.Z. Schoenborn, S. Calvin, T. Frodsham, *Reference voltage distribution for multiload I/O systems*, United States patent No. 6,594,769. Filed 29 Apr. 2002.

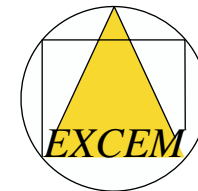

- [27] F. Broydé, E. Clavelier, *Method and device for transmission with reduced crosstalk*, French patent No. 03 00064, international application No. PCT/EP2003/015036 (WO 2004/062129), United States patents No. 7,167,019 and No. 7,362,130. Excem patent No. P26. First priority filed: 6 Jan. 2003.
- [28] F. Broydé, E. Clavelier, *Digital method and device for transmission with reduced crosstalk*, French patent No. 03 02814, international application No. PCT/EP2004/002382 (WO 2004/079941) and United States patent No. 7,477,069. Excem patent No. P27. First priority filed: 6 March 2003.
- [29] F. Broydé, E. Clavelier, *Method and device for transmission without crosstalk*, French patent No. 03 03087, international application No. PCT/EP2004/002383 (WO 2004/082168) and United States patent No. 7,408,426. Excem patent No. P28. First priority filed: 13 March 2003.
- [30] D.G. Kam, H. Lee, J. Kim, J. Kim, “A New Twisted Differential Line Structure on High-Speed Printed Circuit Boards to Enhance Immunity to Crosstalk and External Noise, *IEEE Microwave Wireless Compon. Lett.*, vol. 13, No. 9, pp. 411-413, Sept. 2003.
- [31] H. Johnson and M. Graham, *High-Speed Signal Propagation — Advanced Black Magic*, Prentice Hall PTR, 2003.
- [32] D.M. Dreps, A. Haridass, B.G. Truong, *Circuit for generating a tracking reference voltage*, United States patent No. 7,208,972. Filed 13 May 2004.
- [33] T. Ciamulski, W.K. Gwarek, “On Eliminating Crosstalk within Multiconductor Transmission Lines”, *IEEE Microwave Wireless Compon. Lett.*, vol. 14, No. 6, pp. 298-300, June 2004.
- [34] T. Ciamulski, W.K. Gwarek, “A Study of Feeding Options Aimed at Cancelling Crosstalk in Multiconductor Transmission Lines”, *2004 IEEE MTT-S International Microwave Symposium Digest*, vol. 3, pp. 1631-1634, 6-11 June 2004.
- [35] T. Ciamulski, W.K. Gwarek, “On a Possibility of Crosstalk-Free Propagation of Signals in Coupled Transmission Lines”, *EMC 2004 17th International Wroclaw Symposium and Exhibition on Electromagnetic Compatibility*, Wroclaw, paper H2, 29 June - 1 July 2004.
- [36] F. Broydé, E. Clavelier, “A New Interconnection Architecture for the Reduction of Crosstalk and Reflections”, *Technical Conferences Proceedings of the SAME 2004 Microelectronics Forum*, Session 5: Analog and electrical design, Oct. 6-7, 2004.

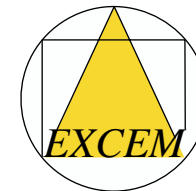


- [37] F. Broydé, “Clear as a Bell - Controlling crosstalk in uniform interconnections”, *IEEE Circuits and Devices Magazine*, Vol. 20, No. 6, pp. 29-37, Nov./Dec. 2004.
- [38] F. Broydé, E. Clavelier, “A New Method for the Reduction of Crosstalk and Echo in Multiconductor Interconnections”, *IEEE Trans. Circuits Syst. I*, vol. 52, No. 2, pp. 405-416, Feb. 2005.
- [39] F. Broydé, E. Clavelier, “A Modal Transmission Technique Providing a Large Reduction of Crosstalk and Echo”, *Proceedings of the 16th Int. Zurich Symposium on Electromagnetic Compatibility*, pp.341-346, 13-18 Feb. 2005.
- [40] D.M. Dreps, A. Haridass, B.G. Truong, J.D. Ziegelbein, *Reduced cross-talk signaling circuit and method*, United States patent No. 7,239,213. Filed 23 Aug. 2005.
- [41] F. Broydé, E. Clavelier, *Multiple-input and multiple-output amplifier*, French patent No. 06/00388, international application No. PCT/IB2006/003950 (WO 2007/083191) and United States patent No. 7,642,849. Excem patent No. P30. First priority filed: 17 Jan. 2006.
- [42] K.-I. Park, S.-J. Bae, S.-J. Jang, *Reference voltage generators for reducing and/or eliminating termination mismatch*, United States patent No. 7,403,040. First priority filed 10 May 2006.
- [43] F. Broydé, E. Clavelier, “Corrections to «A New Method for the Reduction of Crosstalk and Echo in Multiconductor Interconnections»”, *IEEE Trans. Circuits Syst. I*, vol. 53, No. 8, p. 1851, Aug. 2006.
- [44] F. Broydé, E. Clavelier, “A Simple Method for Transmission with Reduced Crosstalk and Echo”, *Proceedings of the 13th IEEE International Conference on Electronics, Circuits and Systems*, ICECS 2006, pp. 684-687, Dec. 10-13, 2006.
- [45] T. Wang, F. Yuan, “A New Current-Mode Incremental Signaling Scheme With Application to Gb/s Parallel Links”, *IEEE Trans. Circuits Syst. I: Regular Papers*, Vol. 54, No. 2, pp. 255-267, Feb. 2007.
- [46] F. Broydé, E. Clavelier, *Pseudo-differential interfacing device having a termination circuit*, French patent No. 07/04421, international application No. PCT/IB2008/051826 (WO 2008/155676) and United States patent No. 7,932,741. Excem patent No. P35. First priority filed: 21 June 2007.
- [47] F. Broydé, E. Clavelier, *Pseudo-differential interfacing device having a balancing circuit*, French patent No. 07/04889, international application No. PCT/IB2008/051942 (WO 2009/007864) and United States patent No. 7,952,380. Excem patent No. P36. First priority filed: 06 July 2007.

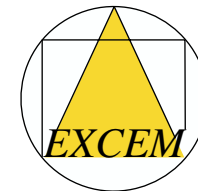


- [48] F. Broydé, E. Clavelier, *Pseudo-differential interfacing device having a switching circuit*, French patent No. 07/04949, international application No. PCT/IB2008/051982 (WO 2009/007866) and United States patent No. 7,834,648. Excem patent No. P37. First priority filed: 09 July 2007.
- [49] F. Broydé, E. Clavelier, *Method and device for pseudo-differential transmission*, French patent No. 07/05260 and international application No. PCT/IB2008/052102 (WO 2009/013644). Excem patent No. P38. First priority filed: 20 July 2007.
- [50] F. Broydé, E. Clavelier, “Crosstalk in Balanced Interconnections Used for Differential Signal Transmission”, *IEEE Trans. Circuits Syst. I: Regular Papers*, Vol. 54, No. 7, pp. 1562-1572, July 2007.
- [51] F. Broydé, E. Clavelier, “MIMO Series-Series Feedback Amplifiers”, *IEEE Trans. Circuits Syst. II: Express Briefs*, Vol. 54, No. 12, pp. 1037-1041, Dec. 2007.
- [52] F. Yuan, *CMOS current-mode circuits for data communications*, Springer, 2007.
- [53] T. Ciamulski, W.K. Gwarek, “Coupling Compensation Concept Applied to Crosstalk Cancelling in Multiconductor Transmission Lines”, *IEEE Trans. Electromagn Compat.*, vol. 50, No. 2, pp. 437-441, May 2008.
- [54] F. Broydé, E. Clavelier, “A new pseudo-differential transmission scheme for on-chip and on-board interconnections”, *Proc. of the CEM 08 Int. Symp. on Electromagnetic Compatibility* (14ème colloque international sur la compatibilité électromagnétique - CEM 08), Paris, session C7, May 2008.
- [55] Y. Choi, H. Braunisch, K. Aygün, P.D. Franzon, “Analysis of inter-bundle crosstalk in multimode signaling for high-density interconnects”, *Proc 58th IEEE Electronic Components and Technology Conference (ECTC)*, pp. 664-668, May 27-30, 2008.
- [56] H. Braunisch, K. Aygün, *Multimode signaling on decoupled input/output and power channels*, United States patent No. 7,816,779. Filed 2 July 2008.
- [57] F. Broydé, E. Clavelier, *Pseudo-differential receiving circuit*, French patent No. 08/03830 and international application No. PCT/IB2009/051053 (WO 2010/004442). Excem patent No. P39. First priority filed: 7 July 2008.
- [58] F. Broydé, E. Clavelier, *Multichannel interfacing device having a termination circuit*, French patent application No. 08/03876 and international application No. PCT/IB2009/051182 (WO 2010/004444). Excem patent No. P40. First priority filed: 8 July 2008.



- [59] F. Broydé, E. Clavelier, *Multiple-input and multiple-output amplifier having pseudo-differential inputs*, French patent application No. 08/03982, international application No. PCT/IB2009/051358 (WO 2010/004445) and United States patent No. 7,952,429. Excem patent No. P41. First priority filed: 11 July 2008.
- [60] F. Broydé, E. Clavelier, *Multichannel interfacing device having a balancing circuit*, French patent No. 08/03985 and international application No. PCT/IB2009/051557 (WO 2010/004448). Excem patent No. P42. First priority filed: 11 July 2008.
- [61] K.-I. Park, S.-J. Bae, S.-J. Jang, *Reference voltage generators for reducing and/or eliminating termination mismatch*, United States patent No. 7,768,298. First priority filed 17 July 2008.
- [62] F. Broydé, E. Clavelier, *Method for pseudo-differential transmission using modal electrical variables*, French patent No. 08/04429 and international application No. PCT/IB2009/052638 (WO 2010/015947). Excem patent No. P43. First priority filed: 4 Aug. 2008.
- [63] F. Broydé, E. Clavelier, *Method for pseudo-differential transmission using natural electrical variables*, French patent No. 08/04430 and international application No. PCT/IB2009/052645 (WO 2010/015948). Excem patent No. P44. First priority filed: 4 Aug. 2008.
- [64] F. Broydé, E. Clavelier, “Pseudo-differential links using a wide return conductor and a floating termination circuit”, *Proc. of the 2008 IEEE Int. Midwest Symposium on Circuits and Systems (MWSCAS)*, pp. 586-589, Aug. 10-13, 2008.
- [65] F. Broydé, G. Broydé, “Two pseudo-differential transmitting circuits producing a constant common-mode current”, *Proc. of the 2008 IEEE Int. Midwest Symposium on Circuits and Systems (MWSCAS)*, pp. 269-272, Aug. 10-13, 2008.
- [66] F. Broydé, E. Clavelier, “A pseudo-differential transmitting circuit causing reduced common-mode current variations”, *Proc. of the 15th IEEE Int. Conf. on Electronics, Circuits and Systems, ICECS 2008*, pp. 17-20, Aug. 31 - Sept. 3, 2008.
- [67] Y. Choi, C. Won, P.D. Franzon, H. Braunisch, K. Aygün, “Multimode Signaling on Non-Ideal Channels”, *Proc 17th IEEE Conf. on Electrical Performance of Electronic Packaging, EPEP 2008*, pp. 51-54, Oct. 27-29, 2008.
- [68] D. Oh, F. Ware, W.P. Kim, J.-H. Kim, J. Wilson, L. Luo, J. Kizer, R. Schmitt, C. Yuan and J. Eble, “Pseudo-differential signaling scheme based on 4b/6b multiwire code”, *Proc. of the IEEE 17th Topical Meeting on Electrical Performance of Electronic Packaging, EPEP 2008*, pp. 29-32, Oct. 2008.

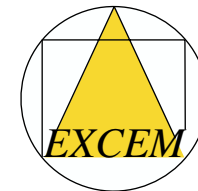

- [69] S.-K. Lee, D.-W. Jee, Y.Suh, H.-J. Park, J.-Y. Sim, “A 8 GByte/s transceiver with current-balanced pseudo-differential signaling for memory interface”, *Proc. 2008 IEEE Asian Solid-State Circuits Conference*, pp. 237-240, Nov. 2008.
- [70] F. Broydé, E. Clavelier, *Multichannel interfacing device having a switching circuit*, French patent No. 09/00042 and international application No. PCT/IB2009/055287 (WO 2010/079390). Excem patent No. P45. First priority filed: 8 Jan. 2009.
- [71] F. Broydé, E. Clavelier, *Transmission device using a plurality of elementary return conductors*, French patent application No. 09/00161 and international application No. PCT/IB2009/055295 (WO 2010/082093). Excem patent No. P46. First priority filed: 15 Jan. 2009.
- [72] D. Oh, F. Ware, J.-H. Kim, A. Abbasfar, J. Wilson, L. Luo, R. Schmitt, C. Yuan, “Pseudo-Differential Vector Signaling for Noise Reduction in Single-Ended Signaling Systems”, *Proc. DesignCon 2009*, Feb. 2009.
- [73] F. Broydé, E. Clavelier, “Echo-Free and Crosstalk-Free Transmission in Particular Interconnections”, *IEEE Microwave and Wireless Components Letters*, Vol. 19, No. 4, pp. 209-211, April 2009.
- [74] A. Hu, F. Yuan, “Intersignal Timing Skew Compensation of Parallel Links With Voltage-Mode Incremental Signaling”, *IEEE Trans. Circuits Syst. I: Regular Papers*, Vol. 56, No. 4, April 2009, pp. 773-783.
- [75] F. Broydé, E. Clavelier, “Modeling the interconnection of a pseudo-differential link using a wide return conductor”, *Proc. 13th IEEE Workshop on Signal Propagation on Interconnects, SPI 2009*, May 12-15, 2009.
- [76] F. Broydé, E. Clavelier, “Signal and noise analysis of an MIMO-SSFA”, *IEEE Trans. Circuits Syst. II: Express Briefs*, Vol. 56, No. 6, pp. 439-443, June 2009.
- [77] F. Broydé, E. Clavelier, *Method for transmission using a non-uniform interconnection*, French patent application No. 09/04610 and international application No. PCT/IB2010/051857. Excem patent No. P47. First priority filed: 28 Sept. 2009.
- [78] F. Broydé, E. Clavelier, *Method for pseudo-differential transmission using a non-uniform interconnection*, French patent application No. 09/04611 and international application No. PCT/IB2010/051863. Excem patent No. P48. First priority filed: 28 Sept. 2009.
- [79] F. Broydé, B. Démoulin, “Designing a ZXnoise Pseudo-Differential Link”, *Proc. IEEE 18th Topical Meeting on Electrical Performance of Electronic Packaging and Systems, EPEPS 2009*, Oct. 19-21, 2009.

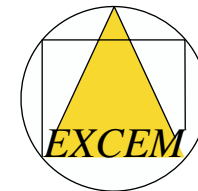

- [80] P. Milosevic, J.E. Schutt-Ainé, N.R. Shanbhag, “DSP-based Multimode Signaling for FEXT Reduction in Multi-Gbps Links”, *Proc. of the IEEE 18th Topical Meeting on Electrical Performance of Electronic Packaging and Systems, EPEPS 2009*, pp. 45-48, Oct 19-21, 2009.
- [81] S.H. Hall, H.L. Heck, *Advanced Signal Integrity for High-Speed Digital Designs*, John Wiley & Sons, 2009.
- [82] F. Broydé, E. Clavelier, *Balanced-input current-sensing differential amplifier*, French patent application No. 10/02662 and International application No. PCT/IB2011/052213. Excem patent No. P49. First priority filed: 25 June 2010.
- [83] Y. Choi, H. Braunisch, K. Aygun, P.D. Franzon, “Multimode transceiver for high-density interconnects: measurement and validation”, *Proc 60th IEEE Electronic Components and Technology Conference, ECTC 2010*, pp. 1733-1738, June 2010.
- [84] F. Broydé, E. Clavelier, “Multichannel Pseudo-Differential Links”, *Proc. of the 2010 IEEE Int. Symp. on Electromagnetic Compatibility, EMC 2010*, Vol. 2, pp. 305-310, July 2010.
- [85] P. Milosevic, J.E. Schutt-Aine, W.T. Beyene, “Crosstalk Mitigation of High-Speed Interconnects with Discontinuities Using Modal Signaling”, *Proc. 19th IEEE Int. Conf. on Electrical Performance of Electronic Packaging and Systems, EPEPS 2010*, Oct. 2010.
- [86] J. Lee, S. Lee, S. Nam, “Propagation Velocity Equalizer Circuit on Multi Microstrip Transmission Line Structure”, *Proc. of the 5th European Conference on Antenna and Propagation (EuCAP 2011)*, pp. 2475-2477, 11-15 April 2011.
- [87] J. Zerbe, B. Daly, L. Luo, W. Stonecypher, W. Dettloff, J.C. Eble, T. Stone, J. Ren, B. Leibowitz, M. Bucher, P. Satarzadeh, Q. Lin, Y. Lu, R. Kollipara, “A 5 Gb/s Link With Matched Source Synchronous and Common-Mode Clocking Techniques”, *IEEE J. Solid-State Circuits*, Vol. 46, No. 4, pp. 974-985, April 2011.
- [88] J. Lee, S. Lee, S. Nam, “A Crosstalk Reduction Technique for Microstrip MTL Using Mode Velocity Equalization”, *IEEE Trans. Electromagn. Compat.*, Vol. 53, No. 2, pp. 366-371, May 2011.
- [89] F. Broydé, E. Clavelier, “Two New Balanced-Input Current-Mode Differential Receivers for High-Speed Links”, *Proc. of the 9th IEEE Int. NEWCAS Conference, NEWCAS 2011*, pp. 329-332, June 2011.
- [90] F. Broydé, E. Clavelier, “A Computation of the High-Frequency Per-Unit-Length Resistance Matrix of a Multiconductor Interconnections”, *Proc. of the 10th Int. Symp. on Electromagnetic Compatibility, EMC Europe 2011*, York, UK, pp. 351-356, Sept. 26-30, 2011.



- [91] J. Ren, D. Oh, R. Kollipara, B. Tsang, Y. Lu, J. Zerbe, Q. Lin, “System Design Considerations for a 5 Gb/s Source-Synchronous Link with Common-Mode Clocking”, *Proc. IEEE 20th Conference on Electrical Performance of Electronic Packaging and Systems, EPEPS 2011*, San Jose, pp. 143-146, Oct. 23-26, 2011.
- [92] P. Milosevic, J.E. Schutt-Aine, “Design of a 12 Gb/s Transceiver for High-Density Links with Discontinuities using Modal Signaling”, *Proc. IEEE 20th Conference on Electrical Performance of Electronic Packaging and Systems, EPEPS 2011*, San Jose, pp. 215-218, Oct. 23-26, 2011.



Annexes

Annex A: Computation of the eigenvectors and the characteristic impedance matrix of a first interconnection

pages A-1 to A-8

Annex B: Computation of the eigenvectors and the characteristic impedance matrix of a second interconnection

pages B-1 to B-8

Annex A: Computation of the eigenvectors and the characteristic impedance matrix

Authors: Frédéric Broydé and Evelyne Clavelier.

Prepared with Mathcad 2000 professional (Mathcad is a registered trademark of its owner).

date: 21 Oct. 2010

© Excem 2010

File: Worksheet A of Tutorial v2a.mcd

1) DEFINITION OF THE MULTICONDUCTOR TRANSMISSION LINE PARAMETERS

(we use some data of Worksheet F of Sem 33 Chap 2 v2a.mcd)

ORIGIN := 1 n := 8

$$L0 := \begin{pmatrix} 531.38820 & 302.97719 & 196.55629 & 135.03626 & 96.48416 & 71.25132 & 54.28431 & 42.80081 \\ 302.97719 & 516.34491 & 294.94966 & 191.73007 & 132.03762 & 94.67304 & 70.33634 & 54.28431 \\ 196.55629 & 294.94966 & 512.06563 & 292.43477 & 190.27838 & 131.34951 & 94.67304 & 71.25132 \\ 135.03626 & 191.73007 & 292.43477 & 510.69139 & 291.81073 & 190.27838 & 132.03762 & 96.48416 \\ 96.48416 & 132.03762 & 190.27838 & 291.81073 & 510.69139 & 292.43477 & 191.73007 & 135.03626 \\ 71.25132 & 94.67304 & 131.34951 & 190.27838 & 292.43477 & 512.06563 & 294.94966 & 196.55629 \\ 54.28431 & 70.33634 & 94.67304 & 132.03762 & 191.73007 & 294.94966 & 516.34491 & 302.97719 \\ 42.80081 & 54.28431 & 71.25132 & 96.48416 & 135.03626 & 196.55629 & 302.97719 & 531.38820 \end{pmatrix} \cdot 10^{-9} \quad \text{H/m}$$

$\text{norme}(L0 - L0^T) = 0$

$$C := \begin{pmatrix} 51.180621 & -23.614594 & -2.461115 & -0.774112 & -0.348395 & -0.203589 & -0.144816 & -0.167753 \\ -23.614594 & 63.054502 & -22.474417 & -2.105959 & -0.615859 & -0.258450 & -0.146408 & -0.144816 \\ -2.461115 & -22.474417 & 63.174880 & -22.436402 & -2.089464 & -0.607986 & -0.258450 & -0.203589 \\ -0.774112 & -2.105959 & -22.436402 & 63.186687 & -22.432098 & -2.089464 & -0.615859 & -0.348395 \\ -0.348395 & -0.615859 & -2.089464 & -22.432098 & 63.186687 & -22.436402 & -2.105959 & -0.774112 \\ -0.203589 & -0.258450 & -0.607986 & -2.089464 & -22.436402 & 63.174880 & -22.474417 & -2.461115 \\ -0.144816 & -0.146408 & -0.258450 & -0.615859 & -2.105959 & -22.474417 & 63.054502 & -23.614594 \\ -0.167753 & -0.144816 & -0.203589 & -0.348395 & -0.774112 & -2.461115 & -23.614594 & 51.180621 \end{pmatrix} \cdot 10^{-12} \quad \text{F/m}$$

$\text{norme}(C - C^T) = 0$

2) DETERMINATION OF ASSOCIATED EIGENVECTORS

$$D1 := \text{eigenvals}(10^{18} \cdot C \cdot L0)$$

$$D2 := \text{eigenvals}(10^{18} \cdot L0 \cdot C)$$

vectors of the eigenvalues

$$i := 1..n$$

$$j := 1..n$$

$$D1 = \begin{pmatrix} 25.35799 \\ 20.63546 \\ 18.54192 \\ 17.51615 \\ 16.12124 \\ 16.52110 \\ 16.91569 \\ 16.26602 \end{pmatrix}$$

$$D2 = \begin{pmatrix} 25.35799 \\ 20.63546 \\ 18.54192 \\ 17.51615 \\ 16.12124 \\ 16.91569 \\ 16.52110 \\ 16.26602 \end{pmatrix}$$

BEWARE ! the order of the eigenvalues is NOT identical in D1 and D2, we choose the order of D1

Propagation velocity of the eigenmodes

$$c_{ij} := \frac{1}{\sqrt{10^{-18} \cdot D1_i}}$$

$$c_i = \begin{pmatrix} 1.986 \times 10^8 \\ 2.201 \times 10^8 \\ 2.322 \times 10^8 \\ 2.389 \times 10^8 \\ 2.491 \times 10^8 \\ 2.460 \times 10^8 \\ 2.431 \times 10^8 \\ 2.479 \times 10^8 \end{pmatrix}$$

m/s

$$\text{Munsurc}_{ij,j} := 0$$

$$\text{Munsurc}_{ij,i} := \frac{1}{c_{ij}}$$

Definition of the change of variables for the currents, i.e. transition matrix from modal currents to natural currents (matrix T)

$$T_{i,j} := (\text{eigenvec}(10^{18} \cdot C \cdot L0, D1_j))_i$$

$$T = \begin{pmatrix} 0.41534 & -0.54029 & -0.50948 & -0.44297 & 0.10052 & 0.28765 & -0.36808 & -0.19704 \\ 0.32623 & -0.37448 & -0.18359 & 0.09610 & -0.27671 & -0.48644 & 0.35047 & 0.45949 \\ 0.32954 & -0.24578 & 0.17435 & 0.47288 & 0.41565 & 0.10000 & 0.34421 & -0.46202 \\ 0.33537 & -0.08629 & 0.41992 & 0.26632 & -0.49047 & 0.41308 & -0.35102 & 0.19128 \\ 0.33537 & 0.08629 & 0.41992 & -0.26632 & 0.49047 & -0.41308 & -0.35102 & 0.19128 \\ 0.32954 & 0.24578 & 0.17435 & -0.47288 & -0.41565 & -0.10000 & 0.34421 & -0.46202 \\ 0.32623 & 0.37448 & -0.18359 & -0.09610 & 0.27671 & 0.48644 & 0.35047 & 0.45949 \\ 0.41534 & 0.54029 & -0.50948 & 0.44297 & -0.10052 & -0.28765 & -0.36808 & -0.19704 \end{pmatrix}$$

Definition of the change of variables for the voltages, i.e. transition matrix from modal voltages to natural voltages (matrix S)

$ck := 10^{-10}$ arbitrary constant

$$S := ck \cdot C^{-1} \cdot T$$

$$S = \begin{pmatrix} 2.054301 & -1.895924 & -1.155304 & -0.702251 & 0.083579 & 0.290674 & -0.444683 & -0.174771 \\ 2.274451 & -1.724031 & -0.462953 & 0.247219 & -0.275695 & -0.609739 & 0.559119 & 0.498559 \\ 2.414446 & -1.187700 & 0.576552 & 0.976135 & 0.405178 & 0.114345 & 0.532082 & -0.483689 \\ 2.484387 & -0.422463 & 1.314582 & 0.543835 & -0.480948 & 0.500468 & -0.515995 & 0.206748 \\ 2.484387 & 0.422463 & 1.314582 & -0.543835 & 0.480948 & -0.500468 & -0.515995 & 0.206748 \\ 2.414446 & 1.187700 & 0.576552 & -0.976135 & -0.405178 & -0.114345 & 0.532082 & -0.483689 \\ 2.274451 & 1.724031 & -0.462953 & -0.247219 & 0.275695 & 0.609739 & 0.559119 & 0.498559 \\ 2.054301 & 1.895924 & -1.155304 & 0.702251 & -0.083579 & -0.290674 & -0.444683 & -0.174771 \end{pmatrix}$$

3) CHARACTERISTIC IMPEDANCE MATRIX

modal characteristic impedances
(for the associated eigenvectors)

$$zC_i := \frac{1}{ck \cdot ci_i}$$

$$zC = \begin{pmatrix} 50.357 \\ 45.426 \\ 43.060 \\ 41.852 \\ 40.151 \\ 40.646 \\ 41.129 \\ 40.331 \end{pmatrix}$$

Ω

modal characteristic impedance matrix

$$Z_{mc} := \text{diag}(zC)$$

characteristic impedance matrix

$$Z_c := S \cdot Z_{mc} \cdot T^{-1}$$

$$Z_c = \begin{pmatrix} 116.390 & 61.099 & 37.310 & 24.238 & 16.431 & 11.564 & 8.446 & 6.438 \\ 61.099 & 113.169 & 59.453 & 36.347 & 23.653 & 16.084 & 11.390 & 8.446 \\ 37.310 & 59.453 & 112.326 & 58.969 & 36.072 & 23.525 & 16.084 & 11.564 \\ 24.238 & 36.347 & 58.969 & 112.066 & 58.852 & 36.072 & 23.653 & 16.431 \\ 16.431 & 23.653 & 36.072 & 58.852 & 112.066 & 58.969 & 36.347 & 24.238 \\ 11.564 & 16.084 & 23.525 & 36.072 & 58.969 & 112.326 & 59.453 & 37.310 \\ 8.446 & 11.390 & 16.084 & 23.653 & 36.347 & 59.453 & 113.169 & 61.099 \\ 6.438 & 8.446 & 11.564 & 16.431 & 24.238 & 37.310 & 61.099 & 116.390 \end{pmatrix} \quad \Omega$$

control of the equations for computing the characteristic impedance matrix:

$$S \cdot \text{Munsurci}^{-1} \cdot S^{-1} \cdot L0 = \begin{pmatrix} 116.390 & 61.099 & 37.310 & 24.238 & 16.431 & 11.564 & 8.446 & 6.438 \\ 61.099 & 113.169 & 59.453 & 36.347 & 23.653 & 16.084 & 11.390 & 8.446 \\ 37.310 & 59.453 & 112.326 & 58.969 & 36.072 & 23.525 & 16.084 & 11.564 \\ 24.238 & 36.347 & 58.969 & 112.066 & 58.852 & 36.072 & 23.653 & 16.431 \\ 16.431 & 23.653 & 36.072 & 58.852 & 112.066 & 58.969 & 36.347 & 24.238 \\ 11.564 & 16.084 & 23.525 & 36.072 & 58.969 & 112.326 & 59.453 & 37.310 \\ 8.446 & 11.390 & 16.084 & 23.653 & 36.347 & 59.453 & 113.169 & 61.099 \\ 6.438 & 8.446 & 11.564 & 16.431 & 24.238 & 37.310 & 61.099 & 116.390 \end{pmatrix}$$

$$C^{-1} \cdot T \cdot \text{Munsurci} \cdot T^{-1} = \begin{pmatrix} 116.390 & 61.099 & 37.310 & 24.238 & 16.431 & 11.564 & 8.446 & 6.438 \\ 61.099 & 113.169 & 59.453 & 36.347 & 23.653 & 16.084 & 11.390 & 8.446 \\ 37.310 & 59.453 & 112.326 & 58.969 & 36.072 & 23.525 & 16.084 & 11.564 \\ 24.238 & 36.347 & 58.969 & 112.066 & 58.852 & 36.072 & 23.653 & 16.431 \\ 16.431 & 23.653 & 36.072 & 58.852 & 112.066 & 58.969 & 36.347 & 24.238 \\ 11.564 & 16.084 & 23.525 & 36.072 & 58.969 & 112.326 & 59.453 & 37.310 \\ 8.446 & 11.390 & 16.084 & 23.653 & 36.347 & 59.453 & 113.169 & 61.099 \\ 6.438 & 8.446 & 11.564 & 16.431 & 24.238 & 37.310 & 61.099 & 116.390 \end{pmatrix}$$

$$S \cdot \text{Munsurci} \cdot S^{-1} \cdot C^{-1} = \begin{pmatrix} 116.390 & 61.099 & 37.310 & 24.238 & 16.431 & 11.564 & 8.446 & 6.438 \\ 61.099 & 113.169 & 59.453 & 36.347 & 23.653 & 16.084 & 11.390 & 8.446 \\ 37.310 & 59.453 & 112.326 & 58.969 & 36.072 & 23.525 & 16.084 & 11.564 \\ 24.238 & 36.347 & 58.969 & 112.066 & 58.852 & 36.072 & 23.653 & 16.431 \\ 16.431 & 23.653 & 36.072 & 58.852 & 112.066 & 58.969 & 36.347 & 24.238 \\ 11.564 & 16.084 & 23.525 & 36.072 & 58.969 & 112.326 & 59.453 & 37.310 \\ 8.446 & 11.390 & 16.084 & 23.653 & 36.347 & 59.453 & 113.169 & 61.099 \\ 6.438 & 8.446 & 11.564 & 16.431 & 24.238 & 37.310 & 61.099 & 116.390 \end{pmatrix}$$

$$L0 \cdot T \cdot \text{Munsurci}^{-1} \cdot T^{-1} = \begin{pmatrix} 116.390 & 61.099 & 37.310 & 24.238 & 16.431 & 11.564 & 8.446 & 6.438 \\ 61.099 & 113.169 & 59.453 & 36.347 & 23.653 & 16.084 & 11.390 & 8.446 \\ 37.310 & 59.453 & 112.326 & 58.969 & 36.072 & 23.525 & 16.084 & 11.564 \\ 24.238 & 36.347 & 58.969 & 112.066 & 58.852 & 36.072 & 23.653 & 16.431 \\ 16.431 & 23.653 & 36.072 & 58.852 & 112.066 & 58.969 & 36.347 & 24.238 \\ 11.564 & 16.084 & 23.525 & 36.072 & 58.969 & 112.326 & 59.453 & 37.310 \\ 8.446 & 11.390 & 16.084 & 23.653 & 36.347 & 59.453 & 113.169 & 61.099 \\ 6.438 & 8.446 & 11.564 & 16.431 & 24.238 & 37.310 & 61.099 & 116.390 \end{pmatrix}$$

4) MATCHED LOADS

$$Z_c^{-1} = \begin{pmatrix} 0.012 & -6.073 \times 10^{-3} & -6.123 \times 10^{-4} & -2.154 \times 10^{-4} & -1.085 \times 10^{-4} & -6.856 \times 10^{-5} & -5.111 \times 10^{-5} & -6.325 \times 10^{-5} \\ -6.073 \times 10^{-3} & 0.015 & -5.767 \times 10^{-3} & -5.064 \times 10^{-4} & -1.629 \times 10^{-4} & -7.643 \times 10^{-5} & -4.724 \times 10^{-5} & -5.111 \times 10^{-5} \\ -6.123 \times 10^{-4} & -5.767 \times 10^{-3} & 0.015 & -5.756 \times 10^{-3} & -5.011 \times 10^{-4} & -1.602 \times 10^{-4} & -7.643 \times 10^{-5} & -6.856 \times 10^{-5} \\ -2.154 \times 10^{-4} & -5.064 \times 10^{-4} & -5.756 \times 10^{-3} & 0.015 & -5.754 \times 10^{-3} & -5.011 \times 10^{-4} & -1.629 \times 10^{-4} & -1.085 \times 10^{-4} \\ -1.085 \times 10^{-4} & -1.629 \times 10^{-4} & -5.011 \times 10^{-4} & -5.754 \times 10^{-3} & 0.015 & -5.756 \times 10^{-3} & -5.064 \times 10^{-4} & -2.154 \times 10^{-4} \\ -6.856 \times 10^{-5} & -7.643 \times 10^{-5} & -1.602 \times 10^{-4} & -5.011 \times 10^{-4} & -5.756 \times 10^{-3} & 0.015 & -5.767 \times 10^{-3} & -6.123 \times 10^{-4} \\ -5.111 \times 10^{-5} & -4.724 \times 10^{-5} & -7.643 \times 10^{-5} & -1.629 \times 10^{-4} & -5.064 \times 10^{-4} & -5.767 \times 10^{-3} & 0.015 & -6.073 \times 10^{-3} \\ -6.325 \times 10^{-5} & -5.111 \times 10^{-5} & -6.856 \times 10^{-5} & -1.085 \times 10^{-4} & -2.154 \times 10^{-4} & -6.123 \times 10^{-4} & -6.073 \times 10^{-3} & 0.012 \end{pmatrix} \quad S$$

$$R_{i,j} := \frac{-1}{(Z_c^{-1})_{i,j}}$$

$$R_{i,i} := \frac{1}{\sum_{j=1}^n (Z_c^{-1})_{i,j}}$$

Values of the resistances of a network of resistors having an impedance matrix equal to Z_c , presented as a matrix (the diagonal entries are the values of the grounded resistors).

$$R = \begin{pmatrix} 205.831 & 164.674 & 1.633 \times 10^3 & 4.643 \times 10^3 & 9.215 \times 10^3 & 1.459 \times 10^4 & 1.956 \times 10^4 & 1.581 \times 10^4 \\ 164.674 & 373.546 & 173.403 & 1.975 \times 10^3 & 6.140 \times 10^3 & 1.308 \times 10^4 & 2.117 \times 10^4 & 1.956 \times 10^4 \\ 1.633 \times 10^3 & 173.403 & 407.954 & 173.740 & 1.996 \times 10^3 & 6.243 \times 10^3 & 1.308 \times 10^4 & 1.459 \times 10^4 \\ 4.643 \times 10^3 & 1.975 \times 10^3 & 173.740 & 418.071 & 173.784 & 1.996 \times 10^3 & 6.140 \times 10^3 & 9.215 \times 10^3 \\ 9.215 \times 10^3 & 6.140 \times 10^3 & 1.996 \times 10^3 & 173.784 & 418.071 & 173.740 & 1.975 \times 10^3 & 4.643 \times 10^3 \\ 1.459 \times 10^4 & 1.308 \times 10^4 & 6.243 \times 10^3 & 1.996 \times 10^3 & 173.740 & 407.954 & 173.403 & 1.633 \times 10^3 \\ 1.956 \times 10^4 & 2.117 \times 10^4 & 1.308 \times 10^4 & 6.140 \times 10^3 & 1.975 \times 10^3 & 173.403 & 373.546 & 164.674 \\ 1.581 \times 10^4 & 1.956 \times 10^4 & 1.459 \times 10^4 & 9.215 \times 10^3 & 4.643 \times 10^3 & 1.633 \times 10^3 & 164.674 & 205.831 \end{pmatrix} \Omega$$

5) ORTHOGONALITY OF ASSOCIATED EIGENVECTORS

$$S \cdot S^T = \begin{pmatrix} 9.962 & 7.766 & 5.775 & 4.303 & 3.254 & 2.508 & 1.977 & 1.604 \\ 7.766 & 9.430 & 7.388 & 5.547 & 4.166 & 3.173 & 2.467 & 1.977 \\ 5.775 & 7.388 & 9.220 & 7.277 & 5.487 & 4.138 & 3.173 & 2.508 \\ 4.303 & 5.547 & 7.277 & 9.165 & 7.253 & 5.487 & 4.166 & 3.254 \\ 3.254 & 4.166 & 5.487 & 7.253 & 9.165 & 7.277 & 5.547 & 4.303 \\ 2.508 & 3.173 & 4.138 & 5.487 & 7.277 & 9.220 & 7.388 & 5.775 \\ 1.977 & 2.467 & 3.173 & 4.166 & 5.547 & 7.388 & 9.430 & 7.766 \\ 1.604 & 1.977 & 2.508 & 3.254 & 4.303 & 5.775 & 7.766 & 9.962 \end{pmatrix}$$

$$T \cdot T^T = \begin{pmatrix} 1.1874 & 0.0015 & 0.0063 & 0.0150 & 0.0187 & 0.0185 & 0.0175 & 0.0254 \\ 0.0015 & 0.9368 & -0.0423 & -0.0101 & 0.0045 & 0.0100 & 0.0114 & 0.0175 \\ 0.0063 & -0.0423 & 0.9377 & -0.0409 & -0.0101 & 0.0041 & 0.0100 & 0.0185 \\ 0.0150 & -0.0101 & -0.0409 & 0.9382 & -0.0410 & -0.0101 & 0.0045 & 0.0187 \\ 0.0187 & 0.0045 & -0.0101 & -0.0410 & 0.9382 & -0.0409 & -0.0101 & 0.0150 \\ 0.0185 & 0.0100 & 0.0041 & -0.0101 & -0.0409 & 0.9377 & -0.0423 & 0.0063 \\ 0.0175 & 0.0114 & 0.0100 & 0.0045 & -0.0101 & -0.0423 & 0.9368 & 0.0015 \\ 0.0254 & 0.0175 & 0.0185 & 0.0187 & 0.0150 & 0.0063 & 0.0015 & 1.1874 \end{pmatrix}$$

Thus, the column-vectors of S (eigen-voltages) are not orthogonal, and the column-vectors of T (eigen-currents) are not orthogonal.

6) MODAL INDUCTANCE MATRIX AND MODAL CAPACITANCE MATRIX, FOR ASSOCIATED EIGENVECTORS

$$L_m := S^{-1} \cdot L_0 \cdot T$$

$$C_m := T^{-1} \cdot C \cdot S$$

$$10^9 L_m = \begin{pmatrix} 253.580 & 4.144 \times 10^{-14} & -1.425 \times 10^{-14} & -1.868 \times 10^{-14} & 1.865 \times 10^{-15} & -9.632 \times 10^{-15} & 2.242 \times 10^{-14} & 2.630 \times 10^{-15} \\ 7.461 \times 10^{-14} & 206.355 & -2.740 \times 10^{-15} & -1.724 \times 10^{-14} & 6.420 \times 10^{-15} & 1.527 \times 10^{-14} & 1.767 \times 10^{-15} & 3.221 \times 10^{-15} \\ -5.558 \times 10^{-14} & 2.882 \times 10^{-15} & 185.419 & -2.416 \times 10^{-14} & -5.492 \times 10^{-15} & -4.199 \times 10^{-15} & 7.819 \times 10^{-15} & -1.985 \times 10^{-14} \\ -9.002 \times 10^{-14} & 7.063 \times 10^{-15} & -3.810 \times 10^{-15} & 175.161 & 2.113 \times 10^{-14} & 5.256 \times 10^{-15} & 1.709 \times 10^{-15} & 4.110 \times 10^{-15} \\ 2.012 \times 10^{-14} & -5.549 \times 10^{-15} & 1.588 \times 10^{-14} & 1.786 \times 10^{-14} & 161.212 & 3.096 \times 10^{-14} & 2.227 \times 10^{-14} & 4.156 \times 10^{-15} \\ 5.023 \times 10^{-14} & -7.112 \times 10^{-15} & -7.566 \times 10^{-15} & 1.637 \times 10^{-15} & 9.008 \times 10^{-15} & 165.211 & 3.187 \times 10^{-14} & 1.583 \times 10^{-14} \\ 6.744 \times 10^{-14} & 1.087 \times 10^{-14} & 2.054 \times 10^{-14} & -1.762 \times 10^{-14} & -1.087 \times 10^{-15} & 1.020 \times 10^{-14} & 169.157 & 1.754 \times 10^{-14} \\ -5.079 \times 10^{-14} & 3.738 \times 10^{-14} & -2.568 \times 10^{-14} & -1.411 \times 10^{-14} & 1.052 \times 10^{-14} & 2.797 \times 10^{-14} & 3.299 \times 10^{-14} & 162.660 \end{pmatrix} \quad \text{nH/m}$$

$$10^{12} C_m = \begin{pmatrix} 100 & -2.031 \times 10^{-14} & 1.002 \times 10^{-14} & 2.112 \times 10^{-15} & -3.549 \times 10^{-15} & 8.423 \times 10^{-15} & 1.208 \times 10^{-15} & 1.04 \times 10^{-14} \\ -2.667 \times 10^{-14} & 100 & 1.805 \times 10^{-15} & 9.49 \times 10^{-16} & -4.554 \times 10^{-16} & 3.399 \times 10^{-15} & -4.195 \times 10^{-15} & 1.54 \times 10^{-16} \\ 3.556 \times 10^{-15} & -1.184 \times 10^{-14} & 100 & 5.186 \times 10^{-15} & 3.411 \times 10^{-15} & 7.134 \times 10^{-15} & -5.636 \times 10^{-15} & 1.153 \times 10^{-14} \\ 3.775 \times 10^{-14} & 1.247 \times 10^{-14} & 1.079 \times 10^{-14} & 100 & -4.045 \times 10^{-15} & -2.608 \times 10^{-15} & 9.185 \times 10^{-15} & -9.26 \times 10^{-15} \\ -2.154 \times 10^{-14} & -2.146 \times 10^{-15} & -3.452 \times 10^{-15} & 1.085 \times 10^{-16} & 100 & -7.198 \times 10^{-15} & 3.846 \times 10^{-15} & -1.016 \times 10^{-14} \\ -1.251 \times 10^{-14} & 4.651 \times 10^{-15} & 4.396 \times 10^{-15} & -1.749 \times 10^{-14} & -2.807 \times 10^{-15} & 100 & -5.786 \times 10^{-15} & -1.322 \times 10^{-14} \\ -2.574 \times 10^{-14} & -1.388 \times 10^{-14} & -1.531 \times 10^{-14} & 1.494 \times 10^{-14} & 2.89 \times 10^{-15} & -4.734 \times 10^{-15} & 100 & 5.916 \times 10^{-15} \\ 1.822 \times 10^{-14} & 2.758 \times 10^{-15} & 2.206 \times 10^{-14} & -1.423 \times 10^{-14} & -1.159 \times 10^{-14} & -1.328 \times 10^{-14} & -9.23 \times 10^{-16} & 100 \end{pmatrix} \quad \text{pF/m}$$

As expected, L_m and C_m are diagonal matrices, within the accuracy of our computation. Here C_m is

$$10^{12} \text{ck-identity}(n) = \begin{pmatrix} 100 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 100 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 100 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 100 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 100 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 100 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 100 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 100 \end{pmatrix} \quad \text{pF/m}$$

7) MODAL CHARACTERISTIC IMPEDANCE MATRIX, FOR BIORTHONORMAL EIGENVECTORS

$$Z_{mc} := \text{diag}(c_i) \cdot T^T \cdot L_0 \cdot T$$

$$Z_{mc} = \begin{pmatrix} 324.707 & 1.600 \times 10^{-14} & 2.132 \times 10^{-14} & 4.545 \times 10^{-16} & -1.662 \times 10^{-14} & -1.006 \times 10^{-16} & 4.386 \times 10^{-14} & 4.533 \times 10^{-15} \\ 2.935 \times 10^{-14} & 181.553 & -1.962 \times 10^{-14} & -4.343 \times 10^{-14} & 1.242 \times 10^{-14} & 3.046 \times 10^{-14} & 5.426 \times 10^{-15} & -1.509 \times 10^{-15} \\ 1.950 \times 10^{-14} & -2.335 \times 10^{-14} & 114.207 & -3.102 \times 10^{-14} & -8.240 \times 10^{-18} & -2.320 \times 10^{-15} & 1.004 \times 10^{-14} & -4.305 \times 10^{-14} \\ -2.021 \times 10^{-14} & -4.805 \times 10^{-14} & -2.759 \times 10^{-14} & 78.788 & 1.016 \times 10^{-14} & 2.057 \times 10^{-15} & 3.634 \times 10^{-16} & 5.609 \times 10^{-15} \\ -2.125 \times 10^{-14} & 1.213 \times 10^{-14} & 1.395 \times 10^{-15} & 9.188 \times 10^{-15} & 39.267 & 2.394 \times 10^{-14} & 5.023 \times 10^{-15} & -2.359 \times 10^{-14} \\ -1.211 \times 10^{-15} & 2.854 \times 10^{-14} & -2.963 \times 10^{-15} & 1.894 \times 10^{-15} & 2.408 \times 10^{-14} & 48.644 & 5.093 \times 10^{-15} & 2.283 \times 10^{-14} \\ 5.125 \times 10^{-14} & 9.272 \times 10^{-16} & 8.773 \times 10^{-15} & 2.068 \times 10^{-15} & 2.918 \times 10^{-15} & 3.946 \times 10^{-15} & 59.546 & 1.262 \times 10^{-14} \\ 3.545 \times 10^{-15} & -1.064 \times 10^{-15} & -4.801 \times 10^{-14} & 2.408 \times 10^{-15} & -2.332 \times 10^{-14} & 1.946 \times 10^{-14} & 1.275 \times 10^{-14} & 42.472 \end{pmatrix} \quad \Omega$$

In this example, Z_{mc} is a diagonal matrix, within the accuracy of our computation.
We note that Z_{mc} is different in section 3 and in section 7.

8) MODAL INDUCTANCE MATRIX AND MODAL CAPACITANCE MATRIX, FOR BIORTHONORMAL EIGENVECTORS

$$L_m := T^T \cdot L_0 \cdot T$$

$$C_m := T^{-1} \cdot C \cdot (T^{-1})^T$$

$$10^9 L_m = \begin{pmatrix} 1.635 \times 10^3 & 1.381 \times 10^{-13} & 1.073 \times 10^{-13} & -3.588 \times 10^{-14} & -1.217 \times 10^{-13} & -4.291 \times 10^{-15} & 1.756 \times 10^{-13} & 1.886 \times 10^{-14} \\ 7.491 \times 10^{-14} & 824.728 & -9.175 \times 10^{-14} & -2.120 \times 10^{-13} & 5.101 \times 10^{-14} & 1.589 \times 10^{-13} & -1.839 \times 10^{-14} & 2.617 \times 10^{-15} \\ 1.044 \times 10^{-13} & -7.941 \times 10^{-14} & 491.780 & -1.048 \times 10^{-13} & -1.650 \times 10^{-14} & -7.290 \times 10^{-15} & 5.081 \times 10^{-14} & -2.023 \times 10^{-13} \\ -3.553 \times 10^{-14} & -1.998 \times 10^{-13} & -1.172 \times 10^{-13} & 329.746 & 4.044 \times 10^{-14} & 5.477 \times 10^{-15} & 1.965 \times 10^{-15} & 1.640 \times 10^{-14} \\ -9.223 \times 10^{-14} & 5.066 \times 10^{-14} & 7.593 \times 10^{-17} & 3.546 \times 10^{-14} & 157.663 & 9.741 \times 10^{-14} & 1.459 \times 10^{-14} & -8.741 \times 10^{-14} \\ -8.327 \times 10^{-15} & 1.405 \times 10^{-13} & -1.665 \times 10^{-14} & 1.018 \times 10^{-14} & 9.787 \times 10^{-14} & 197.718 & 2.192 \times 10^{-14} & 8.884 \times 10^{-14} \\ 2.212 \times 10^{-13} & 2.003 \times 10^{-16} & 3.467 \times 10^{-14} & 3.315 \times 10^{-15} & 2.408 \times 10^{-14} & 1.398 \times 10^{-14} & 244.906 & 5.111 \times 10^{-14} \\ 1.510 \times 10^{-14} & -6.921 \times 10^{-15} & -1.934 \times 10^{-13} & 1.474 \times 10^{-14} & -9.384 \times 10^{-14} & 8.847 \times 10^{-14} & 4.211 \times 10^{-14} & 171.293 \end{pmatrix} \quad \text{nH/m}$$

$$10^{12} \cdot C_m = \begin{pmatrix} 15.508 & -3.295 \times 10^{-15} & -4.422 \times 10^{-16} & -3.410 \times 10^{-15} & 3.831 \times 10^{-17} & 7.541 \times 10^{-15} & -2.624 \times 10^{-15} & 3.093 \times 10^{-15} \\ -3.701 \times 10^{-15} & 25.021 & 2.773 \times 10^{-15} & 1.177 \times 10^{-14} & -8.526 \times 10^{-15} & -9.900 \times 10^{-15} & -4.224 \times 10^{-16} & -1.647 \times 10^{-16} \\ -6.409 \times 10^{-16} & 1.892 \times 10^{-15} & 37.704 & 1.144 \times 10^{-14} & 1.904 \times 10^{-15} & 6.926 \times 10^{-15} & -8.489 \times 10^{-15} & 4.172 \times 10^{-14} \\ -2.699 \times 10^{-15} & 1.063 \times 10^{-14} & 1.169 \times 10^{-14} & 53.120 & -4.637 \times 10^{-15} & -3.911 \times 10^{-15} & 6.848 \times 10^{-15} & -1.407 \times 10^{-14} \\ -1.347 \times 10^{-15} & -9.571 \times 10^{-15} & 1.539 \times 10^{-15} & -5.944 \times 10^{-15} & 102.251 & -5.048 \times 10^{-14} & -3.976 \times 10^{-15} & 4.703 \times 10^{-14} \\ 8.307 \times 10^{-15} & -9.552 \times 10^{-15} & 8.964 \times 10^{-15} & -4.823 \times 10^{-15} & -4.906 \times 10^{-14} & 83.559 & -5.401 \times 10^{-15} & -4.648 \times 10^{-14} \\ -2.580 \times 10^{-15} & -1.466 \times 10^{-15} & -8.872 \times 10^{-15} & 7.046 \times 10^{-15} & -4.360 \times 10^{-16} & -4.062 \times 10^{-15} & 69.070 & -1.454 \times 10^{-14} \\ 8.539 \times 10^{-16} & 3.708 \times 10^{-16} & 4.264 \times 10^{-14} & -1.471 \times 10^{-14} & 4.269 \times 10^{-14} & -4.578 \times 10^{-14} & -1.673 \times 10^{-14} & 94.960 \end{pmatrix} \quad \text{pF/m}$$

In this example, L_m and C_m are diagonal matrices, within the accuracy of our computation. We note that L_m and C_m are different in section 6 and in section 8.

[Back to the link "Annex A" of § 7](#)

Annex B: Computation of the eigenvectors and the characteristic impedance matrix

Authors: Frédéric Broydé and Evelyne Clavelier.

Prepared with Mathcad 2000 professional (Mathcad is a registered trademark of its owner).

date: 21 Oct. 2010

© Excem 2010

File: Worksheet B of Tutorial v2a.mcd

1) DEFINITION OF THE MULTICONDUCTOR TRANSMISSION LINE PARAMETERS

(we use some data of Worksheet N of Sem 33 Chap 2 v2a.mcd)

$$\begin{aligned}
 &L0 := \begin{pmatrix} 446.404 & 220.552 & 120.338 & 67.269 & 37.881 & 21.415 & 12.19 & 7.099 \\ 220.552 & 432.448 & 213.654 & 116.608 & 65.225 & 36.801 & 20.936 & 12.19 \\ 120.338 & 213.654 & 429.05 & 211.844 & 115.666 & 64.819 & 36.801 & 21.415 \\ 67.269 & 116.608 & 211.844 & 428.134 & 211.454 & 115.666 & 65.225 & 37.881 \\ 37.881 & 65.225 & 115.666 & 211.454 & 428.134 & 211.844 & 116.608 & 67.269 \\ 21.415 & 36.801 & 64.819 & 115.666 & 211.844 & 429.05 & 213.654 & 120.338 \\ 12.19 & 20.936 & 36.801 & 65.225 & 116.608 & 213.654 & 432.448 & 220.552 \\ 7.099 & 12.19 & 21.415 & 37.881 & 67.269 & 120.338 & 220.552 & 446.404 \end{pmatrix} \cdot 10^{-9} \quad \text{H/m} \\
 &\text{ORIGIN} := 1 \quad n := 8 \\
 &\epsilon_0 := 8.854188 \cdot 10^{-12} \quad \text{F/m} \quad \mu_0 := 4 \cdot \pi \cdot 10^{-7} \quad \text{H/m} \\
 &\text{norme}(L0 - L0^T) = 0 \\
 &\epsilon_r := 2.8 \quad C := \epsilon_r \epsilon_0 \mu_0 L0^{-1} \\
 &10^{12} C = \begin{pmatrix} 93.415 & -45.995 & -2.952 & -0.61 & -0.141 & -0.033 & -7.907 \times 10^{-3} & -2.178 \times 10^{-3} \\ -45.995 & 118.313 & -44.538 & -2.653 & -0.541 & -0.124 & -0.03 & -7.907 \times 10^{-3} \\ -2.952 & -44.538 & 118.408 & -44.519 & -2.649 & -0.54 & -0.124 & -0.033 \\ -0.61 & -2.653 & -44.519 & 118.412 & -44.517 & -2.649 & -0.541 & -0.141 \\ -0.141 & -0.541 & -2.649 & -44.517 & 118.412 & -44.519 & -2.653 & -0.61 \\ -0.033 & -0.124 & -0.54 & -2.649 & -44.519 & 118.408 & -44.538 & -2.952 \\ -7.907 \times 10^{-3} & -0.03 & -0.124 & -0.541 & -2.653 & -44.538 & 118.313 & -45.995 \\ -2.178 \times 10^{-3} & -7.907 \times 10^{-3} & -0.033 & -0.141 & -0.61 & -2.952 & -45.995 & 93.415 \end{pmatrix} \quad \text{pF/m}
 \end{aligned}$$

2) DETERMINATION OF ASSOCIATED EIGENVECTORS

$$i := 1..n \quad j := 1..n$$

In this worksheet, we use the *a priori* knowledge concerning completely degenerate interconnections.

$$D1_i := \epsilon_r \epsilon_0 \mu_0$$

Propagation velocity of the eigenmodes

$$c_{ij} := \frac{1}{\sqrt{D1_i}}$$

$$c_i = \begin{pmatrix} 1.792 \times 10^8 \\ 1.792 \times 10^8 \\ 1.792 \times 10^8 \\ 1.792 \times 10^8 \\ 1.792 \times 10^8 \\ 1.792 \times 10^8 \\ 1.792 \times 10^8 \\ 1.792 \times 10^8 \end{pmatrix} \quad \text{m/s}$$

$$\text{Munsur}c_{ij,j} := 0$$

$$\text{Munsur}c_{ij,i} := \frac{1}{c_{ij}}$$

Definition of the change of variables for the currents, i.e. transition matrix from modal currents to natural currents (matrix T)

Here, we can use $T := \text{identity}(n)$

$$T = \begin{pmatrix} 1.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 \\ 0.00000 & 1.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 \\ 0.00000 & 0.00000 & 1.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 \\ 0.00000 & 0.00000 & 0.00000 & 1.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 \\ 0.00000 & 0.00000 & 0.00000 & 0.00000 & 1.00000 & 0.00000 & 0.00000 & 0.00000 \\ 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 1.00000 & 0.00000 & 0.00000 \\ 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 1.00000 & 0.00000 \\ 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 0.00000 & 1.00000 \end{pmatrix}$$

Definition of the change of variables for the voltages, i.e. transition matrix from modal voltages to natural voltages (matrix S)

$ck := 10^{-10}$ arbitrary constant

$$S := ck \cdot C^{-1} \cdot T$$

$$S = \begin{pmatrix} 1.432885 & 0.707937 & 0.386266 & 0.215923 & 0.121592 & 0.068739 & 0.039128 & 0.022787 \\ 0.707937 & 1.388089 & 0.685795 & 0.374293 & 0.209362 & 0.118125 & 0.067201 & 0.039128 \\ 0.386266 & 0.685795 & 1.377182 & 0.679985 & 0.371269 & 0.208059 & 0.118125 & 0.068739 \\ 0.215923 & 0.374293 & 0.679985 & 1.374242 & 0.678733 & 0.371269 & 0.209362 & 0.121592 \\ 0.121592 & 0.209362 & 0.371269 & 0.678733 & 1.374242 & 0.679985 & 0.374293 & 0.215923 \\ 0.068739 & 0.118125 & 0.208059 & 0.371269 & 0.679985 & 1.377182 & 0.685795 & 0.386266 \\ 0.039128 & 0.067201 & 0.118125 & 0.209362 & 0.374293 & 0.685795 & 1.388089 & 0.707937 \\ 0.022787 & 0.039128 & 0.068739 & 0.121592 & 0.215923 & 0.386266 & 0.707937 & 1.432885 \end{pmatrix}$$

3) CHARACTERISTIC IMPEDANCE MATRIX

modal characteristic impedances
(for the associated eigenvectors)

$$zC_i := \frac{1}{ck \cdot ci_i}$$

$$zC = \begin{pmatrix} 55.816 \\ 55.816 \\ 55.816 \\ 55.816 \\ 55.816 \\ 55.816 \\ 55.816 \\ 55.816 \end{pmatrix}$$

Ω

modal characteristic impedance matrix

$$Z_{mc} := \text{diag}(zC)$$

characteristic impedance matrix

$$Z_c := S \cdot Z_{mc} \cdot T^{-1}$$

$$Z_c = \begin{pmatrix} 79.978 & 39.514 & 21.560 & 12.052 & 6.787 & 3.837 & 2.184 & 1.272 \\ 39.514 & 77.477 & 38.278 & 20.892 & 11.686 & 6.593 & 3.751 & 2.184 \\ 21.560 & 38.278 & 76.869 & 37.954 & 20.723 & 11.613 & 6.593 & 3.837 \\ 12.052 & 20.892 & 37.954 & 76.705 & 37.884 & 20.723 & 11.686 & 6.787 \\ 6.787 & 11.686 & 20.723 & 37.884 & 76.705 & 37.954 & 20.892 & 12.052 \\ 3.837 & 6.593 & 11.613 & 20.723 & 37.954 & 76.869 & 38.278 & 21.560 \\ 2.184 & 3.751 & 6.593 & 11.686 & 20.892 & 38.278 & 77.477 & 39.514 \\ 1.272 & 2.184 & 3.837 & 6.787 & 12.052 & 21.560 & 39.514 & 79.978 \end{pmatrix}$$

Ω

control of the equations for computing the characteristic impedance matrix:

$$S \cdot \text{Munsurci}^{-1} \cdot S^{-1} \cdot L0 = \begin{pmatrix} 79.978 & 39.514 & 21.560 & 12.052 & 6.787 & 3.837 & 2.184 & 1.272 \\ 39.514 & 77.477 & 38.278 & 20.892 & 11.686 & 6.593 & 3.751 & 2.184 \\ 21.560 & 38.278 & 76.869 & 37.954 & 20.723 & 11.613 & 6.593 & 3.837 \\ 12.052 & 20.892 & 37.954 & 76.705 & 37.884 & 20.723 & 11.686 & 6.787 \\ 6.787 & 11.686 & 20.723 & 37.884 & 76.705 & 37.954 & 20.892 & 12.052 \\ 3.837 & 6.593 & 11.613 & 20.723 & 37.954 & 76.869 & 38.278 & 21.560 \\ 2.184 & 3.751 & 6.593 & 11.686 & 20.892 & 38.278 & 77.477 & 39.514 \\ 1.272 & 2.184 & 3.837 & 6.787 & 12.052 & 21.560 & 39.514 & 79.978 \end{pmatrix}$$

$$C^{-1} \cdot T \cdot \text{Munsurci} \cdot T^{-1} = \begin{pmatrix} 79.978 & 39.514 & 21.560 & 12.052 & 6.787 & 3.837 & 2.184 & 1.272 \\ 39.514 & 77.477 & 38.278 & 20.892 & 11.686 & 6.593 & 3.751 & 2.184 \\ 21.560 & 38.278 & 76.869 & 37.954 & 20.723 & 11.613 & 6.593 & 3.837 \\ 12.052 & 20.892 & 37.954 & 76.705 & 37.884 & 20.723 & 11.686 & 6.787 \\ 6.787 & 11.686 & 20.723 & 37.884 & 76.705 & 37.954 & 20.892 & 12.052 \\ 3.837 & 6.593 & 11.613 & 20.723 & 37.954 & 76.869 & 38.278 & 21.560 \\ 2.184 & 3.751 & 6.593 & 11.686 & 20.892 & 38.278 & 77.477 & 39.514 \\ 1.272 & 2.184 & 3.837 & 6.787 & 12.052 & 21.560 & 39.514 & 79.978 \end{pmatrix}$$

$$S \cdot \text{Munsurci} \cdot S^{-1} \cdot C^{-1} = \begin{pmatrix} 79.978 & 39.514 & 21.560 & 12.052 & 6.787 & 3.837 & 2.184 & 1.272 \\ 39.514 & 77.477 & 38.278 & 20.892 & 11.686 & 6.593 & 3.751 & 2.184 \\ 21.560 & 38.278 & 76.869 & 37.954 & 20.723 & 11.613 & 6.593 & 3.837 \\ 12.052 & 20.892 & 37.954 & 76.705 & 37.884 & 20.723 & 11.686 & 6.787 \\ 6.787 & 11.686 & 20.723 & 37.884 & 76.705 & 37.954 & 20.892 & 12.052 \\ 3.837 & 6.593 & 11.613 & 20.723 & 37.954 & 76.869 & 38.278 & 21.560 \\ 2.184 & 3.751 & 6.593 & 11.686 & 20.892 & 38.278 & 77.477 & 39.514 \\ 1.272 & 2.184 & 3.837 & 6.787 & 12.052 & 21.560 & 39.514 & 79.978 \end{pmatrix}$$

$$L0 \cdot T \cdot \text{Munsurci}^{-1} \cdot T^{-1} = \begin{pmatrix} 79.978 & 39.514 & 21.560 & 12.052 & 6.787 & 3.837 & 2.184 & 1.272 \\ 39.514 & 77.477 & 38.278 & 20.892 & 11.686 & 6.593 & 3.751 & 2.184 \\ 21.560 & 38.278 & 76.869 & 37.954 & 20.723 & 11.613 & 6.593 & 3.837 \\ 12.052 & 20.892 & 37.954 & 76.705 & 37.884 & 20.723 & 11.686 & 6.787 \\ 6.787 & 11.686 & 20.723 & 37.884 & 76.705 & 37.954 & 20.892 & 12.052 \\ 3.837 & 6.593 & 11.613 & 20.723 & 37.954 & 76.869 & 38.278 & 21.560 \\ 2.184 & 3.751 & 6.593 & 11.686 & 20.892 & 38.278 & 77.477 & 39.514 \\ 1.272 & 2.184 & 3.837 & 6.787 & 12.052 & 21.560 & 39.514 & 79.978 \end{pmatrix}$$

4) MATCHED LOADS

$$Z_c^{-1} = \begin{pmatrix} 0.017 & -8.241 \times 10^{-3} & -5.288 \times 10^{-4} & -1.093 \times 10^{-4} & -2.518 \times 10^{-5} & -5.943 \times 10^{-6} & -1.417 \times 10^{-6} & -3.902 \times 10^{-7} \\ -8.241 \times 10^{-3} & 0.021 & -7.979 \times 10^{-3} & -4.754 \times 10^{-4} & -9.696 \times 10^{-5} & -2.225 \times 10^{-5} & -5.309 \times 10^{-6} & -1.417 \times 10^{-6} \\ -5.288 \times 10^{-4} & -7.979 \times 10^{-3} & 0.021 & -7.976 \times 10^{-3} & -4.746 \times 10^{-4} & -9.680 \times 10^{-5} & -2.225 \times 10^{-5} & -5.943 \times 10^{-6} \\ -1.093 \times 10^{-4} & -4.754 \times 10^{-4} & -7.976 \times 10^{-3} & 0.021 & -7.976 \times 10^{-3} & -4.746 \times 10^{-4} & -9.696 \times 10^{-5} & -2.518 \times 10^{-5} \\ -2.518 \times 10^{-5} & -9.696 \times 10^{-5} & -4.746 \times 10^{-4} & -7.976 \times 10^{-3} & 0.021 & -7.976 \times 10^{-3} & -4.754 \times 10^{-4} & -1.093 \times 10^{-4} \\ -5.943 \times 10^{-6} & -2.225 \times 10^{-5} & -9.680 \times 10^{-5} & -4.746 \times 10^{-4} & -7.976 \times 10^{-3} & 0.021 & -7.979 \times 10^{-3} & -5.288 \times 10^{-4} \\ -1.417 \times 10^{-6} & -5.309 \times 10^{-6} & -2.225 \times 10^{-5} & -9.696 \times 10^{-5} & -4.754 \times 10^{-4} & -7.979 \times 10^{-3} & 0.021 & -8.241 \times 10^{-3} \\ -3.902 \times 10^{-7} & -1.417 \times 10^{-6} & -5.943 \times 10^{-6} & -2.518 \times 10^{-5} & -1.093 \times 10^{-4} & -5.288 \times 10^{-4} & -8.241 \times 10^{-3} & 0.017 \end{pmatrix} \quad S$$

$$R_{i,j} := \frac{-1}{(Z_c^{-1})_{i,j}}$$

$$R_{i,i} := \frac{1}{\sum_{j=1}^n (Z_c^{-1})_{i,j}}$$

Values of the resistances of a network of resistors having an impedance matrix equal to Z_c , presented as a matrix (the diagonal entries are the values of the grounded resistors).

$$R = \begin{pmatrix} 127.799 & 121.351 & 1.891 \times 10^3 & 9.152 \times 10^3 & 3.972 \times 10^4 & 1.683 \times 10^5 & 7.059 \times 10^5 & 2.563 \times 10^6 \\ 121.351 & 228.535 & 125.322 & 2.104 \times 10^3 & 1.031 \times 10^4 & 4.493 \times 10^4 & 1.884 \times 10^5 & 7.059 \times 10^5 \\ 1.891 \times 10^3 & 125.322 & 242.123 & 125.377 & 2.107 \times 10^3 & 1.033 \times 10^4 & 4.493 \times 10^4 & 1.683 \times 10^5 \\ 9.152 \times 10^3 & 2.104 \times 10^3 & 125.377 & 245.005 & 125.380 & 2.107 \times 10^3 & 1.031 \times 10^4 & 3.972 \times 10^4 \\ 3.972 \times 10^4 & 1.031 \times 10^4 & 2.107 \times 10^3 & 125.380 & 245.005 & 125.377 & 2.104 \times 10^3 & 9.152 \times 10^3 \\ 1.683 \times 10^5 & 4.493 \times 10^4 & 1.033 \times 10^4 & 2.107 \times 10^3 & 125.377 & 242.123 & 125.322 & 1.891 \times 10^3 \\ 7.059 \times 10^5 & 1.884 \times 10^5 & 4.493 \times 10^4 & 1.031 \times 10^4 & 2.104 \times 10^3 & 125.322 & 228.535 & 121.351 \\ 2.563 \times 10^6 & 7.059 \times 10^5 & 1.683 \times 10^5 & 3.972 \times 10^4 & 9.152 \times 10^3 & 1.891 \times 10^3 & 121.351 & 127.799 \end{pmatrix} \Omega$$

5) ORTHOGONALITY OF ASSOCIATED EIGENVECTORS

$$S \cdot S^T = \begin{pmatrix} 2.772 & 2.380 & 1.783 & 1.253 & 0.846 & 0.556 & 0.358 & 0.226 \\ 2.380 & 3.102 & 2.537 & 1.858 & 1.287 & 0.861 & 0.561 & 0.358 \\ 1.783 & 2.537 & 3.178 & 2.573 & 1.874 & 1.293 & 0.861 & 0.556 \\ 1.253 & 1.858 & 2.573 & 3.195 & 2.580 & 1.874 & 1.287 & 0.846 \\ 0.846 & 1.287 & 1.874 & 2.580 & 3.195 & 2.573 & 1.858 & 1.253 \\ 0.556 & 0.861 & 1.293 & 1.874 & 2.573 & 3.178 & 2.537 & 1.783 \\ 0.358 & 0.561 & 0.861 & 1.287 & 1.858 & 2.537 & 3.102 & 2.380 \\ 0.226 & 0.358 & 0.556 & 0.846 & 1.253 & 1.783 & 2.380 & 2.772 \end{pmatrix}$$

$$T \cdot T^T = \begin{pmatrix} 1.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 \\ 0.0000 & 1.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 \\ 0.0000 & 0.0000 & 1.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 \\ 0.0000 & 0.0000 & 0.0000 & 1.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 \\ 0.0000 & 0.0000 & 0.0000 & 0.0000 & 1.0000 & 0.0000 & 0.0000 & 0.0000 \\ 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 1.0000 & 0.0000 & 0.0000 \\ 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 1.0000 & 0.0000 \\ 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 0.0000 & 1.0000 \end{pmatrix}$$

Thus, the column-vectors of S (eigen-voltages) are not orthogonal, but the column-vectors of T (eigen-currents) are orthogonal.

6) MODAL INDUCTANCE MATRIX AND MODAL CAPACITANCE MATRIX, FOR ASSOCIATED EIGENVECTORS

$$L_m := S^{-1} \cdot L_0 \cdot T$$

$$C_m := T^{-1} \cdot C \cdot S$$

$$10^9 L_m = \begin{pmatrix} 311.542 & -3.139 \times 10^{-14} & -1.777 \times 10^{-14} & -1.614 \times 10^{-14} & -2.104 \times 10^{-15} & -7.114 \times 10^{-15} & -2.852 \times 10^{-15} & -2.331 \times 10^{-15} \\ -1.478 \times 10^{-14} & 311.542 & -4.832 \times 10^{-14} & -3.299 \times 10^{-15} & -7.094 \times 10^{-15} & -6.145 \times 10^{-15} & -1.917 \times 10^{-15} & 1.262 \times 10^{-15} \\ -2.636 \times 10^{-14} & -3.212 \times 10^{-14} & 311.542 & -6.829 \times 10^{-15} & -1.030 \times 10^{-14} & 9.968 \times 10^{-17} & 1.243 \times 10^{-15} & -1.027 \times 10^{-15} \\ -1.031 \times 10^{-14} & -7.195 \times 10^{-15} & -2.901 \times 10^{-14} & 311.542 & -2.227 \times 10^{-14} & -1.029 \times 10^{-14} & -8.843 \times 10^{-15} & -1.596 \times 10^{-14} \\ 5.078 \times 10^{-15} & -1.065 \times 10^{-14} & 7.759 \times 10^{-15} & 1.607 \times 10^{-14} & 311.542 & -6.588 \times 10^{-15} & 3.888 \times 10^{-15} & 3.115 \times 10^{-14} \\ 9.722 \times 10^{-15} & 1.581 \times 10^{-14} & 3.657 \times 10^{-14} & 4.203 \times 10^{-14} & 1.199 \times 10^{-14} & 311.542 & 6.764 \times 10^{-14} & 1.356 \times 10^{-14} \\ -8.609 \times 10^{-15} & -1.310 \times 10^{-14} & -2.748 \times 10^{-14} & -3.632 \times 10^{-14} & -6.019 \times 10^{-14} & -1.816 \times 10^{-13} & 311.542 & -1.231 \times 10^{-13} \\ 4.160 \times 10^{-17} & 1.414 \times 10^{-16} & 2.730 \times 10^{-15} & -1.049 \times 10^{-14} & 5.616 \times 10^{-15} & -5.125 \times 10^{-15} & 1.092 \times 10^{-14} & 311.542 \end{pmatrix} \quad \text{nH/m}$$

$$10^{12} C_m = \begin{pmatrix} 100 & -2.265 \times 10^{-15} & -2.577 \times 10^{-15} & 1.473 \times 10^{-15} & -8.685 \times 10^{-16} & 9.493 \times 10^{-16} & 1.246 \times 10^{-16} & 2.548 \times 10^{-16} \\ 2.435 \times 10^{-15} & 100 & 2.201 \times 10^{-15} & -9.185 \times 10^{-16} & 2.908 \times 10^{-15} & 5.915 \times 10^{-16} & 9.604 \times 10^{-17} & -5.367 \times 10^{-16} \\ 5.506 \times 10^{-15} & 1.519 \times 10^{-14} & 100 & 1.53 \times 10^{-14} & -1.117 \times 10^{-15} & 1.549 \times 10^{-15} & 7.077 \times 10^{-16} & 1.087 \times 10^{-15} \\ 8.469 \times 10^{-16} & 7.196 \times 10^{-16} & 6.63 \times 10^{-15} & 100 & 1.493 \times 10^{-14} & 3.615 \times 10^{-16} & 1.232 \times 10^{-15} & 1.5 \times 10^{-15} \\ 1.685 \times 10^{-15} & 2.124 \times 10^{-15} & -4.243 \times 10^{-15} & 1.797 \times 10^{-14} & 100 & 1.54 \times 10^{-15} & -1.909 \times 10^{-16} & -1.45 \times 10^{-15} \\ -1.256 \times 10^{-15} & -6.702 \times 10^{-16} & -3.756 \times 10^{-15} & -6.098 \times 10^{-15} & -2.805 \times 10^{-15} & 100 & -4.289 \times 10^{-15} & -1.52 \times 10^{-15} \\ 1.465 \times 10^{-15} & 2.315 \times 10^{-15} & 4.614 \times 10^{-15} & 7.937 \times 10^{-15} & 1.305 \times 10^{-14} & 3.112 \times 10^{-14} & 100 & 1.799 \times 10^{-14} \\ -1.061 \times 10^{-16} & -9.506 \times 10^{-17} & 6.035 \times 10^{-17} & 7.534 \times 10^{-16} & 1.251 \times 10^{-15} & -3.253 \times 10^{-15} & -4.146 \times 10^{-15} & 100 \end{pmatrix} \quad \text{pF/m}$$

As expected, L_m and C_m are diagonal matrices, within the accuracy of our computation. Here C_m is

$$10^{12} \text{ck-identity}(n) = \begin{pmatrix} 100 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 100 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 100 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 100 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 100 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 100 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 100 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 100 \end{pmatrix} \quad \text{pF/m}$$

7) MODAL CHARACTERISTIC IMPEDANCE MATRIX, FOR BIORTHONORMAL EIGENVECTORS

$$Z_{mc} := \text{diag}(c_i) \cdot T^T \cdot L_0 \cdot T$$

$$Z_{mc} = \begin{pmatrix} 79.978 & 39.514 & 21.560 & 12.052 & 6.787 & 3.837 & 2.184 & 1.272 \\ 39.514 & 77.477 & 38.278 & 20.892 & 11.686 & 6.593 & 3.751 & 2.184 \\ 21.560 & 38.278 & 76.869 & 37.954 & 20.723 & 11.613 & 6.593 & 3.837 \\ 12.052 & 20.892 & 37.954 & 76.705 & 37.884 & 20.723 & 11.686 & 6.787 \\ 6.787 & 11.686 & 20.723 & 37.884 & 76.705 & 37.954 & 20.892 & 12.052 \\ 3.837 & 6.593 & 11.613 & 20.723 & 37.954 & 76.869 & 38.278 & 21.560 \\ 2.184 & 3.751 & 6.593 & 11.686 & 20.892 & 38.278 & 77.477 & 39.514 \\ 1.272 & 2.184 & 3.837 & 6.787 & 12.052 & 21.560 & 39.514 & 79.978 \end{pmatrix}$$

Ω

In this example, Z_{mc} is not a diagonal matrix.
We note that Z_{mc} is different in section 3 and in section 7.

8) MODAL INDUCTANCE MATRIX AND MODAL CAPACITANCE MATRIX, FOR BIORTHONORMAL EIGENVECTORS

$$L_m := T^T \cdot L_0 \cdot T$$

$$C_m := T^{-1} \cdot C \cdot (T^{-1})^T$$


$$10^9 L_m = \begin{pmatrix} 446.404 & 220.552 & 120.338 & 67.269 & 37.881 & 21.415 & 12.190 & 7.099 \\ 220.552 & 432.448 & 213.654 & 116.608 & 65.225 & 36.801 & 20.936 & 12.190 \\ 120.338 & 213.654 & 429.050 & 211.844 & 115.666 & 64.819 & 36.801 & 21.415 \\ 67.269 & 116.608 & 211.844 & 428.134 & 211.454 & 115.666 & 65.225 & 37.881 \\ 37.881 & 65.225 & 115.666 & 211.454 & 428.134 & 211.844 & 116.608 & 67.269 \\ 21.415 & 36.801 & 64.819 & 115.666 & 211.844 & 429.050 & 213.654 & 120.338 \\ 12.190 & 20.936 & 36.801 & 65.225 & 116.608 & 213.654 & 432.448 & 220.552 \\ 7.099 & 12.190 & 21.415 & 37.881 & 67.269 & 120.338 & 220.552 & 446.404 \end{pmatrix}$$

nH/m

$$10^{12} \cdot \mathbf{C}_m = \begin{pmatrix} 93.415 & -45.995 & -2.952 & -0.610 & -0.141 & -0.033 & -7.907 \times 10^{-3} & -2.178 \times 10^{-3} \\ -45.995 & 118.313 & -44.538 & -2.653 & -0.541 & -0.124 & -0.030 & -7.907 \times 10^{-3} \\ -2.952 & -44.538 & 118.408 & -44.519 & -2.649 & -0.540 & -0.124 & -0.033 \\ -0.610 & -2.653 & -44.519 & 118.412 & -44.517 & -2.649 & -0.541 & -0.141 \\ -0.141 & -0.541 & -2.649 & -44.517 & 118.412 & -44.519 & -2.653 & -0.610 \\ -0.033 & -0.124 & -0.540 & -2.649 & -44.519 & 118.408 & -44.538 & -2.952 \\ -7.907 \times 10^{-3} & -0.030 & -0.124 & -0.541 & -2.653 & -44.538 & 118.313 & -45.995 \\ -2.178 \times 10^{-3} & -7.907 \times 10^{-3} & -0.033 & -0.141 & -0.610 & -2.952 & -45.995 & 93.415 \end{pmatrix} \quad \text{pF/m}$$

In this example, \mathbf{L}_m and \mathbf{C}_m are not diagonal matrices.
 We note that \mathbf{L}_m and \mathbf{C}_m are different in section 6 and in section 8.

[Back to the link "Annex B" of § 7](#)

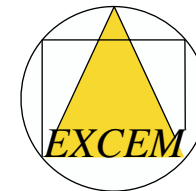

Editeur:
Excem
12, chemin des Hauts de Clairefontaine
78580 Maule, France
<http://www.eurexcem.com>

Imprimeur:
2IP Communication
21 bis, Côte de Beulle
78580 Maule, France

Achevé d'imprimer en février 2012.

Dépôt légal: février 2012.

Imprimé en France

Seminar 32

Tutorial on Echo and Crosstalk in Printed Circuit Boards and Multi-Chip Modules — Lecture Slides

Part A — Propagation models

1. Introduction and definitions
2. The 2-conductor transmission line in the frequency domain
3. Problems involving a TL and linear terminations
4. Telegrapher's equations of a uniform MTL and modal decomposition
5. The characteristic impedance matrix
6. Biorthonormal eigenvectors and associated eigenvectors
7. The choice of eigenvectors and total decoupling
8. Propagation in the frequency domain
9. Matched termination circuit and pseudo-matched terminations
10. Problems involving an MTL and linear terminations

Part B — Techniques for reducing crosstalk and echo

11. The degradation of transmitted signals
12. Single-ended parallel links
13. Multichannel differential links
14. Modal signaling
15. Modal signaling in a decoupled interconnection
16. Pseudo-differential links

Appendix

Bibliography

Annexes

Frédéric Broydé received an M.S. degree in physics engineering and a Ph.D. in microwaves and microtechnologies. He is the chief technical officer of Excem and he directly takes part in engineering or R&D projects related to electromagnetic compatibility (EMC) and signal integrity. He is a Senior Member of the IEEE.

Evelyne Clavelier received the M.S. degree in physics engineering in 1984. She co-founded Excem in 1988. She is currently the chief executive officer of Excem, where she is also active as a senior R&D engineer. She is a Senior Member of the IEEE since 2002.

Frédéric Broydé and Evelyne Clavelier are authors or co-authors of more than 80 technical papers, and inventors or co-inventors for more than 50 patent families.

Excem

12, chemin des Hauts de Clairefontaine
78580 Maule - France

<http://www.eurexcem.com>

ISBN 978-2-909056-06-7



ISBN 978-2-909056-06-7



9 782909 056067 >